


EE 240C

Analog-Digital Interface Integrated Circuits

Comparators – Latch

Regenerative Sense Amplifier (Latch)

 
$t < 0$ setup initial condition $v_{10} - v_{20} = v_{d0}$
 $t \geq 0$ enable positive feedback



$$\frac{dv_1}{dt} = \frac{i_1(t)}{C} = \frac{-g_m v_2(t)}{C}$$

$$\frac{dv_2}{dt} = \frac{i_2(t)}{C} = \frac{-g_m v_1(t)}{C}$$



$$\tau_u = \frac{C}{g_m}$$

 


$$\Rightarrow v_1(t) - v_2(t) = v_d(t) = v_{d0} \cdot e^{t/\tau_u}$$

$$\Rightarrow A(t) = \frac{v_d(t)}{v_{d0}} = e^{t/\tau_u}$$

Regenerative Sense Amplifier (Latch)

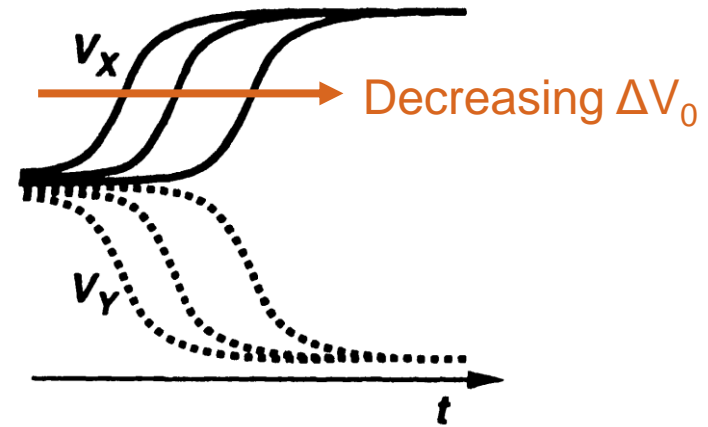 


 [Razavi, "Principles of Data Conversion System Design"]



[Pelgrom, "Analog to Digital Conversion", 3rd Ed]

Comparison

 

- Latch is much faster than cascade of amplifiers/integrators

Latch "Gain"

$A(\tau_d)$	τ_d/τ_u
10	2.3
100	4.6
1,000	6.9
10,000	9.2

Metastability (1)

- References

- H. J. Veendrick, “The behaviour of flip-flops used as synchronizers and prediction of their failure rate,” *JSSC*, Apr. 1980
- P. M. Figueiredo, “Comparator metastability in the presence of noise,” *TCAS-I*, May 2013.

- Consider minimum initial latch input voltage needed to regenerate to V_{DD} within maximum available time T_{\max}

$$V_{d0\min} = \frac{V_{DD}}{e^{T_{\max}/\tau_u}}$$

- Minimum required pre-amplifier input:

$$V_{id0\min} = \frac{1}{A_v} \frac{V_{DD}}{e^{T_{\max}/\tau_u}}$$


- Probability of seeing a metastable output:

$$P(\text{Error}) = P(|V_{id0}| < V_{id0\min})$$

Metastability (2)

- Assuming a uniform input signal distribution over some range, we have
 
$$P(\text{Error}) = \frac{V_{id0min}}{V_{id0max}}$$



- In a *flash ADC*, only one out of all comparators can be metastable. The effective input range V_{id0max} over which the signal is distributed is therefore $\frac{1}{2}$ LSB ($\Delta/2$)

$$\therefore P(\text{Error}) = \frac{V_{id0min}}{V_{id0max}} = \frac{\frac{1}{A_v} \frac{V_{DD}}{e^{T_{max}/\tau_u}}}{\frac{\Delta}{2}} = \frac{\frac{1}{A_v} \frac{V_{DD}}{e^{T_{max}/\tau_u}}}{\frac{V_{FS}}{2 \cdot 2^B}} = \frac{2^{B+1}}{A_v} \frac{V_{DD}}{V_{FS}} e^{-T_{max}/\tau_u}$$

Metastability (3)

- Example: 6-bit, 500MHz Flash ADC, $T_{\max} = T_s/2 = 1\text{ns}$,
 $\tau_u = 1/(2\pi \cdot 5\text{GHz}) = 32\text{ps}$, $A_v = 3$, $V_{FS} = 0.5V_{DD}$

$$P(\text{Error}) = \frac{2^{6+1}}{3} \cdot 2 \cdot e^{-1000/32} \cong 2 \cdot 10^{-12}$$

- Mean time to failure (MTF)

$$MTF = \frac{1}{P(\text{Error}) \cdot f_s} = \frac{1}{2 \cdot 10^{-12} \cdot 0.5 \cdot 10^9} \text{s} = 1000\text{s} \cong 16 \text{ minutes}$$


- Ideally design for $MTF > 1 \dots 10$ years (not always possible)
- Can improve MTF by
 - Reducing speed (larger T_{\max}/τ_u)
 - Exponential dependence
 - Adding pre-amplifier gain
 - Linear dependence

EE 240C

Analog-Digital Interface Integrated Circuits

Comparators – Offset

Dynamic Offset

 


$$\Delta C = C_1 - C_2$$

- $C_1 \neq C_2$ causes dynamic offset:
- Can show $V_{os} \cong 0.5 \cdot \Delta C / C \cdot (V_{(t=0)} - V_S)$;
 V_S = inverter switching voltage
 - Nikoozadeh & Murmann, IEEE TCAS II, Dec. 2006.
- Example
 - $0.5 \cdot 10\text{fF} / 100\text{fF} \cdot (1\text{V} - 0.5\text{V}) = 25\text{mV}$ (!)
 - symmetrical layout (incl. routing !)

Dynamic Offset

- Dynamic offset can be caused by signal-dependent capacitive loading of the comparator
 - capacitive load depends on previous decision
 - comparator hysteresis
- Example: logic gates being driven by comparator

Input Referred Offset

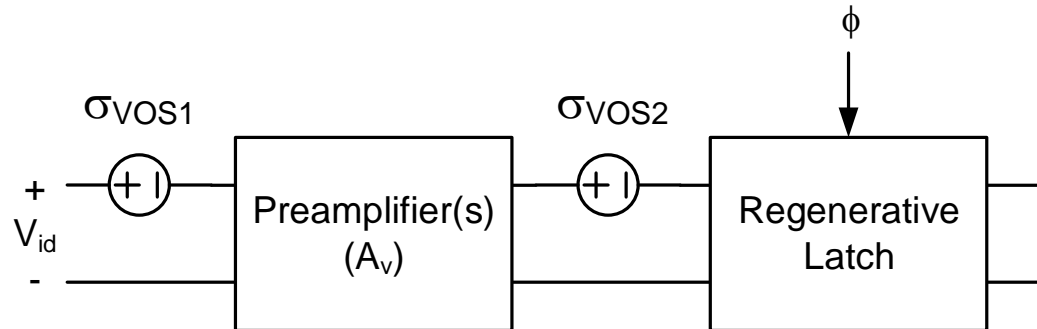


$$\sigma_{VOS}^2 = \sigma_{VOS1}^2 + \frac{1}{A_v^2} \sigma_{VOS2}^2$$

- Example: $\sigma_{VOS1}=3mV$, $\sigma_{VOS2}=30mV$, $A_v=10$


$$\sigma_{VOS} = \sqrt{(3mV)^2 + \frac{1}{10^2} (30mV)^2} = 4.2mV$$

Offset Cancellation

OUTPUT SERIES CANCELLATION

 


INPUT SERIES CANCELLATION

 

Output Series Cancellation


Ref: Poujois, et al., JSSC 8/78

 

- Phase 1: Offset storage, phase 2: Amplify
- Design considerations
 - Must ensure that amplifier does not saturate during phase 1
 - Must make C sufficiently large to avoid attenuation and mitigate charge injection error

Input Series Cancellation

Refs: McCreary & Gray
Yee, et al.

 

- Phase 1: Offset storage, phase 2: Amplify
- In phase 2, input referred offset is $\approx V_{os}/(A+1)$
 - 4x reduction if $A=3$


EE 240C

Analog-Digital Interface Integrated Circuits



Comparators - Noise

Noise in Comparators

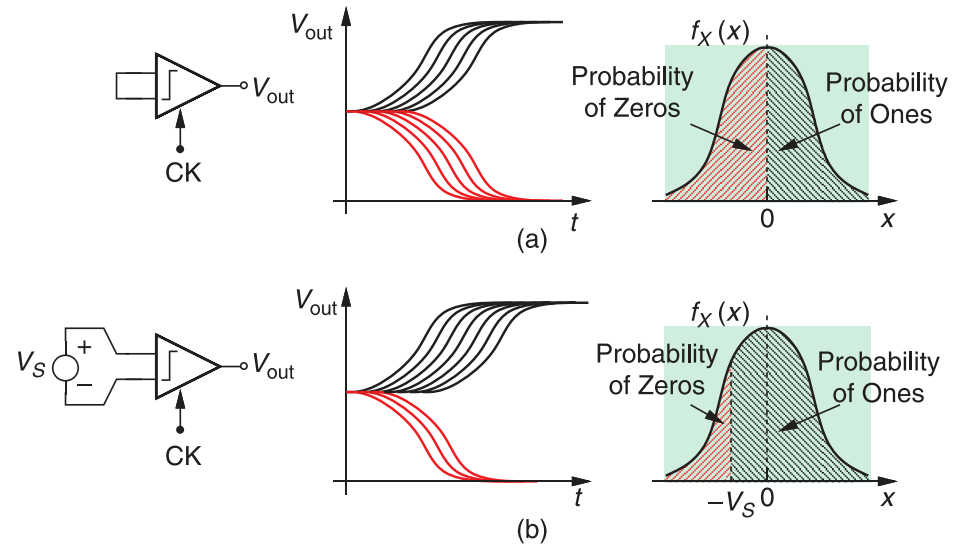- Comparator noise randomizes decisions around transition point
 - At transition point:
 $P_0 = P_1 = 0.5$
 - $P_0 = 1 - P_1$ increases below transition point;
 $P_1 = 1 - P_0$ increases above transition point
- P_0, P_1 as a function of (cumulative) distribution function of comparator noise


  
$$\begin{aligned}
 P_0 &= P(V_{in} + v_n \leq 0) & P_1 &= P(V_{in} + v_n \leq 0) \\
 &= P(v_n \leq -V_{in}) & &= P(v_n \leq -V_{in}) \\
 &= F_{v_n}(-V_{in}) & &= 1 - F_{v_n}(-V_{in})
 \end{aligned}$$



[I. Opris, "Noise estimation in strobed comparators,"
Electronics Letters, vol. 33, no. 15, pp. 1273–1274, Jul. 1997]


- Comparator has a noisy transition region between 0 and 1
- Usually dominated by noise of pre-amplifier

EE 240C

Analog-Digital Interface Integrated Circuits

Comparators - Examples


Commercial Example: AD7671

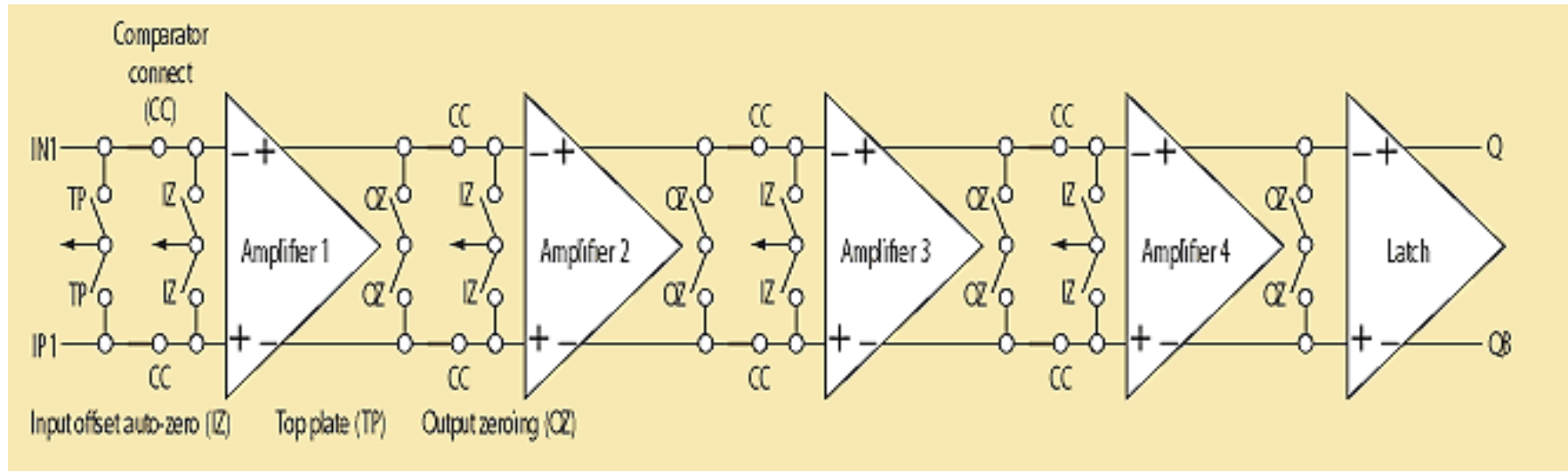

- Used in 16-bit, 1 MS/s successive approximation ADC, 0.6 μm CMOS technology
- Uses cascaded output series offset cancellation
- Offset < 3 mV (over process, temperature)


Comparator Examples (1a)

- Mehr & Dalton, JSSC 7/1999

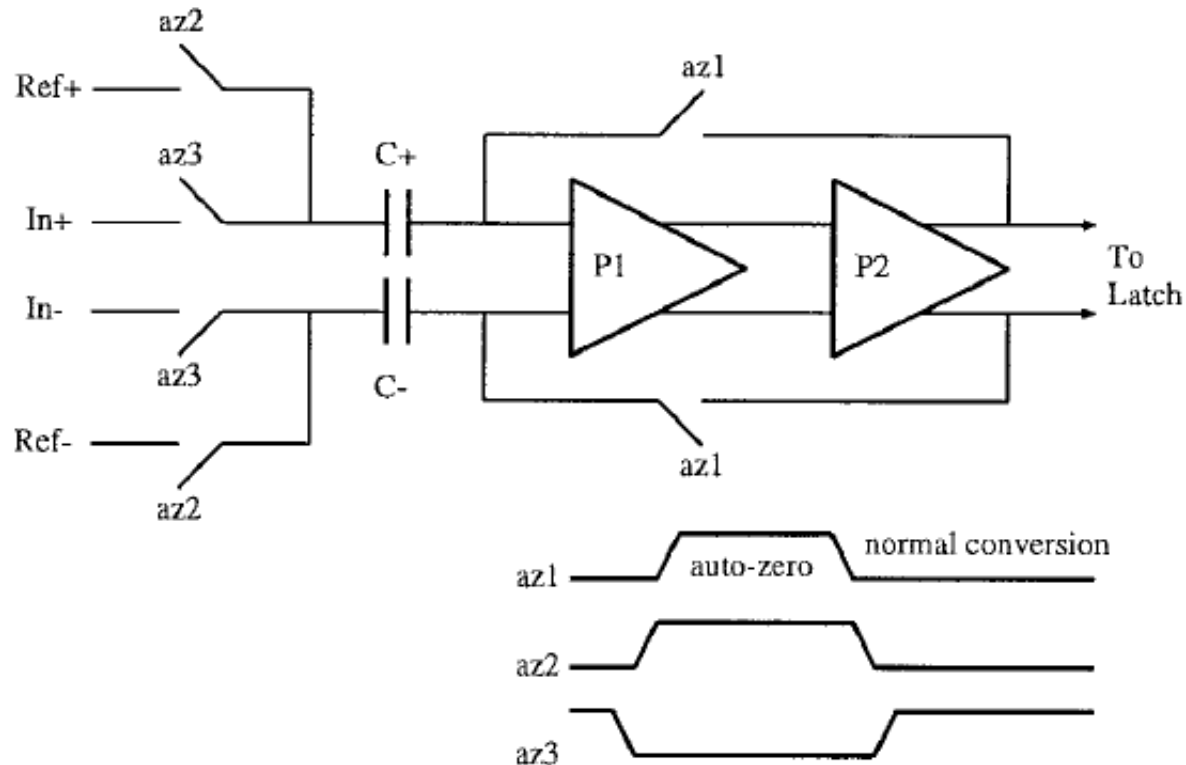

Comparator Examples (2)


- Mehr & Singer, JSSC 3/2000

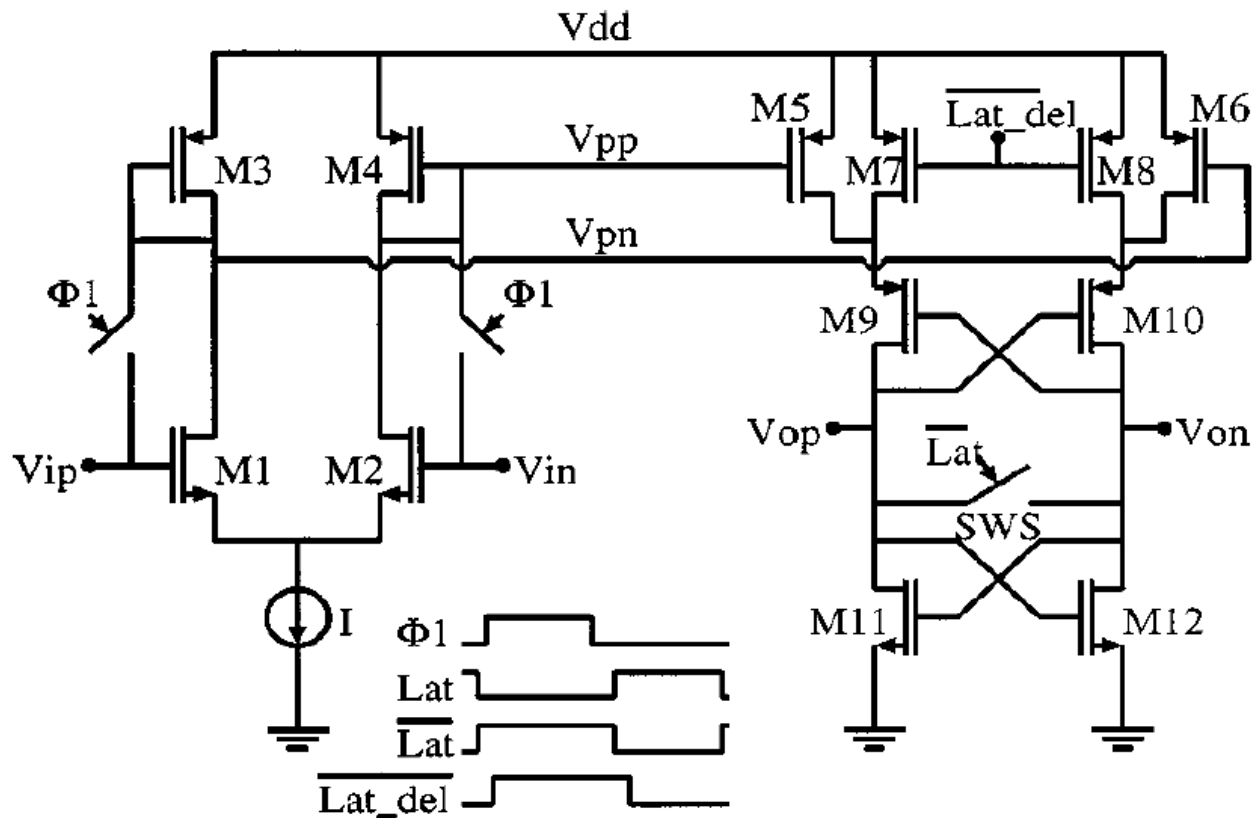

Comparator Examples (3a)


- Purely dynamic "sense amplifier"
 - No DC current
 - Headroom problems with low V_{DD}
 - Sensitive to V_{icm}
 - Offset–speed tradeoff:
 - Narrow M9 for low offset
 - Wide M9 for high speed

 [B. Razavi, "The StrongARM latch",
IEEE Solid- State Circuits Mag.,
vol. 7, no. 2, pp. 12–17, Spring 2015]



StrongARM Latch


 
- Phase 0: Reset \rightarrow internal latch nodes reset to V_{DD}
- Phase 1: Dynamic amplification



- $\Delta T_1 = \frac{C_P V_{thn}}{I_{tail}/2}$
- Dynamic amplification: $A_v = \frac{g_{m1,2}}{C_P} \Delta T_1 = \frac{g_{m1,2} V_{thn}}{I_{tail}/2}$
- Dynamic input-referred offset: $V_{offset} \approx \Delta C_P \frac{V_{thn}}{g_{m1,2} \Delta T_1} = \frac{\Delta C_P}{C_P} \frac{I_{tail}/2}{g_{m1,2}}$
- Input-referred noise: $v_n^2 \approx (2 \frac{k T}{C_P} + 2 \frac{4kT\gamma g_{m1,2}}{C_P^2} \Delta T_1) / A_v^2$

StrongARM Latch

  - Phase 3: Regeneration
 - Phase 3a: cross-coupled NMOS only
 - Phase 3b: cross-coupled NMOS & PMOS



- Power consumption: $P \approx f_{\text{clock}}(2C_P + C_L)V_{DD}^2$

Comparator Examples (3b)

- Schinkel, ISSCC 2007: "Double tail sense amplifier"

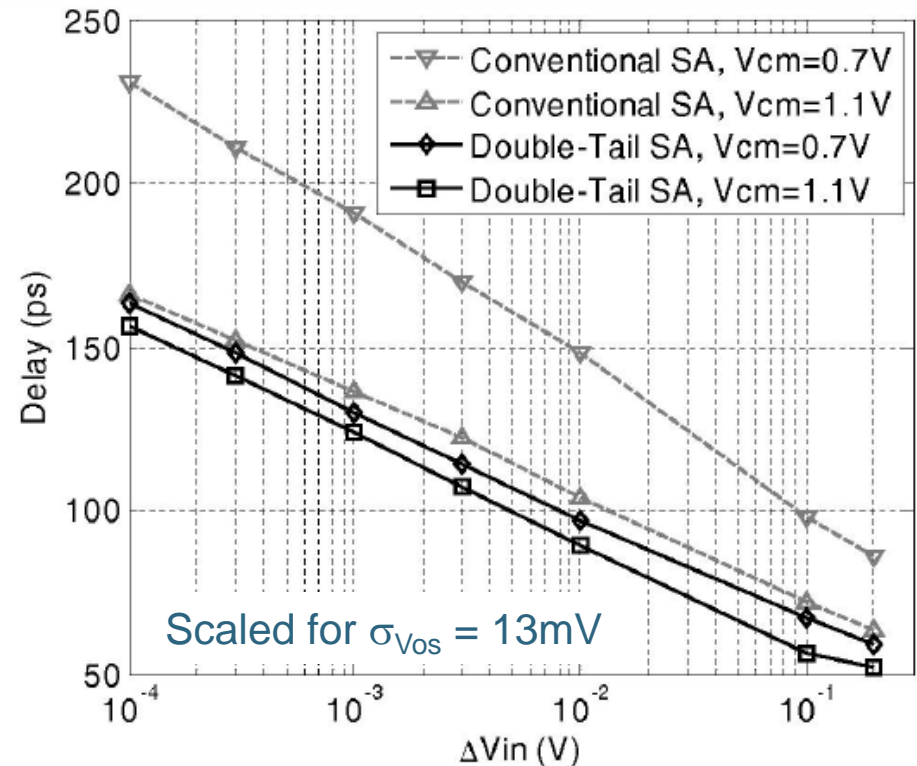
 


Figure 17.7.3: Simulated sense amplifier delays versus differential input voltage. The delay is the time between the clock edge and the instant when ΔOut crosses $1/2 V_{DD}$.

Narrow M9 (low offset) and wide M12 (fast)

Selected References (1)

1. R. Poujois and J. Borel, "A Low Drift Fully Integrated MOSFET Operational Amplifier," *IEEE J. of Solid-State Circuits*, pp. 499–503, Aug. 1978.
2. H.-S. Lee, D. A. Hodges and P. R. Gray, "A Self-Calibrating 15 Bit CMOS A/D Converter," *IEEE J. of Solid-State Circuits*, vol. SC-19, pp. 813–819, Dec. 1984.
3. J. L. McCreary and P. R. Gray, "All-MOS Charge Redistribution Analog-to-Digital Conversion Techniques — Part I," *IEEE J. of Solid-State Circuits*, vol. SC-10, no. 6, pp. 371–379, Dec. 1975.
4. Y. S. Yee, L. M. Terman and L. G. Heller, "A 1mV MOS Comparator," *IEEE J. of Solid-State Circuits*, vol. SC-13, pp. 294–297, June 1978.
5. A. Yukawa, "A CMOS 8-Bit High-Speed A/D Converter IC," *IEEE J. of Solid-State Circuits*, vol. SC-20, pp. 775–779, June 1985.
6. B. J. McCarroll, C. G. Sodini, and H.-S. Lee, "A High-Speed CMOS Comparator for Use in an ADC," *IEEE J. of Solid-State Circuits*, vol. 23, pp. 159–165, Feb. 1988.
7. J.-T. Wu and B. A. Wooley, "A 100-MHz Pipelined CMOS Comparator," *IEEE J. Solid-State Circuits*, vol. 23, pp. 1379–1385, Dec. 1988.
8. B. Razavi and B. A. Wooley, "A 12-b 5-MSample/s Two-Step CMOS A/D Converter," *IEEE J. Solid-State Circuits*, vol. 27, pp. 1667–1678, Dec. 1992.
9. B. Razavi and B. A. Wooley, "Design Techniques for High-Speed, High-Resolution Comparators," *IEEE J. Solid-State Circuits*, vol. 27, pp. 1916–1926, Dec. 1992.

Selected References (2)


9. M. Choi and A. A. Abidi, "A 6-b 1.3-GSample/s A/D converter in 0.35- μ m CMOS," *IEEE J. Solid-State Circuits*, pp. 1847–1858, Dec. 2001.
10. I. Mehr and D. Dalton, "A 500-MSample/s, 6-bit Nyquist-rate ADC for disk-drive read-channel applications," *IEEE J. Solid-State Circuits*, pp. 912–920, July 1999.
11. I. Mehr and L. Singer, "A 55-mW, 10-bit, 40-MSample/s Nyquist-Rate CMOS ADC," *IEEE J. Solid-State Circuits*, pp. 318–25, March 2000.
12. H. J. M. Veendrick, "The Behavior of Flip-Flops Used as Synchronizers and Prediction of Their Failure Rate," *IEEE J. Solid-State Circuits*, April 1980.
13. B. Zojer, et al., "A 6-bit/200-MHz full Nyquist A/D converter," *IEEE J. Solid-State Circuits*, vol. SC-20, pp. 780–786, June 1985.
14. K.-L.J. Wong and C.-K.K. Yang, "Offset compensation in comparators with minimum input-referred supply noise," *IEEE J. Solid-State Circuits*, vol.39, pp. 837–840, May 2004.
15. A. Graupner, "A Methodology for the Offset-Simulation of Comparators," <http://www.designers-guide.org/Analysis/comparator.pdf>.
16. D. Schinkel et al., "A Double-Tail Latch-Type Voltage Sense Amplifier with 18ps Setup+Hold Time," *ISSCC Dig. Techn. Papers*, pp. 314–315, 2007.
17. P.P. Nuzzo, et al., "Noise Analysis of Regenerative Comparators for Reconfigurable ADC Architectures, *IEEE Trans. Circuits Syst. I*, pp.1441–1454, July 2008.
18. B.S. Leibowitz, et al., "Characterization of Random Decision Errors in Clocked Comparators," *Proc. IEEE CICC*, pp.691–694, Sep. 2008.

EE 240C

Analog-Digital Interface Integrated Circuits

Successive Approximation ADC


Successive Approximation Register ADC

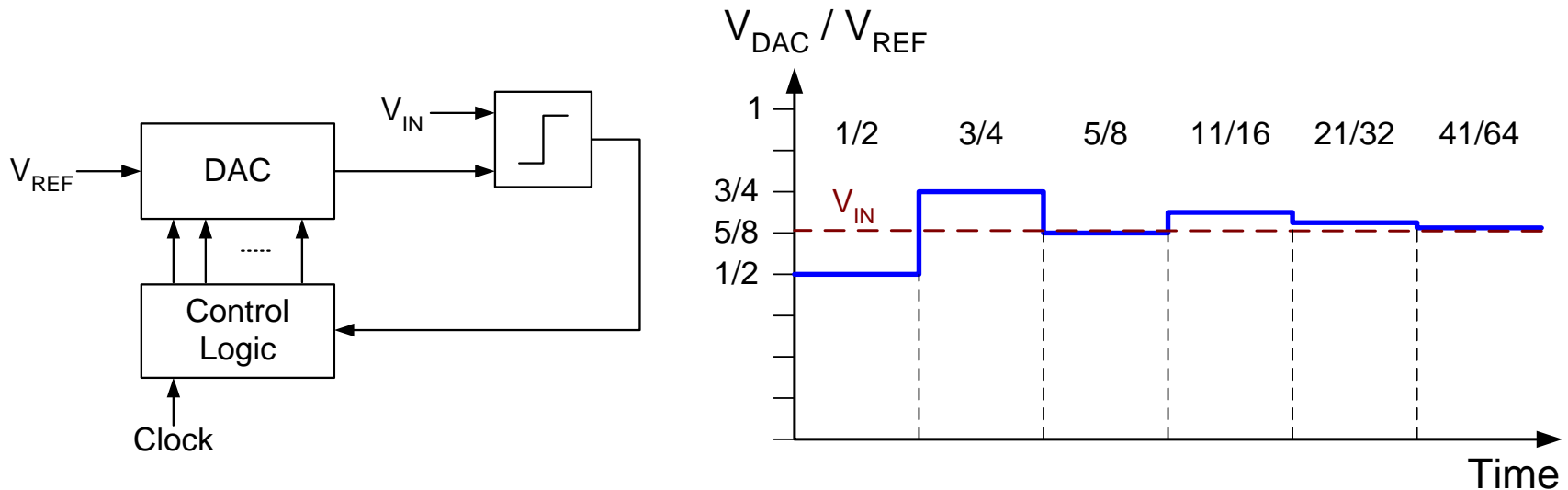

- Binary search over DAC output
- High accuracy achievable (16+ Bits)
 - Relies on highly accurate comparator
 - No amplifier
- Moderate speed (1+ + MHz)

High Performance Example

FUNCTIONAL BLOCK DIAGRAM

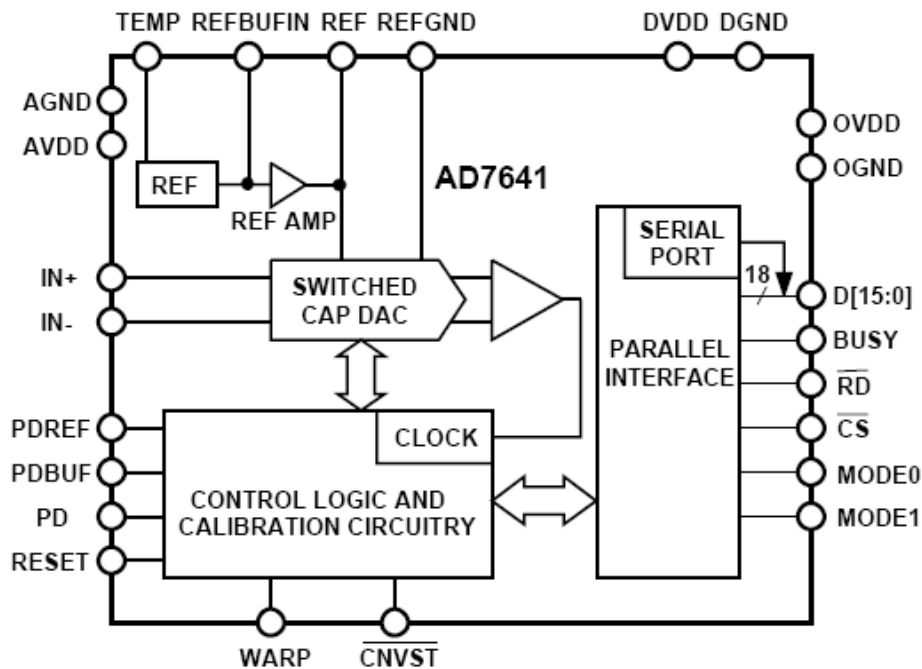

FEATURES

Throughput:

2 MSPS (Warp mode)

1.5 MSPS (Normal mode)

18-bit resolution with no missing codes

2.048V internal low drift reference

INL: ± 2 LSB typical

S/(N+D): 93 dB typical @ 20 kHz

THD: -115 dB typical @ 20 kHz

Differential input range: $\pm V_{REF}$ (V_{REF} up to 2.5 V)

No pipeline delay (SAR architecture)

Parallel (18-, 16-, or 8-bit bus)


Serial 5 V/3.3 V/2.5 V interface

SPI®/QSPI™/MICROWIRE™/DSP compatible

Single 2.5 V supply operation

Power dissipation: 65 mW typical @ 2 MSPS

Low Power Example

 


SUMMARY OF ADC PERFORMANCE

Performance Metric	Value
Voltage supply	1 V (nominal)
Input range	Rail-to rail
Sampling rate	100 kHz
Unit capacitance	12 fF
DNL	$< \pm 0.5$ LSB typical
INL	$< \pm 0.5$ LSB typical
ENOB (1V)	7.9 (DC), 7.0 (4.61 kHz)
Power dissipation (1V)	3.1 μW
Energy per sample (1V)	31 pJ
Standby power (1V)	70 pW
Die area (active)	0.053 mm^2
Process	0.25 μm CMOS (2P5M)

M.D. Scott, B.E. Boser, K.S.J. Pister, "An ultralow-energy ADC for Smart Dust," IEEE J. Solid-State Circuits, pp. 1123 -1129, July 2003.

Implementation

- See e.g. [McCreary, JSSC 12/1975]

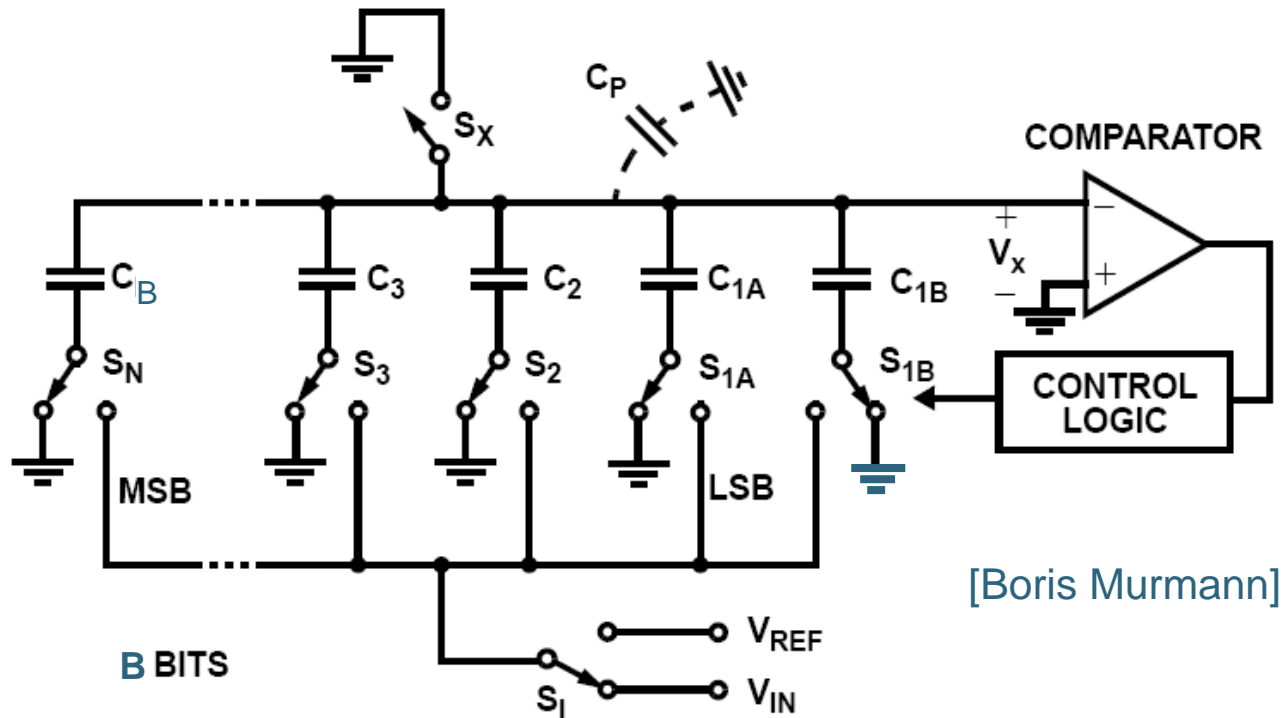

$$C_{1A} = C_{1B} = C$$


$$C_2 = 2C$$

$$C_3 = 4C$$

$$C_B = 2^{B-1}C$$

$$C_{TOTAL} = 2^B C$$


Sampling Phase (5-bit Example)

 

- Total charge at node V_x after opening S_x

$$Q = -V_{in} \cdot 32C = -V_{in} \cdot C_{total}$$

Bit5 Test (MSB)

 


$$Q = -V_{in} \cdot C_{total} = (V_x - V_{ref}) \cdot 16C + V_x \cdot (16C + C_p)$$

$$\therefore V_x = \left(\frac{1}{2} V_{ref} - V_{in} \right) \cdot \frac{C_{total}}{C_{total} + C_p}$$

- $V_x < 0 \Rightarrow V_{in} > 0.5V_{ref} \Rightarrow \text{Bit5} = 1$
- $V_x > 0 \Rightarrow V_{in} < 0.5V_{ref} \Rightarrow \text{Bit5} = 0$

Bit4 Test (Assuming bit5=0)

 


$$Q = -V_{in} \cdot C_{total} = (V_x - V_{ref}) \cdot 8C + V_x \cdot (24C + C_p)$$

$$\therefore V_x = \left(\frac{1}{4} V_{ref} - V_{in} \right) \cdot \frac{C_{total}}{C_{total} + C_p}$$

- $V_x < 0 \Rightarrow V_{in} > 0.25V_{ref} \Rightarrow \text{Bit4} = 1$
- $V_x > 0 \Rightarrow V_{in} < 0.25V_{ref} \Rightarrow \text{Bit4} = 0$

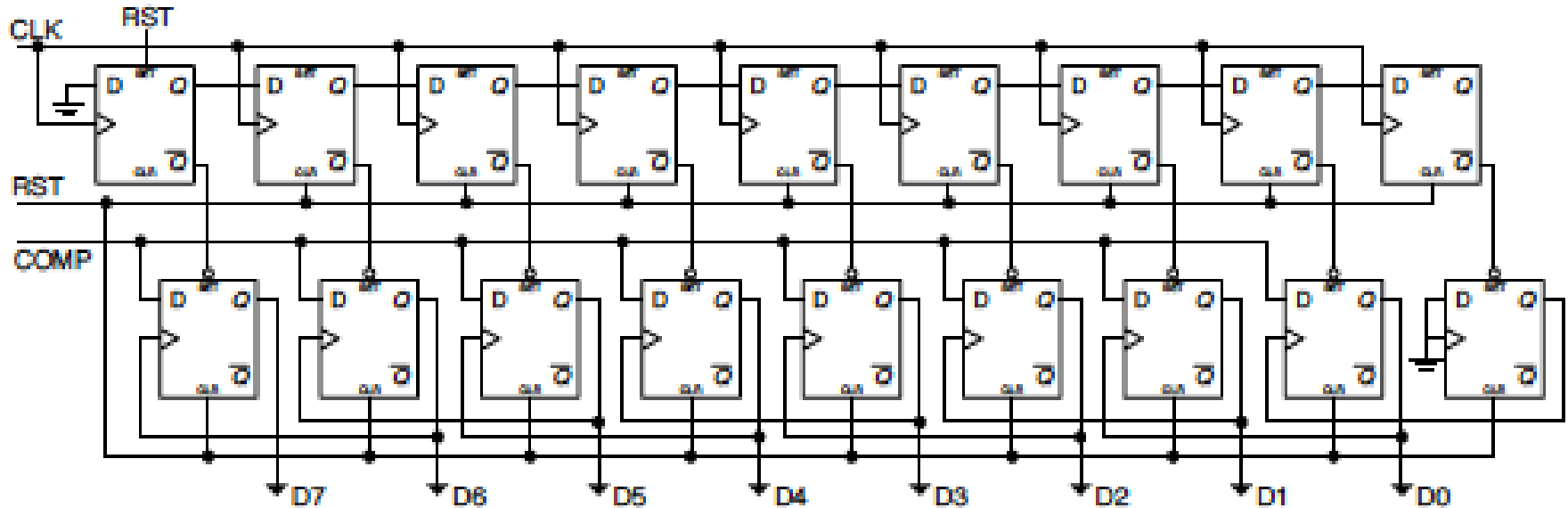© 2013 Pearson Education, Inc. or its affiliate(s). All rights reserved. This material is intended solely for the personal use of the individual user and is not to be disseminated broadly.



[M.D. Scott, B.E. Boser, K.S.J. Pister, "An ultralow-energy ADC for Smart Dust," IEEE J. Solid-State Circuits, pp. 1123 -1129, July 2003.]

- One register to store “1” for bit tests
- One register to store comparator results

Limitations

- Conversion rate typically limited by finite bandwidth of RC network during sampling and bit-tests
- For high resolution, the binary weighted capacitor array can become quite large
 - E.g. 16-bit resolution, $C_{\text{total}} \sim 100\text{pF}$ for reasonable kT/C noise contribution
- If matching is an issue, an even larger value may be needed
 - E.g. if matching dictates $C_{\text{min}} = 10\text{fF}$, then $2^{16}C_{\text{min}} = 655\text{pF}$
- Commonly used techniques
 - Implement "two-stage" or "multi-stage" capacitor network to reduce array size [Yee, JSSC 8/79]
 - Calibrate capacitor array to obtain precision beyond raw technology matching [Lee, JSSC 12/84]

SAR Techniques

- Small custom unit capacitors for low- to mid-resolution SAR ADC
- DAC schemes and switching schemes for low power or lower area
- Self-timed comparator or asynchronous SAR
 - At most 2 critical comparator decisions
 - Optimize time needed for comparator
- Redundant SAR
 - Make SAR robust against DAC settling errors and comparator noise
- SAR DAC Calibration
 - DAC non-linearity
 - Digital overhead


EE 240C

Analog-Digital Interface Integrated

Circuits


Capacitors

DAC Capacitors: MIMCap

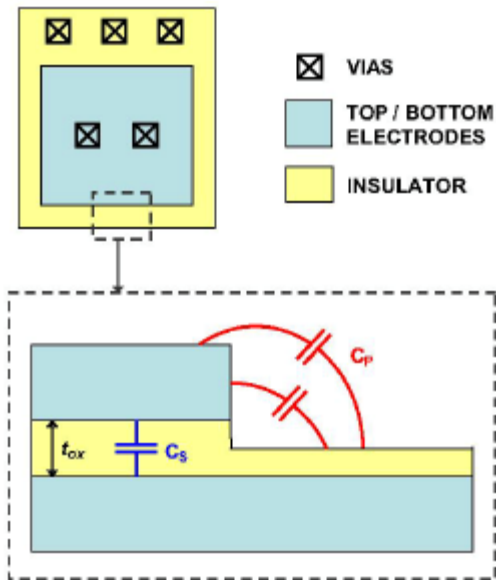

- Minimum capacitor value (10s of fF)
- Area overhead
- Routing parasitics (difficult to separate top and bottom plate)
→ grounded shield with one hole per unit capacitor for bottom-plate

DAC Capacitors: MOMCap

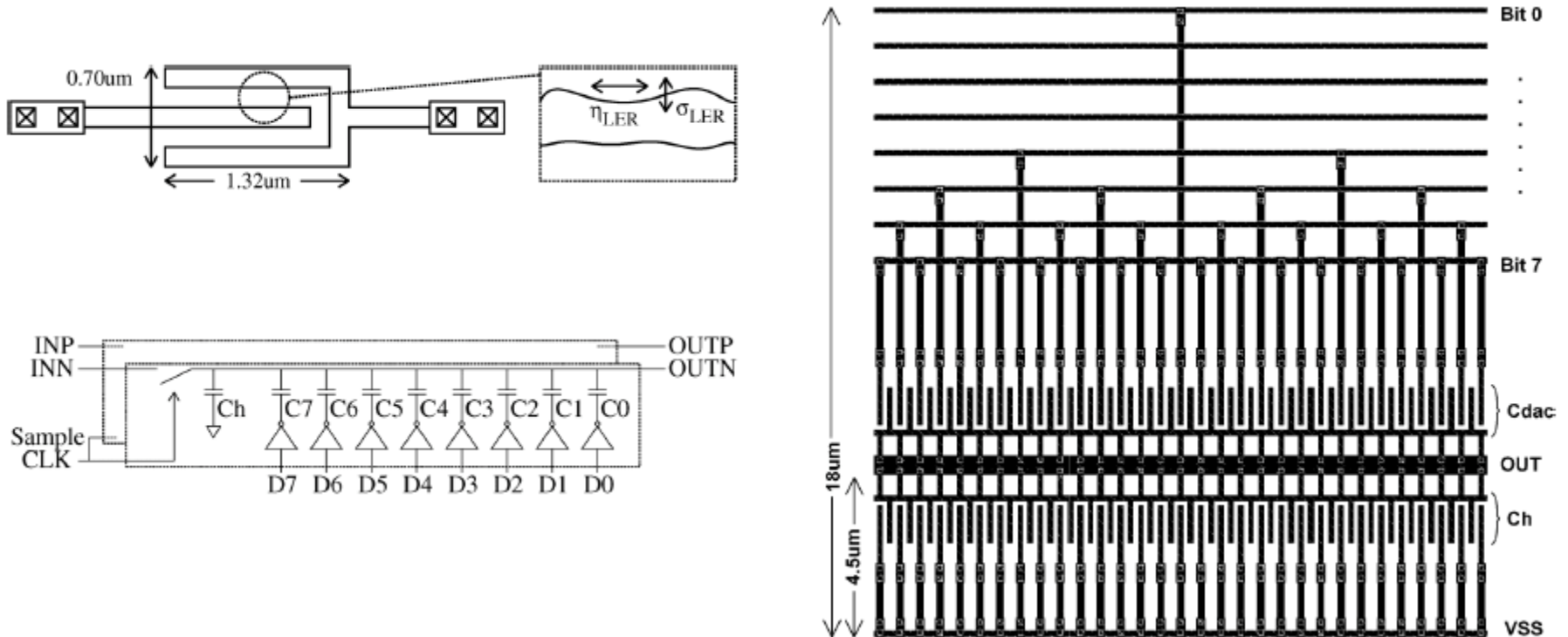

[P. J. A. Harpe et al., "A 26 w 8 bit 10 MS/s asynchronous SAR ADC for low energy radios," IEEE J. Solid-State Circuits, vol. 46, no. 7, pp. 1585–1595, Jul. 2011]


- Custom structure with low minimum capacitor size ($< 1\text{fF}$)
- Custom mismatch model (typ. 0.2 % for 0.25fF unit cap in 90nm)

EE 240C

Analog-Digital Interface Integrated Circuits


SAR ADC Capacitor and Switching Schemes

Conventional Switching Scheme

 

- Fully differential variants
- Unsuccessful bit trials lead to reference power loss
- Comparator input node swing


Conventional Switching Scheme

 

- Parasitic capacitor C_p only causes smaller comparator signal
 - Capacitive divider between switched capacitor and parasitic capacitor


Split Capacitor Array

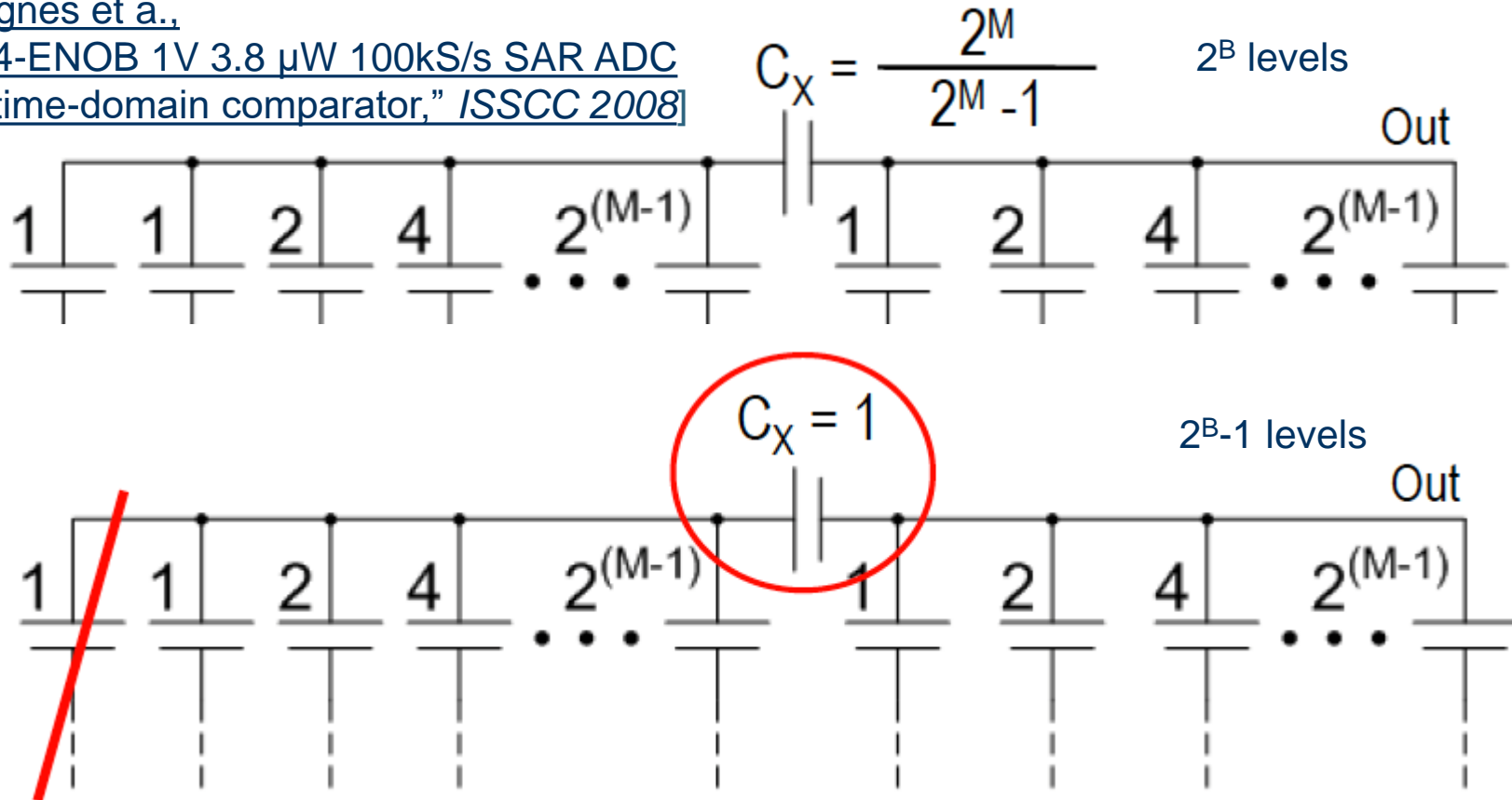[A. Agnes et al.,
“A 9.4-ENOB 1V 3.8 μ W 100kS/s SAR ADC
with time-domain comparator,” *ISSCC 2008*]



- Smaller number of unit elements, but needs calibration
 - Sensitive to parasitic capacitor on secondary summing node

Monotonic Switching Scheme

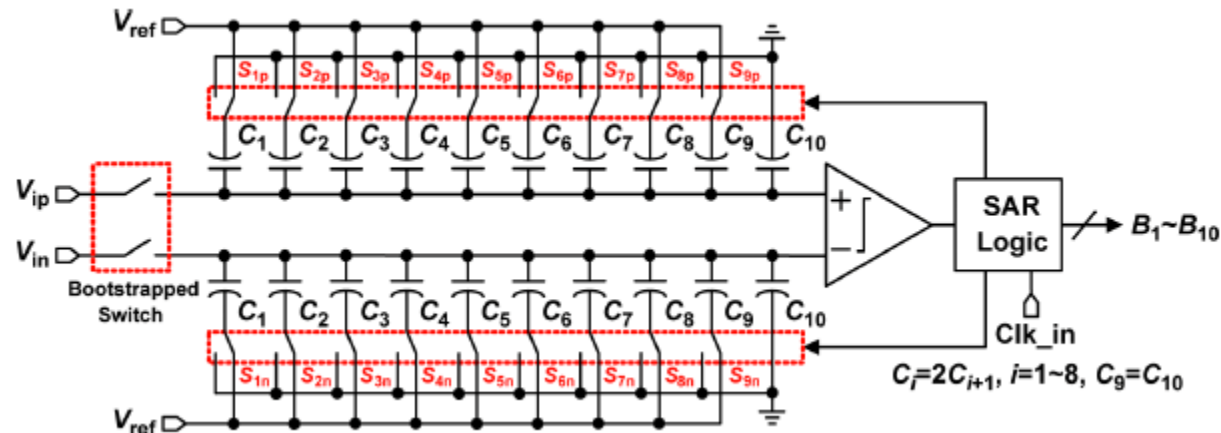


[C.-C. Liu et al., "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, vol. 45, no. 4, pp. 731–740, Apr. 2010]

- Top-plate sampling
- Compare before switching (B–1 single-ended switches for B bits)
- Parasitic capacitor C_p (not shown) leads to gain error
- Comparator common-mode


Monotonic Switching Scheme

- Conventional Switching Scheme

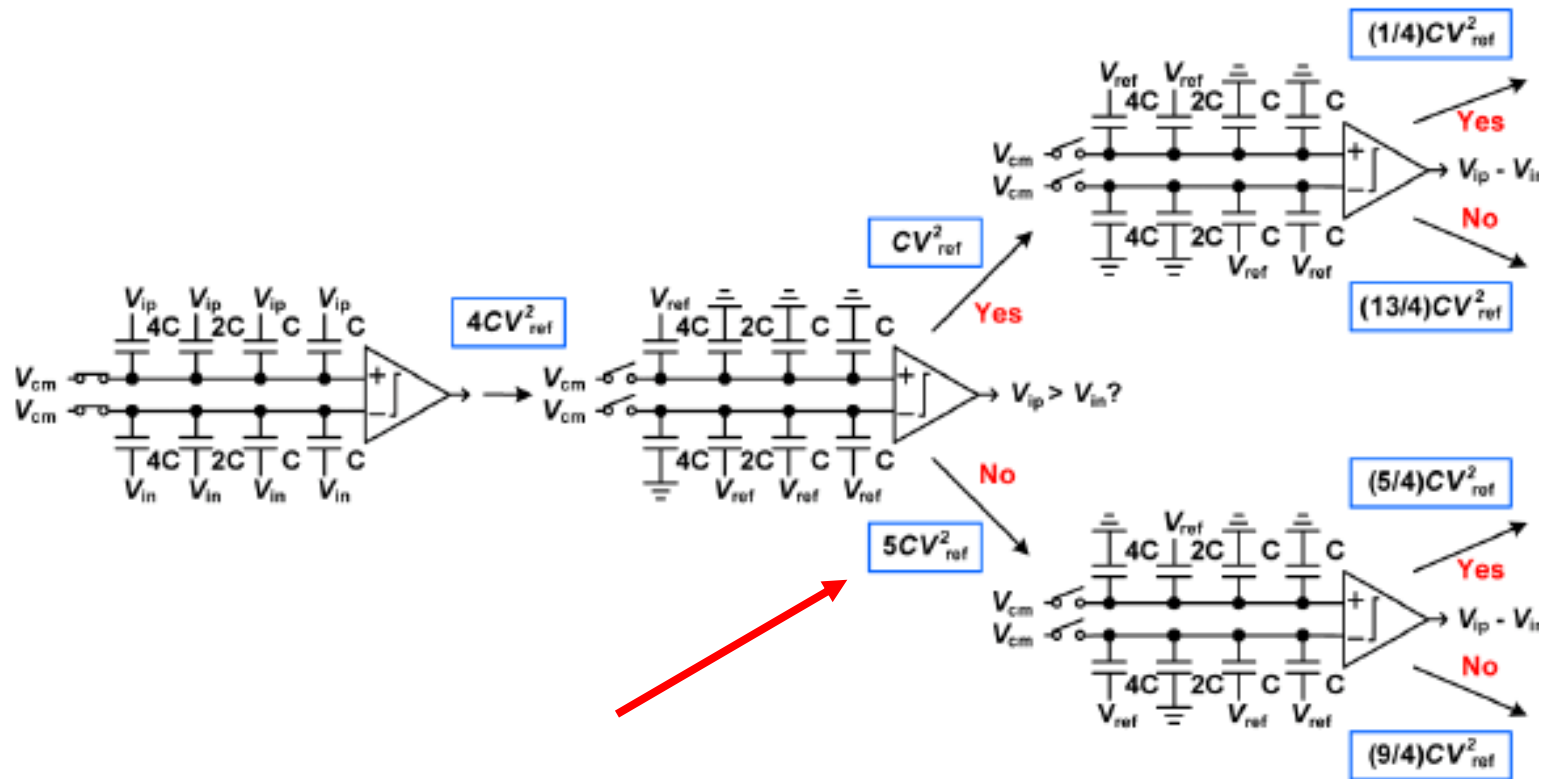

Monotonic Switching Scheme

- Monotonic Switching Scheme

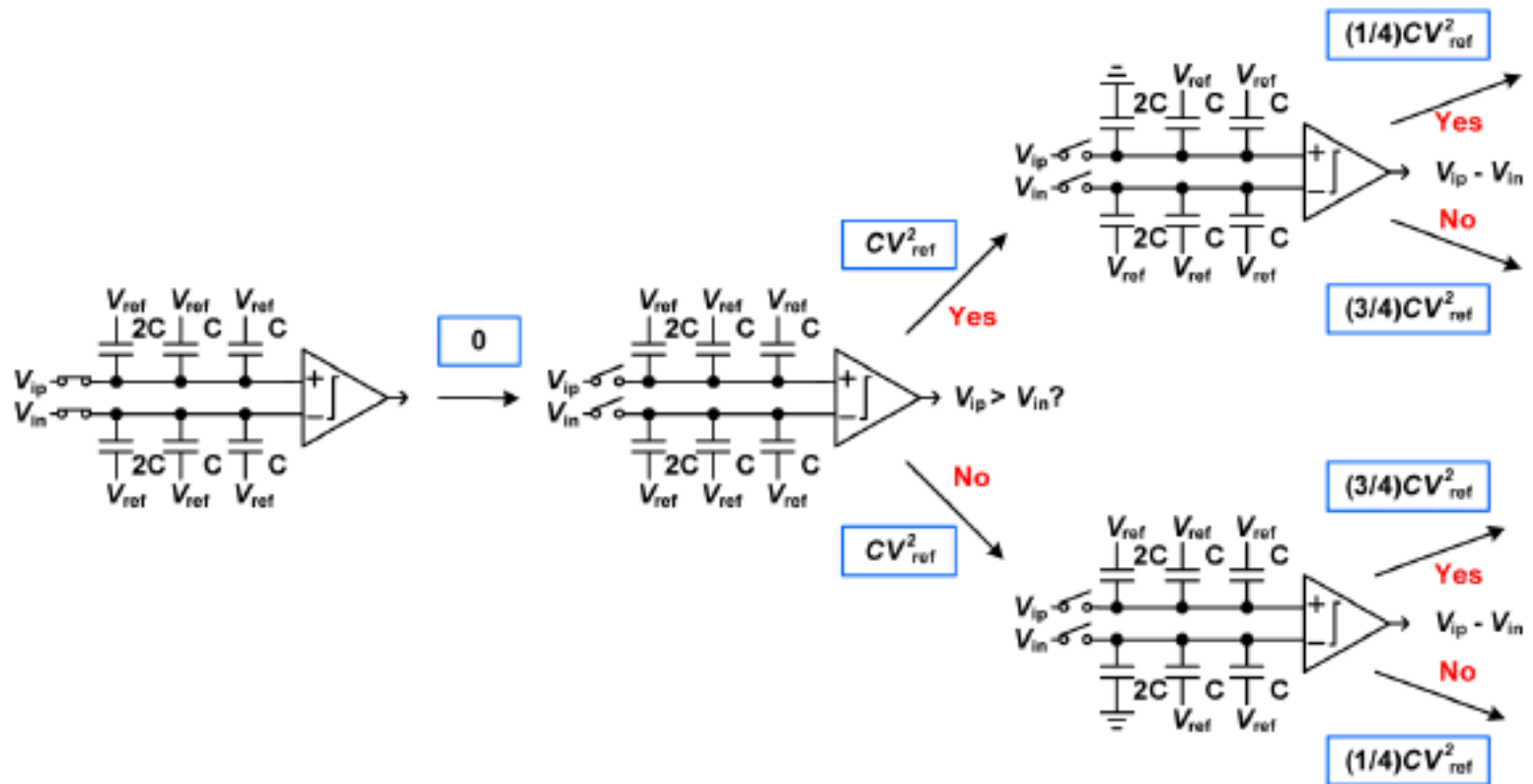

EE 240C

Analog-Digital Interface Integrated Circuits

Successive Approximation ADC

SAR Techniques



- Small custom unit capacitors for low- to mid-resolution SAR ADC
- DAC schemes and switching schemes for low power or lower area
- Self-timed comparator or asynchronous SAR
 - At most 2 critical comparator decisions
 - Optimize time needed for comparator
- Redundant SAR
 - Make SAR robust against DAC settling errors and comparator noise
- SAR DAC Calibration
 - DAC non-linearity
 - Digital overhead

EE 240C

Analog-Digital Interface Integrated Circuits

Asynchronous SAR ADC




Asynchronous SAR ADC

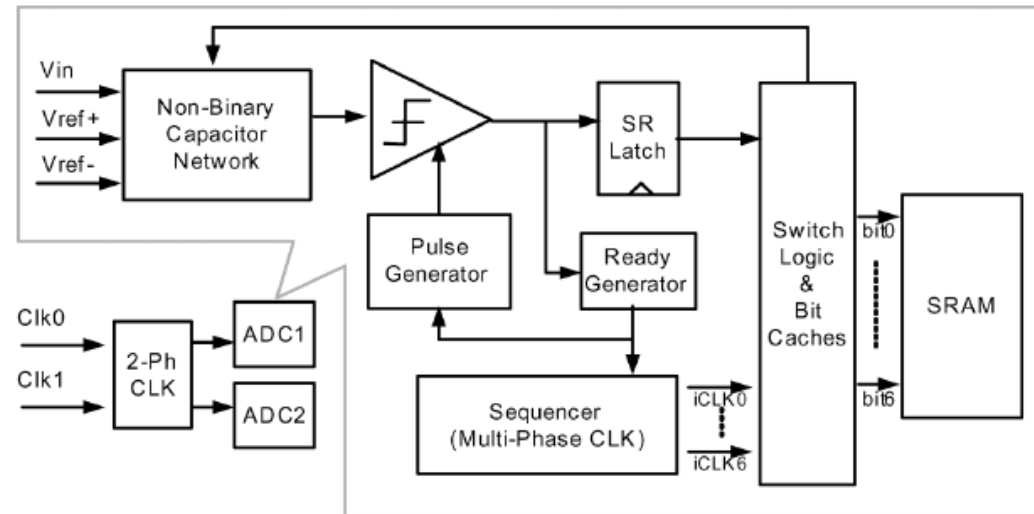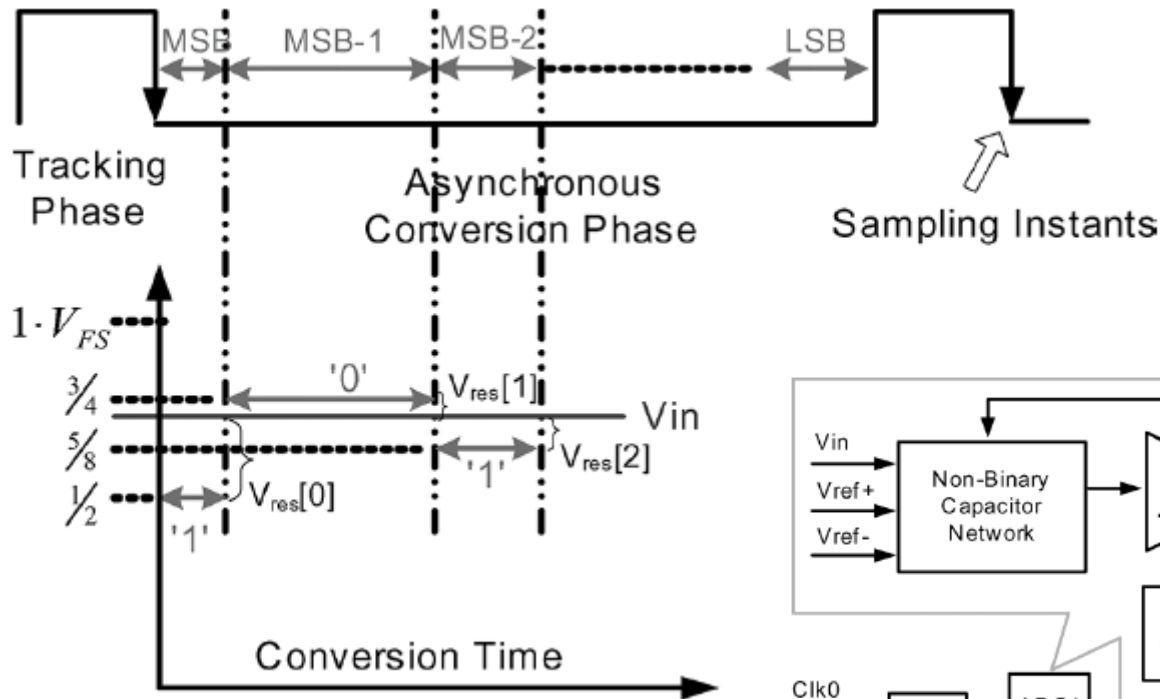

[S. W. M. Chen and R. W. Brodersen,
 "A 6-bit 600-MS/s 5.3-mW asynchronous ADC in 0.13- m CMOS,"
 IEEE J. Solid-State Circuits, vol. 41, no. 12, pp. 2669–2680, Dec. 2006]

Asynchronous SAR ADC: Metastability

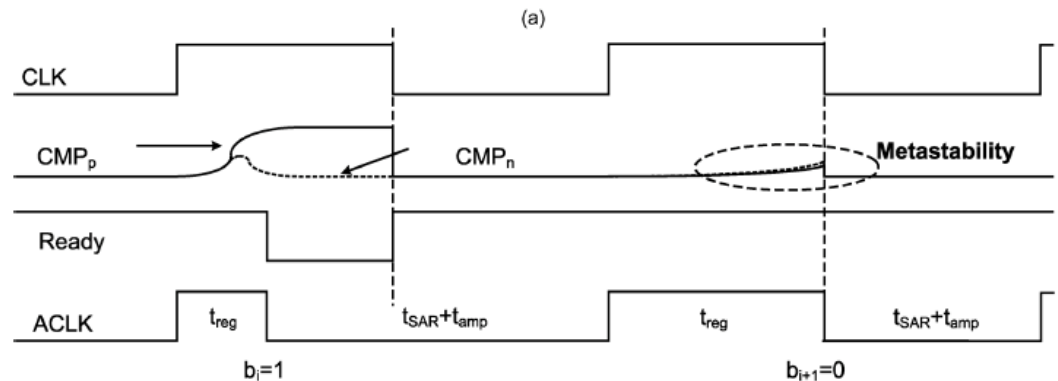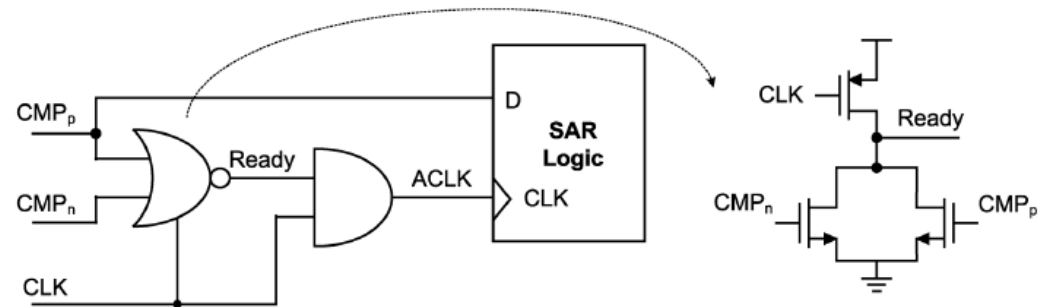 [S. W. M. Chen and R. W. Brodersen,
“A 6-bit 600-MS/s 5.3-mW asynchronous ADC in 0.13- m CMOS,”
IEEE J. Solid-State Circuits, vol. 41, no. 12, pp. 2669–2680, Dec. 2006]




[W. Liu, P. Huang, and Y. Chiu,
“A 12-bit, 45-MS/s, 3-mW redundant
Successive-Approximation-Register
Analog-to-Digital converter with
digital calibration,” IEEE J. Solid-State Circuits, vol. 46, no. 11, pp. 2661– 2672, Nov. 2011]

EE 240C


Analog-Digital Interface Integrated Circuits

SAR ADC Redundancy

Redundant Non-Binary DAC

 

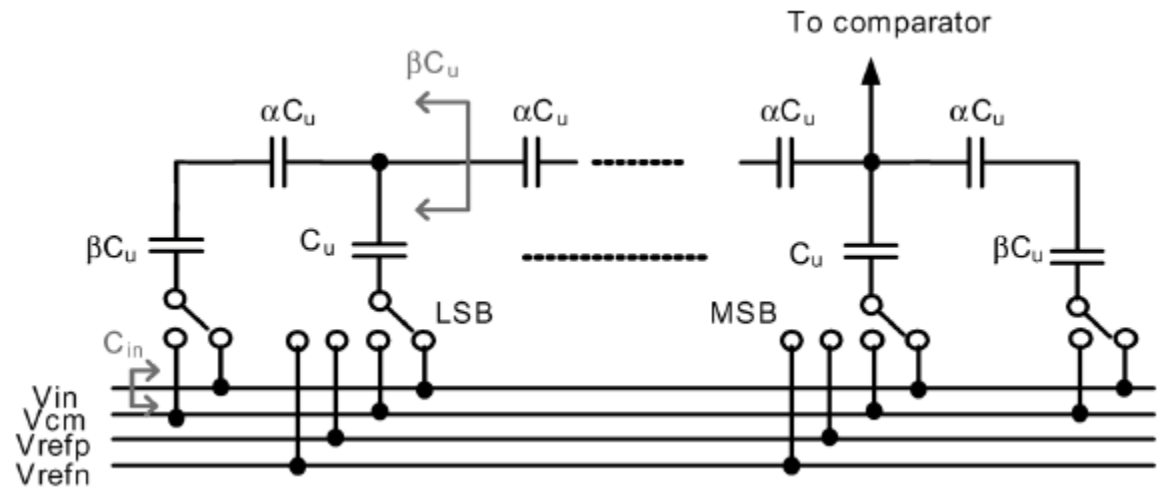
$$\begin{cases} \beta = 1 + \alpha \\ \text{Radix} = 1 + (\beta/\alpha) \end{cases}$$




- Non-binary DAC (with $1 < \text{Radix} < 2$) allows for recovery of erroneous comparator decisions, due to:
 - Incomplete DAC settling
 - Comparator noise

Non-binary Search

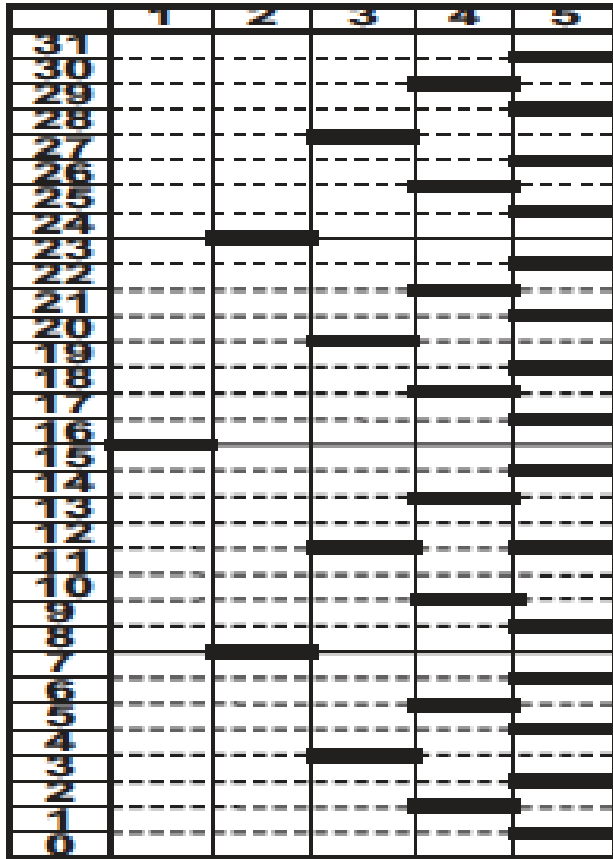[Ogowa, "SAR ADC Algorithm with Redundancy", 2008]




Binary Search (5b / 5 steps)

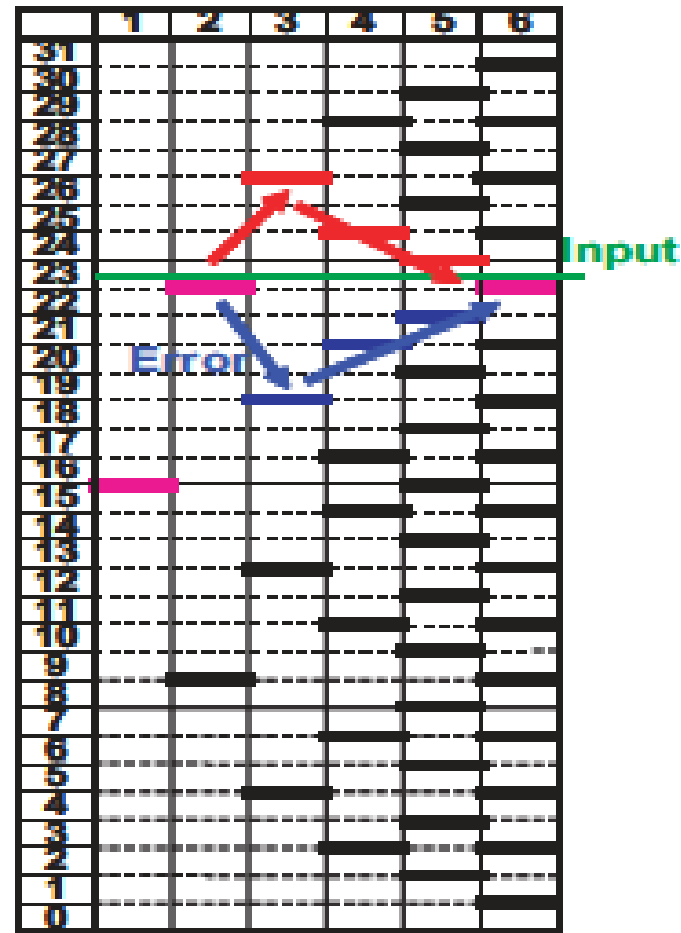


Non-Binary Search (5b / 6 steps)

Redundant Binary DAC

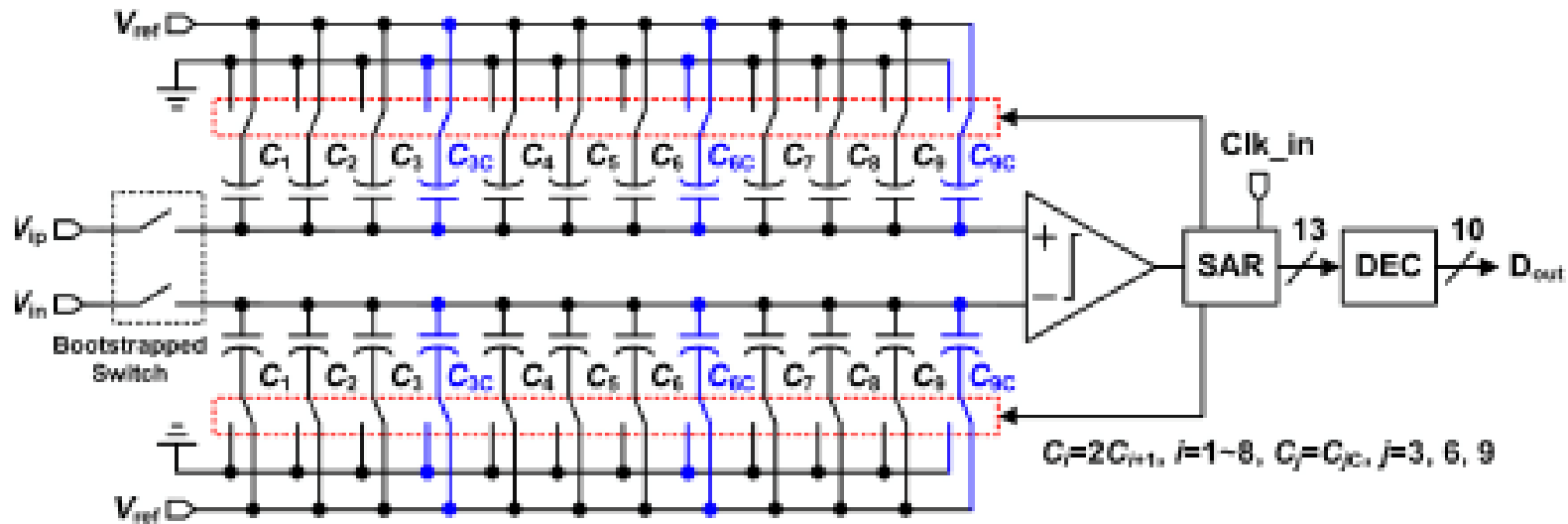

[C.-C. Liu et al., "A 10b 100ms/s 1.13mW SAR ADC with binary-scaled error compensation," in 2010 IEEE ISSCC, pp. 386–387]

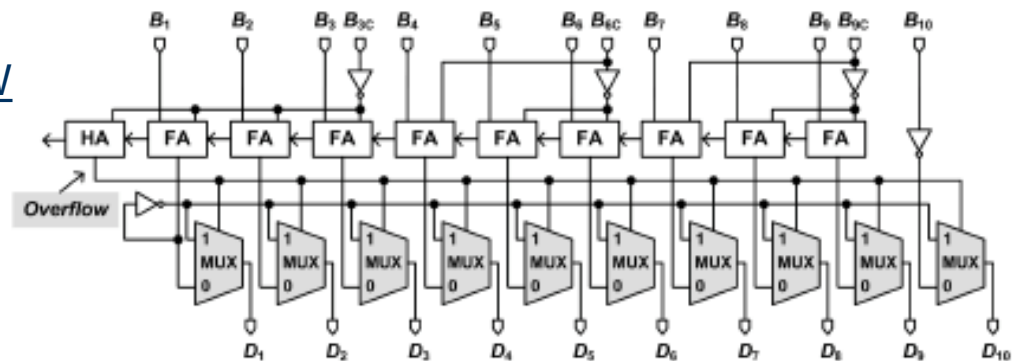

EE 240C


Analog-Digital Interface Integrated Circuits

SAR ADC DAC Calibration

Johan Vanderhaegen
University of California, Berkeley
jpv@eecs.berkeley.edu

Copyright © 2017
Bernhard Boser, Johan Vanderhaegen

DAC Calibration Scheme (5-bit Example)

 


- Voltage V_x after opening S_x and switching cap voltages for MSB:

$$V_{x1} = \frac{\Delta C}{C_{TOTAL}} V_{REF}$$

- Use calibration DAC to digitize residual and to correct

[H.-S. Lee, "Self calibration techniques for successive approximation analog- to-Digital converters, conversion" PhD thesis, University of California at Berkeley, 1984]

DAC Calibration Scheme

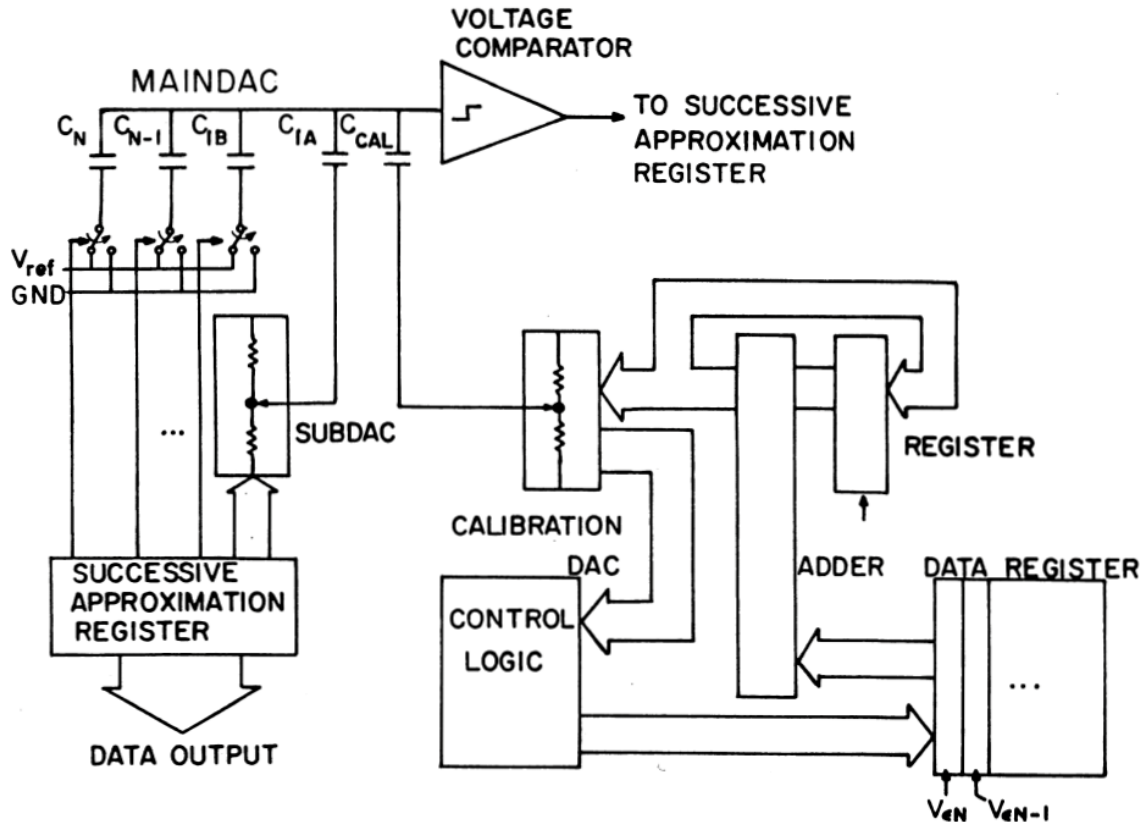

[H.-S. Lee, "Self-calibration techniques for successive approximation analog- to-Digital converters," PhD thesis, University of California at Berkeley, 1984]

- Digital overhead