

Midterm Exam

*Instructor: Johan Vanderhaegen (jpv@berkeley.edu)*Name: Solution

SID: _____

Score:

1	2	3	4	5	

- One (1) 8 ½" by 11" sheet of notes (no copies)
- Closed books
- Mark all results with a box around.
- Clearly cross out incorrect results.
- Write solutions on the exam sheets. Add extra pages where needed.
- Simplify algebraic results as much as possible.
- Bring into standard form where applicable.
- Show derivations.

1 TRUE/FALSE QUESTIONS (10 POINTS)

Problem 1. True/False Questions (10 points)

Answer with "T" for a true statement, and with "F" for a false statement; no explanation necessary. (correct: +1; incorrect: -1; unanswered: 0; minimum overall score: 0).

Question	T/F
a) The effective number of bits of an ADC is always an integer.	F
b) Increasing the number of samples used to create an FFT plot helps lower the spectrum's noise floor.	T
c) A thermometer encoded DAC typically exhibits its worst DNL at codes near the center of the transfer characteristic.	F
d) DNL measurements are not affected by noise, only INL measurements are.	F
e) An imbalance in the capacitive loading of a regenerative comparator can lead to input-referred offset.	T
f) Transient dynamic errors, such as sparkles, cannot be detected by a histogram test.	T
g) Bottom-plate sampling improves kT/C noise.	F
h) SNR can be lower than SNDR.	F
i) ADC gain and offset errors do not affect non-linearity measures such as INL and DNL.	T
j) A dynamic comparator does not introduce noise.	F

2 ADC SNR AND BW (10 POINTS)

Problem 2. ADC SNR and BW (10 points)

The dynamic range of an ADC is dominated by thermal noise from the sampler. Technical constraints limit the sampling capacitance to 1 pF.

1. Determine the minimum sampling rate f_s to achieve a SNR of 90 dB for sinusoidal inputs with frequency 0...1 MHz and **zero-to-peak** amplitude of 1 V. Note that the assumption is that the ADC is followed by an ideal digital low pass filter.
2. By what factor does the f_s have to increase to improve the SNR by 1 bit.

1. signal power $S = 1V^2/2$

noise power $N = \underbrace{\frac{kT}{C} \cdot \frac{2}{f_s}}_{\text{PSD after sampling}} \cdot 1 \text{ MHz}$

$$\frac{S}{N} = \frac{1V^2/2}{\frac{kT}{C} \cdot \frac{2}{f_s} \cdot 1 \text{ MHz}} \geq 10^9$$

$$\Rightarrow f_s \geq 1 \text{ MHz} \cdot \frac{kT}{C} \cdot \frac{4 \cdot 10^9}{1V^2} \approx 16.5 \text{ MHz}$$

2. 1 bit SNR improvement is 6dB

$\Rightarrow f_s$ has to increase by a factor
of 4

3 SAMPLING (10 POINTS)

Problem 3. Sampling (10 points)

What is the result of sampling $v(t)$ at sampling times kT , with $T = 1 \mu s$?

$$v(t) = 0.5 \sin(2\pi \cdot 217 \text{ kHz} \cdot t) + 0.5 \sin(2\pi \cdot 783 \text{ kHz} \cdot t)$$

$$= 0.5 \sin(2\pi \cdot 0.217 \cdot k)$$

$$+ 0.5 \sin(2\pi \cdot 0.783 \cdot k)$$

$$= 0.5 \sin(2\pi \cdot 0.217k)$$


$$+ 0.5 \sin(2\pi \cdot 0.783k - 2\pi \cdot k)$$

$$= 0.5 \sin(2\pi \cdot 0.217k)$$


$$+ 0.5 \sin(-2\pi \cdot 0.217k)$$

$$= 0$$

Frequency domain before sampling:

 

Frequency domain after sampling:

 

4 SAR ADC (10 POINTS)

Problem 4. SAR ADC (10 points)

Consider a single-ended SAR ADC switching scheme: the single-ended input is sampled on the top-plate of the capacitors and the bottom-plate of the capacitors is used for feedback, as shown in figure 1. The DAC is a binary-weighted capacitive DAC: $C_1 = 2C_0$, $C_2 = 2C_1$, The node OUT is connected to one of the inputs of a comparator.

 


Figure 1: SAR ADC DAC array

1. Using charge conservation, write the voltage on node OUT as a function of the input voltage during the sampling phase, the DAC feedback during the sampling, and the DAC feedback during the SAR algorithm phase. The DAC feedback D7-D0 can be represented as a single voltage V_{DAC} (which would need to be defined).
2. How does a parasitic capacitor C_p influence the input-output characteristic of this SAR ADC?

$$\begin{aligned}
 1. \quad & C_{DAC} (V_{IN} - V_{DAC}^0) + C_p V_{IN} \\
 &= C_{DAC} (V_{OUT} - V_{DAC}) + C_p V_{OUT} \\
 \Rightarrow \quad & V_{OUT} = V_{IN} + \frac{C_{DAC}}{C_{DAC} + C_p} (V_{DAC} - V_{DAC}^0)
 \end{aligned}$$

$$C_{DAC} = C_7 + C_6 + \dots + C_0 = 255 C_0$$

$$V_{DAC} = \frac{\sum C_k D_k V_{ref}}{\sum C_k}$$

$$= V_{ref} \sum_{k=0}^7 \frac{C_k}{C_{DAC}} D_k \quad \text{with } D_k \in \{0, 1\}$$

2. After convergence of the SAR algorithm:
 $V_{OUT} \approx V_{ref}^{comparator}$

$$\Rightarrow V_{IN} = - \frac{C_{DAC}}{C_{DAC} + C_p} (V_{DAC} - V_{DAC}^0) + V_{ref}^{comp}$$

$$V_{DAC} = V_{ref} \frac{\sum C_k D_k}{C_{DAC}}$$

$$= \frac{C_{DAC} + C_p}{C_{DAC}} (V_{IN} - V_{ref}^{comp}) - V_{DAC}^0$$

C_p leads to a gain error
 of C_p/C_{DAC}
 (and potentially an offset error
 depending on the choice
 of V_{DAC}^0 & $V_{ref}^{comparator}$)

5 REGENERATIVE LATCH (10 POINTS)

Problem 5. Regenerative latch (10 points)

1. A regenerative latch with two cross-coupled transistors each having a transconductance g_m and each having a capacitive load C_L has a regeneration time constant equal to C_L/g_m .

If the regenerative latch additionally has a coupling capacitor C_c between the two sides, as shown in figure 2, what is the regeneration time constant ?

 


Figure 2: Comparator

2. A regenerative comparator with a latch time-constant of 20 ps is used in a 6-bit flash converter. If the comparator pre-amplifier has a gain of 5, and $V_{FS} = V_{DD}$, what is the maximum ADC clock speed for a metastability error probability lower than 10^{-12} ?

5 REGENERATIVE LATCH (10 POINTS)

1. Differential equations:

$$\begin{cases} C_L \frac{dv_1}{dt} + C_c \frac{d(v_1 - v_2)}{dt} + g_m v_2 = 0 \\ C_L \frac{dv_2}{dt} + C_c \frac{d(v_2 - v_1)}{dt} + g_m v_1 = 0 \end{cases}$$

$$C_L \frac{d(v_1 - v_2)}{dt} + 2C_c \frac{d(v_1 - v_2)}{dt} - g_m (v_1 - v_2) = 0$$

$$\tau = \frac{C_L + 2C_c}{g_m} \quad (\text{this result can also be derived from the differential half-circuit by inspection})$$

$$2. \quad P_E = \frac{1}{A_v} \frac{\frac{V_{DD}}{2}}{\frac{1}{2} \frac{V_{FS}}{2^B}} e^{-T/2\tau}$$

$$\Rightarrow f_s \leq \frac{1}{2\tau} \frac{1}{\log \frac{1}{P_E} \frac{1}{A_v} \frac{V_{DD}}{\frac{1}{2} \frac{V_{FS}}{2^B}}}$$

$$= \frac{1}{40\text{ps}} \frac{1}{\log \frac{10^{12}}{5} 2^7}$$

$$\approx 810 \text{ MHz}$$