


EE 240C

Analog-Digital Interface Integrated Circuits


Oversampled ADCs

The Case for Oversampling

Nyquist sampling:


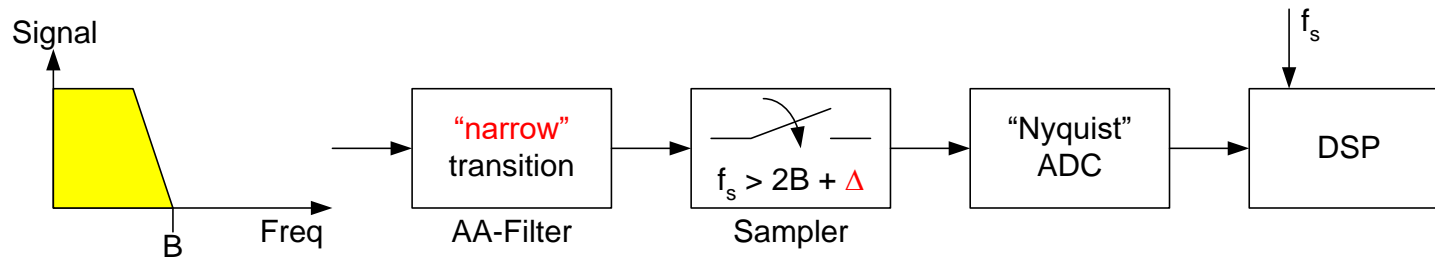


Oversampling:

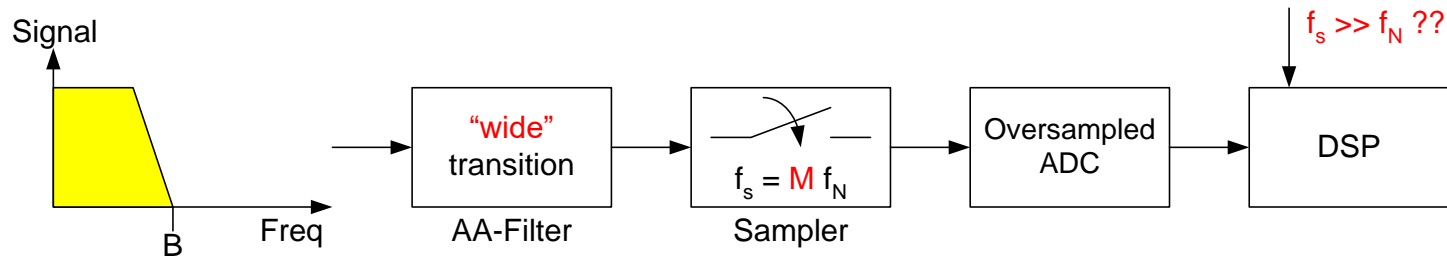


- Nyquist rate $f_N = 2B$
- Oversampling rate $M = f_s/f_N > 1$

Pulse-Count Modulation

  


Mean of pulse-count signal approximates analog input!

Pulse-Count Spectrum

 

- Signal: low frequencies, $f < B \ll f_s$
- Quantization error: high frequency, $B \dots f_s / 2$
- Separate with low-pass filter!

Oversampled ADC

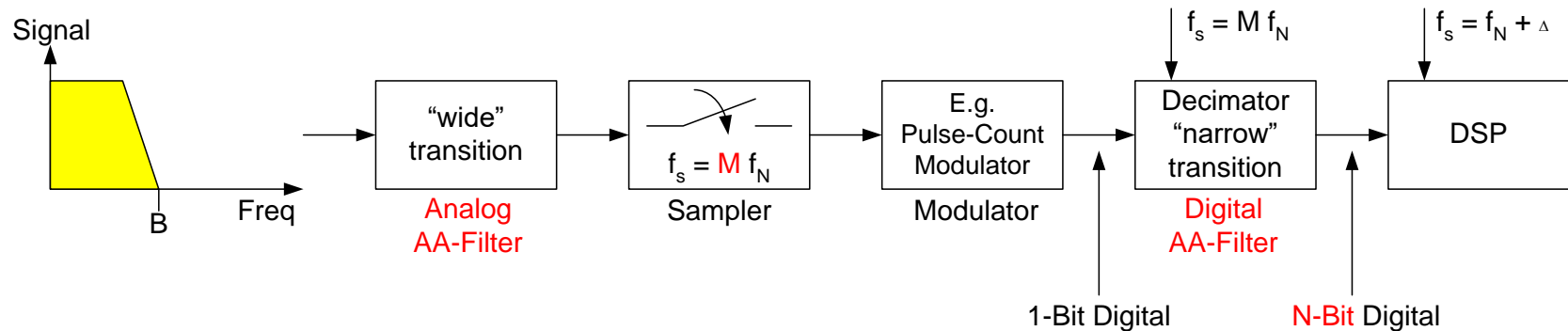

Decimator:

- Digital (low-pass) filter
- Removes quantization error for $f > B$
- Provides most anti-alias filtering
- Narrow transition band, high-order
- 1-Bit input, N-Bit output (essentially computes “average”)

EE 240C


Analog-Digital Interface Integrated Circuits

Modulator

Modulator


- Objectives:
 - Convert analog input to 1-Bit pulse density stream
 - Move quantization error to high frequencies $f \gg B$
 - Operates at high frequency $f_s \gg f_N$
 - $M = 4 \dots 256$ (typical)
 - Better be “simple”
- $\rightarrow \Sigma\Delta = \Delta\Sigma$ Modulator

1st Order $\Sigma\Delta$ Modulator

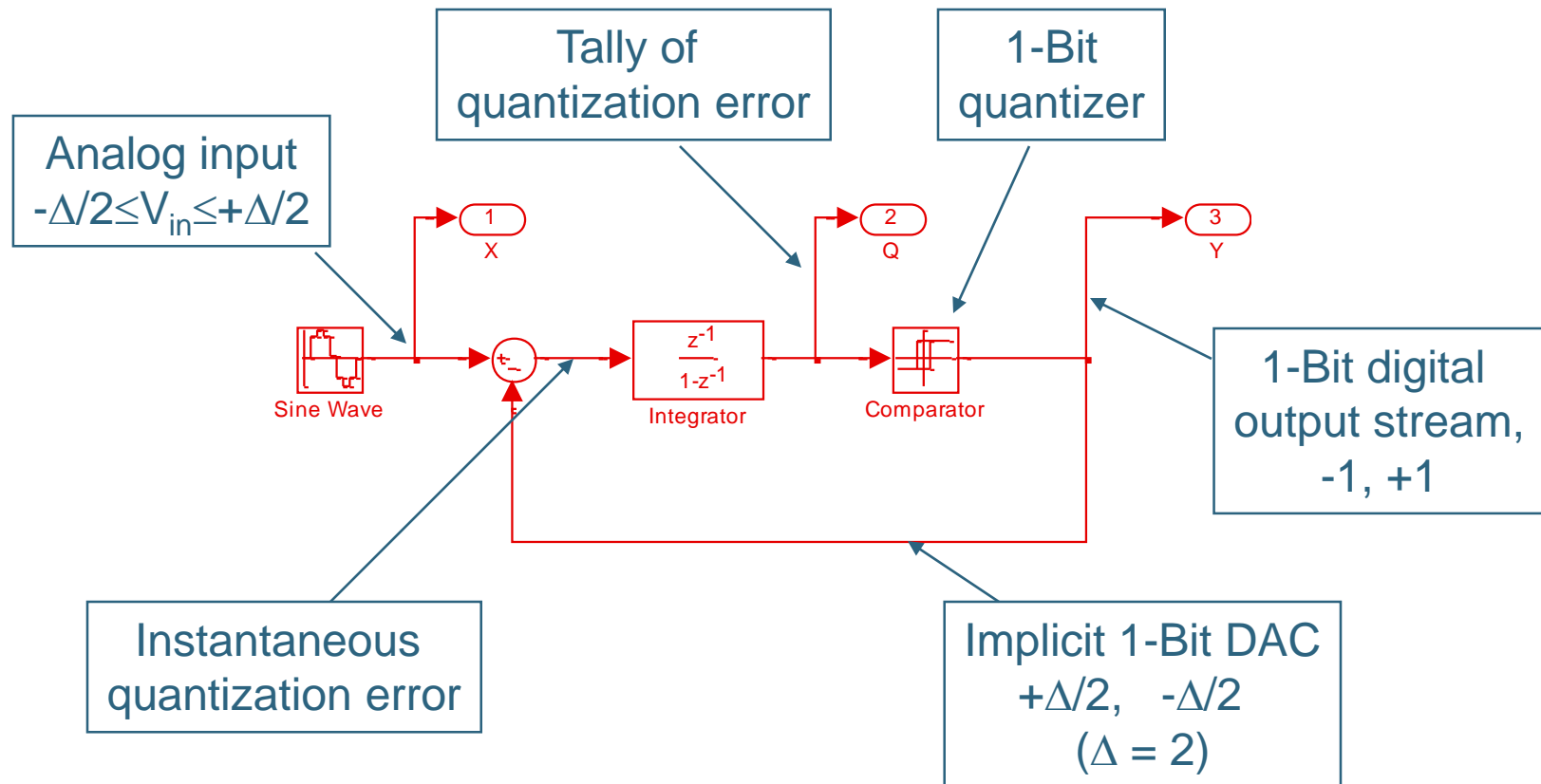

sigma_delta_L1.mdl

1st Order Modulator Signals

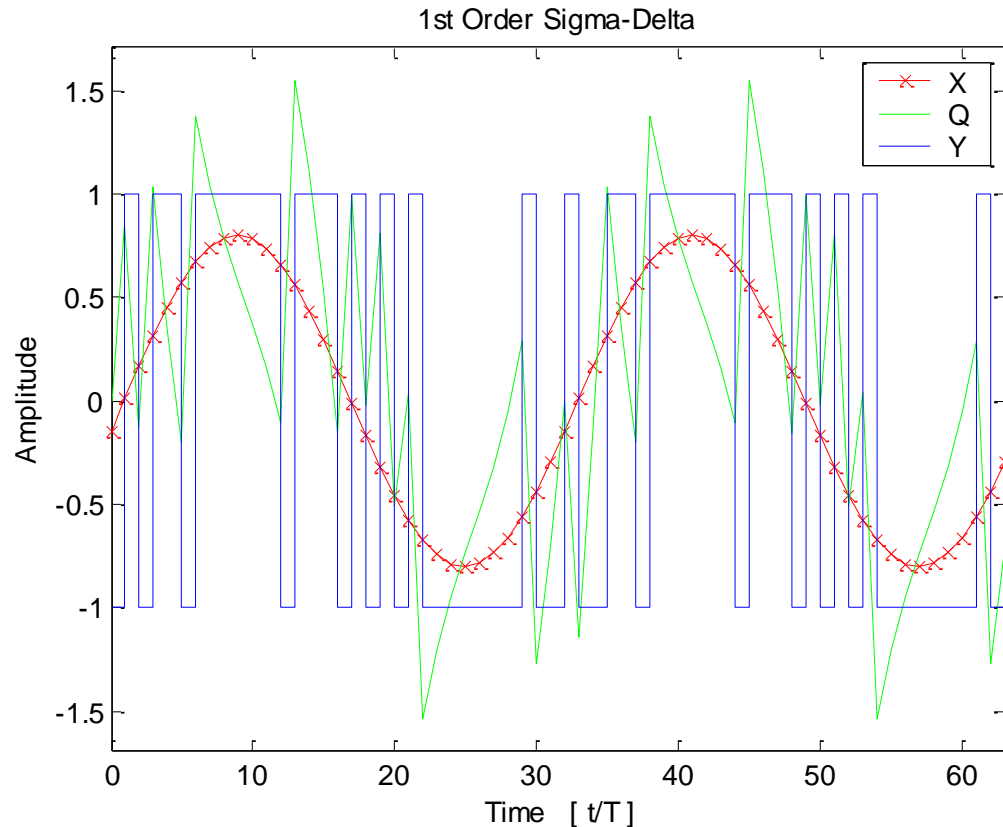

sigma_delta_L1.m

X analog input
Q tally of q-error
Y digital/DAC output


Mean of Y approximates X

$$T = 1/f_s = 1/(M f_N)$$

$\Sigma\Delta$ Modulator Characteristics

- Quantization error independent of component matching
 - Very high SQNR achievable (> 20 Bits!)
 - Inherently linear for 1-Bit DAC
 - Limited to “moderate” speed
(try to build a 10GS/s, 8-Bit oversampled ADC)
-
- What about the quantization noise spectrum?

Output Spectrum

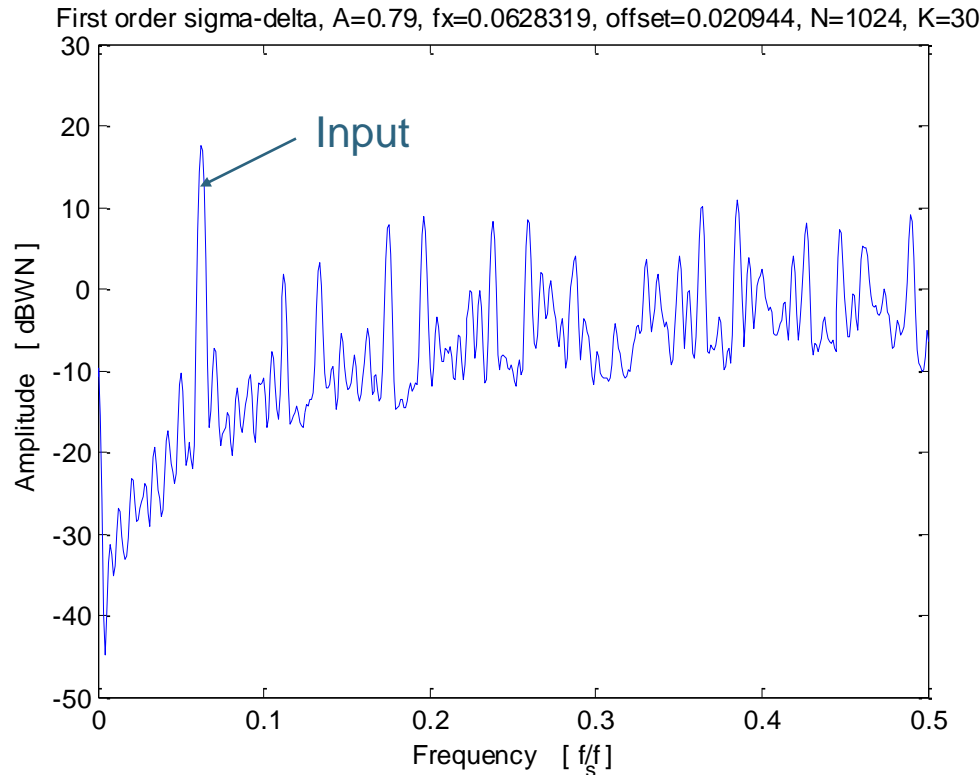

- Definitely not white!
- Skewed towards higher frequencies
- Tones
- dBWN (dB White Noise) scale sets the 0dB line at the noise per bin of a random -1, +1 sequence


sigma_delta_L1_sin.m

EE 240C

Analog-Digital Interface Integrated Circuits


Quantization Noise Analysis

Quantization Noise Analysis

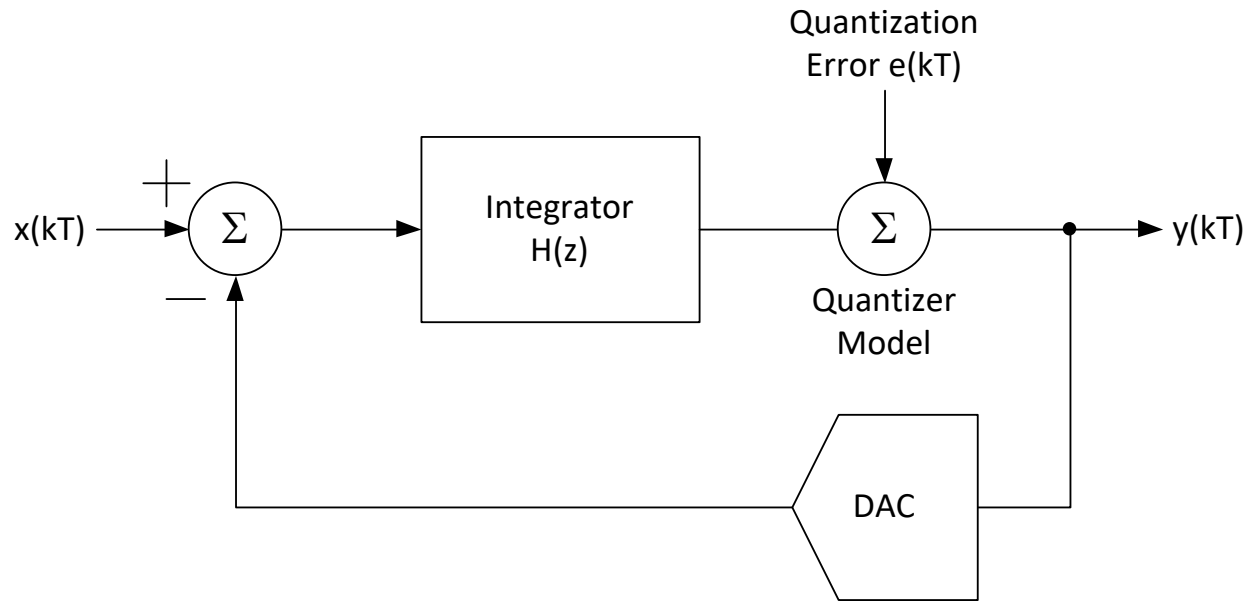

- Sigma-Delta modulators are nonlinear systems with memory
→ very difficult to analyze
- Representing the quantizer as an additive noise source linearizes the system

STF and NTF

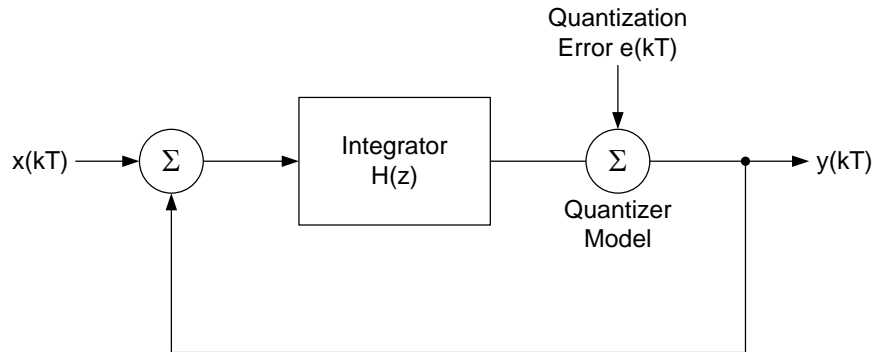

$$H(z) = \frac{z^{-1}}{1 - z^{-1}}$$

Signal transfer function:


$$\text{STF} = \frac{Y(z)}{X(z)} = \frac{H(z)}{1 + H(z)} = z^{-1} \Rightarrow \text{Delay}$$

Noise transfer function:

$$\text{NTF} = \frac{Y(z)}{E(z)} = \frac{1}{1 + H(z)} = 1 - z^{-1} \Rightarrow \text{Differentiator}$$

Noise Transfer Function, NTF

 First order sigma-delta, sin input, $A=0.79$, $f_x=0.0628319$, offset=0.020944, $N=1024$, $K=3$



sigma_delta_L1_ntf.m

Quantizer Error

- For quantizer with many bits

$$\overline{e^2(kT)} = \frac{\Delta^2}{12}$$

- Let's use the same expression for the 1-Bit case
- And assume the spectrum of the quantization error is white
- Simulation will tell if the result is useful

Experience: often sufficiently accurate to be useful,
with enough exceptions to be careful

In-Band Quantization Noise

$$H(z) = \frac{z^{-1}}{1 - z^{-1}}$$

$$G = 1$$

$$NTF(z) = 1 - z^{-1}$$

$$|NTF(z)|^2 = NTF(z)NTF(z^{-1})$$

$$= (1 - z^{-1})(1 - z)$$

$$= 1 - z^{-1} - z + 1$$

$$= 2 - 2\cos\omega T$$

$$= (2\sin\pi fT)^2$$

$$\approx (2\pi fT)^2 \quad \text{for } M \gg 1$$

$$\overline{S_Y} = \int_{-B}^B S_Q(f) |NTF(z)|_{z=e^{2\pi jfT}}^2 df$$

$$\cong \int_{-f_s/2M}^{f_s/2M} \frac{1}{f_s} \frac{\Delta^2}{12} (2\sin\pi fT)^2 df$$

$$\approx \frac{\pi^2}{3} \frac{1}{M^3} \frac{\Delta^2}{12}$$

Dynamic Range (Quantization Error)

$$DR = \frac{\text{peak signal power}}{\text{peak noise power}} = \frac{\overline{S_X}}{\overline{S_Y}}$$

$$\overline{S_X} = \frac{1}{2} \left(\frac{\Delta}{2} \right)^2$$


sinusoidal input, $STF = 1$

$$\overline{S_Y} = \frac{\pi^2}{3} \frac{1}{M^3} \frac{\Delta^2}{12}$$

M	DR
16	33 dB
32	42 dB
1024	87 dB

$$DR = \frac{9}{2\pi^2} M^3$$

Integrated Noise

 


sigma_delta_L1_total_noise.m

The signal+noise at the modulator output sums to 1 (0dB)

→ This is consistent with a binary ± 1 signal

[Eric Swanson]

SQNR

 

Remarkably good agreement between simulation and analysis, despite violated assumptions about ADC quantization error.

Detail: actually simulation is 3dB short of analysis, since dBFS scale assumes full-scale DC input, not sinusoid

Matlab Source Code

```
K = 30; % number of averaged simulations
N = 2^10; % number of output samples
fs = 1; % sampling frequency
fx = pi/53; % signal freq
A = 0.79; % signal amplitude (full-scale=1)
offset = pi/150; % signal offset

Y = zeros(N, K); % result vector
for i=1:K % average K results
    [t,x,y] = sim('sigma_delta_L1_sim', T*(N-1));
    Y(:, i) = y(:, 3);
end

[f, p, pint, pintfx] = avg_spectrum(Y, fx/fs);

plot(f, 10*log10(p), f, 10*log10(pintfx));
```

EE 240C


Analog-Digital Interface Integrated Circuits

Quantization Noise Characteristics

Oversampling and Noise Shaping

- $\Sigma\Delta$ modulators have interesting characteristics
 - Unity gain for the the input signal V_{IN}
 - Large attenuation of quantization noise injected at q
 - Much better than 1-Bit noise performance is possible if we're only interested in frequencies $\ll f_s$
- Oversampling ($M = f_s/f_N > 1$) improves SQNR considerably
 - 1st-Order SD: DR increases 9dB for each doubling of M or 30 dB per decade
 - L^{th} -Order SD: DR increases $(3 + 6L)$ dB for each doubling of M or $(10 + 20L)$ dB per decade
 - SQNR independent of circuit complexity and accuracy
- Analysis assumes that the quantizer noise is “white”
 - Not true in practice, especially for low-order modulators
 - Practical modulators suffer from other noise sources also (e.g. thermal noise)


DC Input

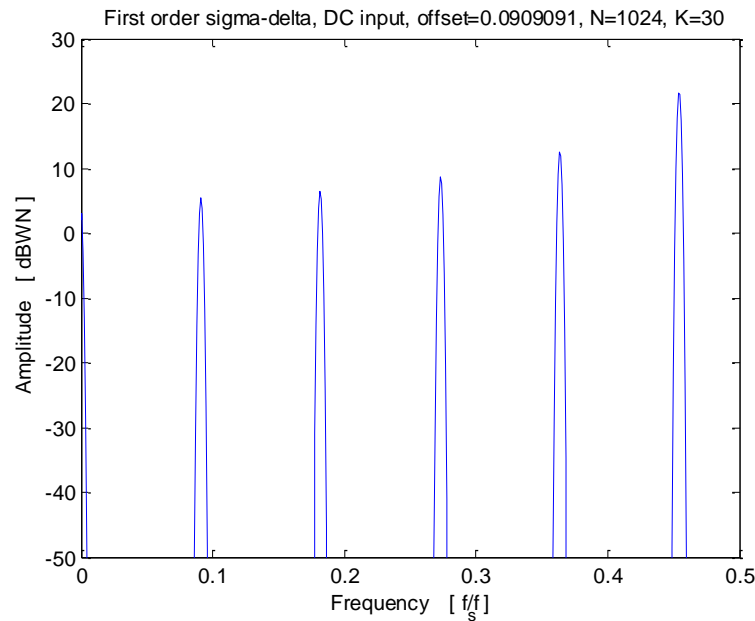

sigma_delta_L1_sin.m

- DC input $A = 1/11$
- Doesn't look like spectrum of DC at all
- The ADC “sings” ???
- → Quantization “noise” is periodic

Limit Cycle

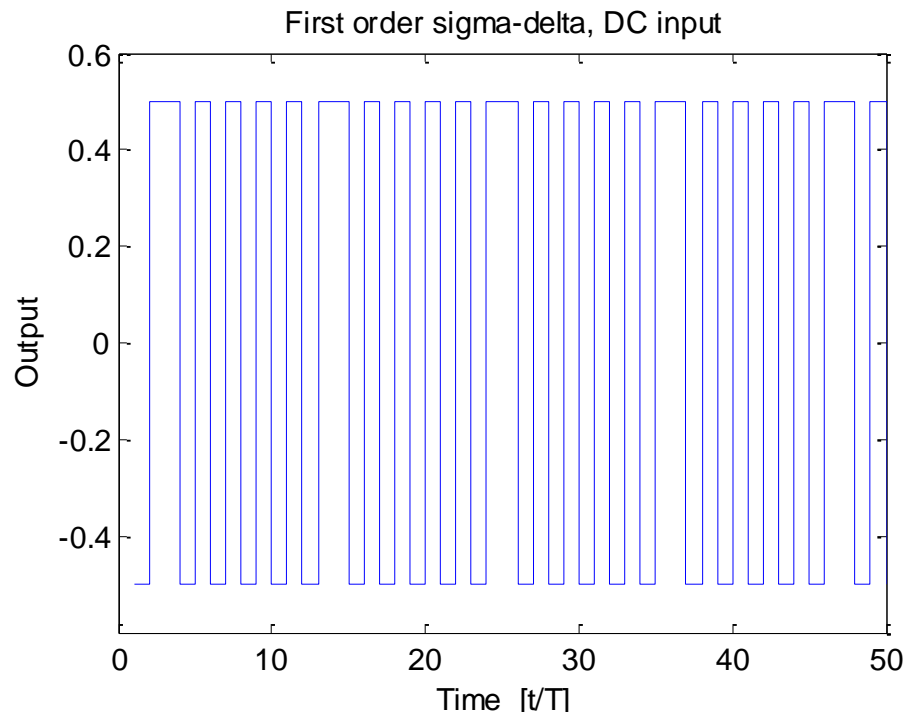

`sigma_delta_L1_dc.m`

DC input 1/11 →
Periodic sequence:

1	+1
2	+1
3	-1
4	+1
5	-1
6	+1
7	-1
8	+1
9	-1
10	+1
11	-1

Summary

- Oversampled ADCs decouple SQNR from circuit complexity and accuracy
- If a 1-Bit DAC is used, the converter is inherently linear— independent of component matching
- Higher order loop filters consisting of several integrators provide much better noise shaping than 1st order realizations and are less prone to limit cycles
- References
 - S. Pavan, R. Schreier, G. C. Temes, *Understanding Sigma Delta Converters*, IEEE Press, 2017
 - J. C. Candy and G. C. Temes, “Oversampling Methods for A/D and D/A Conversion”, Oversampling Delta-Sigma Data Converters: Theory, Design, and Simulation, 1992, pp. 1–25.
 - S. R. Norsworthy, R. Schreier, and G. C. Temes, “Delta-Sigma Data Converters, Theory, Design, and Simulation,” IEEE Press, 1997.
 - + many others (see course website)

EE 240C

Analog-Digital Interface Integrated Circuits

5th Order Modulator (Example)

Overview

- Building and evaluating behavioral models
 - Focus on functionality first
 - Add nonidealities later
 - Beware: changes get more expensive later in the process ...
- A 5th-order, 1-Bit $\Sigma\Delta$ modulator example
 - Noise shaping
 - Complex loop filters
 - Stability
 - Voltage scaling

SD Modulator Filter Design

- Procedure
 - Establish requirements
 - Design noise-transfer function, NTF
 - Determine loop-filter, H
 - Synthesize filter
 - Evaluate performance, stability
- References:
 - R. W. Adams and R. Schreier, “Stability Theory for DS Modulators,” in *Delta-Sigma Data Converters*, S. Norsworthy et al. (eds), IEEE Press, 1997, pp. 141–164.
 - S. Pavan, R. Schreier, and G. C. Temes, Understanding Delta-Sigma Data Converters. Wiley-IEEE Press, 2017. Chapter 4.

Modulator Specification

- Example: Audio ADC
 - Dynamic range DR 16 Bits
 - Signal bandwidth B 20 kHz
 - Nyquist frequency fN 44.1 kHz
 - Modulator order L 5
 - Oversampling ratio $M = f_s/f_N$ 64
 - Sampling frequency f_s 2.822 MHz
- The order L and oversampling ratio M are chosen based on
 - SQNR > 120dB (20dB below thermal noise)
 - Experience (e.g. Figure 4.14 in Adams & Schreier or Figure 4.18, 4.19, 4.20 in Understand Delta-Sigma Data Converters)

Modulator Specification

- SQNR

- Modulator Order (N in graphs below)
- Oversampling Ratio (OSR)
- Number of levels / bits in quantizer

[S. Pavan, R. Schreier, and G. C. Temes, *Understanding Delta-Sigma Data Converters*. Wiley-IEEE Press, 2017. Chapter 4.]

 


Figure 4.18 Empirical SQNR limit for 1-bit modulators of order N .


 


Figure 4.20 Empirical SQNR limit for modulators with 3-bit quantizers of order N .

Modulator Block Diagram

 

$$\text{STF} = \frac{Y(z)}{X(z)} = \frac{H(z)}{1 + H(z)}$$

$$\text{NTF} = \frac{Y(z)}{E(z)} = \frac{1}{1 + H(z)}$$

Approach:

Design NTF and solve for $H(z)$

Noise Transfer Function, NTF(z)


```
% stop-band attenuation Rstop ...  
% reduce if design is not stable
```

```
Rstop = 80;  
[b,a] = cheby2(L, Rstop, 1/M, 'high');
```

```
% normalize (for causality)  
b = b/b(1);  
NTF = filt(b, a, 1/fs);
```

```
% check stability (mag < 1.5)  
[mag] = bode(NTF, pi*fs)
```
 
```
>> mag = 1.32  
sigma_delta_L5_design.m
```



Loop-Filter, $H(z)$


```
H = inv(NTF) - filt(1, 1, 1/fs);
```

```
% check causality ... y(1) should be 0
```


```
y = impulse(H);
```

```
y = y(1)
```

```
>> y = 0
```

 

5th Order Loop Filter

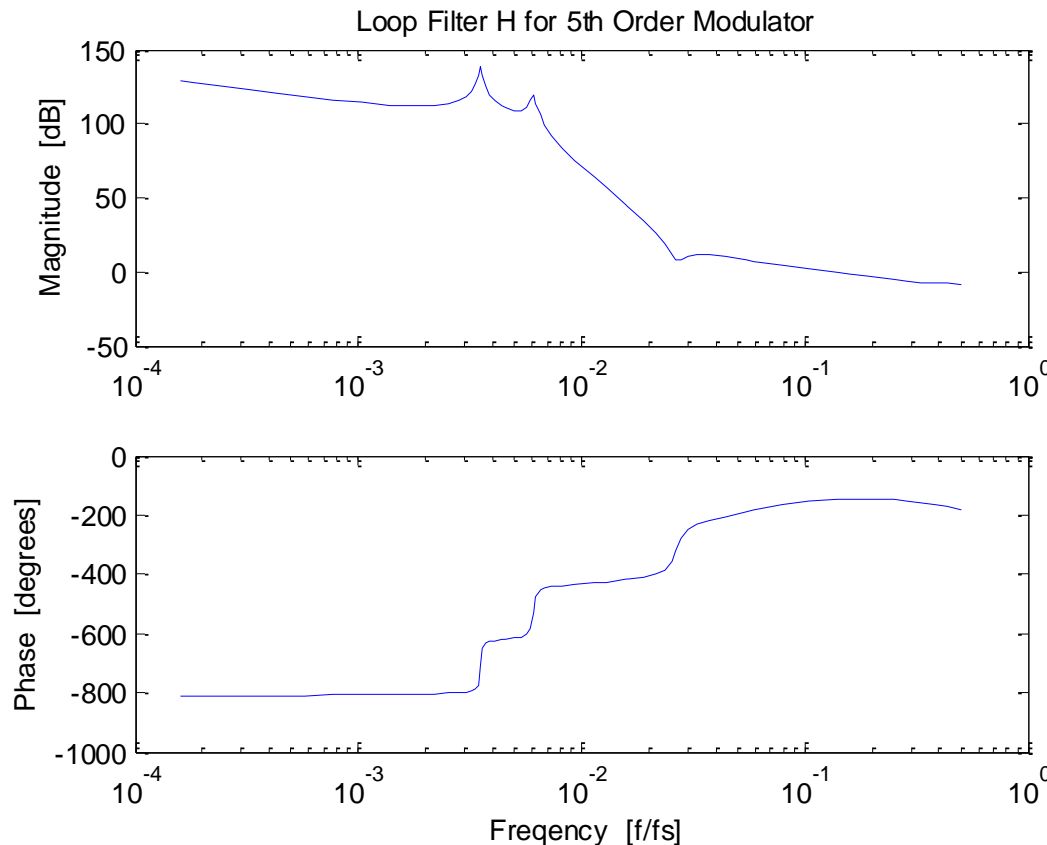

sigma_delta_L5_H.m

- Lot's of gain in the pass-band
- Remember that $\text{NTF} \sim 1/H$
- $H \sim 0\text{dB}$ in stop-band gives quantization noise a place to show up

Modulator Topologies

- CIFB: Cascade of Integrators with Feedback
 - State at the output of the integrators
→ larger unscaled signals at output of integrators
 - Multiple DACs


 


Figure 4.21 A third-order NTF realized as a cascade of integrators with feedback (CIFB) structure. All NTF zeros are at $z = 1$.

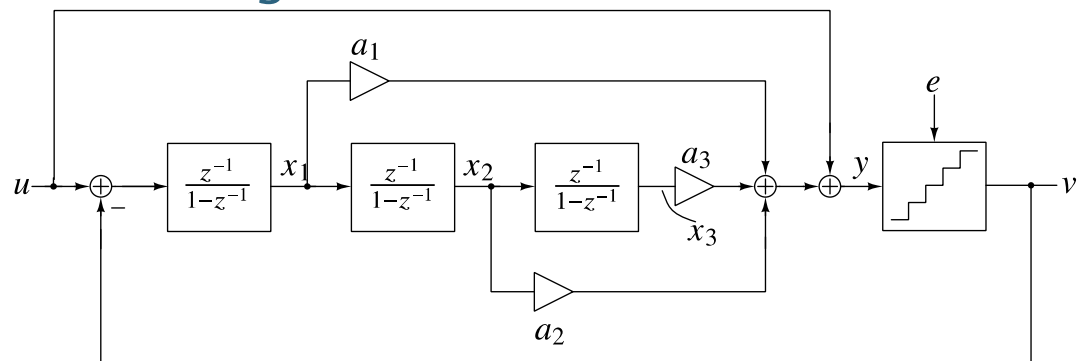
- CIFF: Cascade of Integrators with Feed-forward
 - Only quantization noise in integrators



[S. Pavan, R. Schreier, and G. C. Temes,
Understanding Delta-Sigma Data Converters.
Wiley-IEEE Press, 2017. Chapter 4.]

Figure 4.29 A low distortion CIFF structure, accomplished using input feedforward.

Modulator Topology

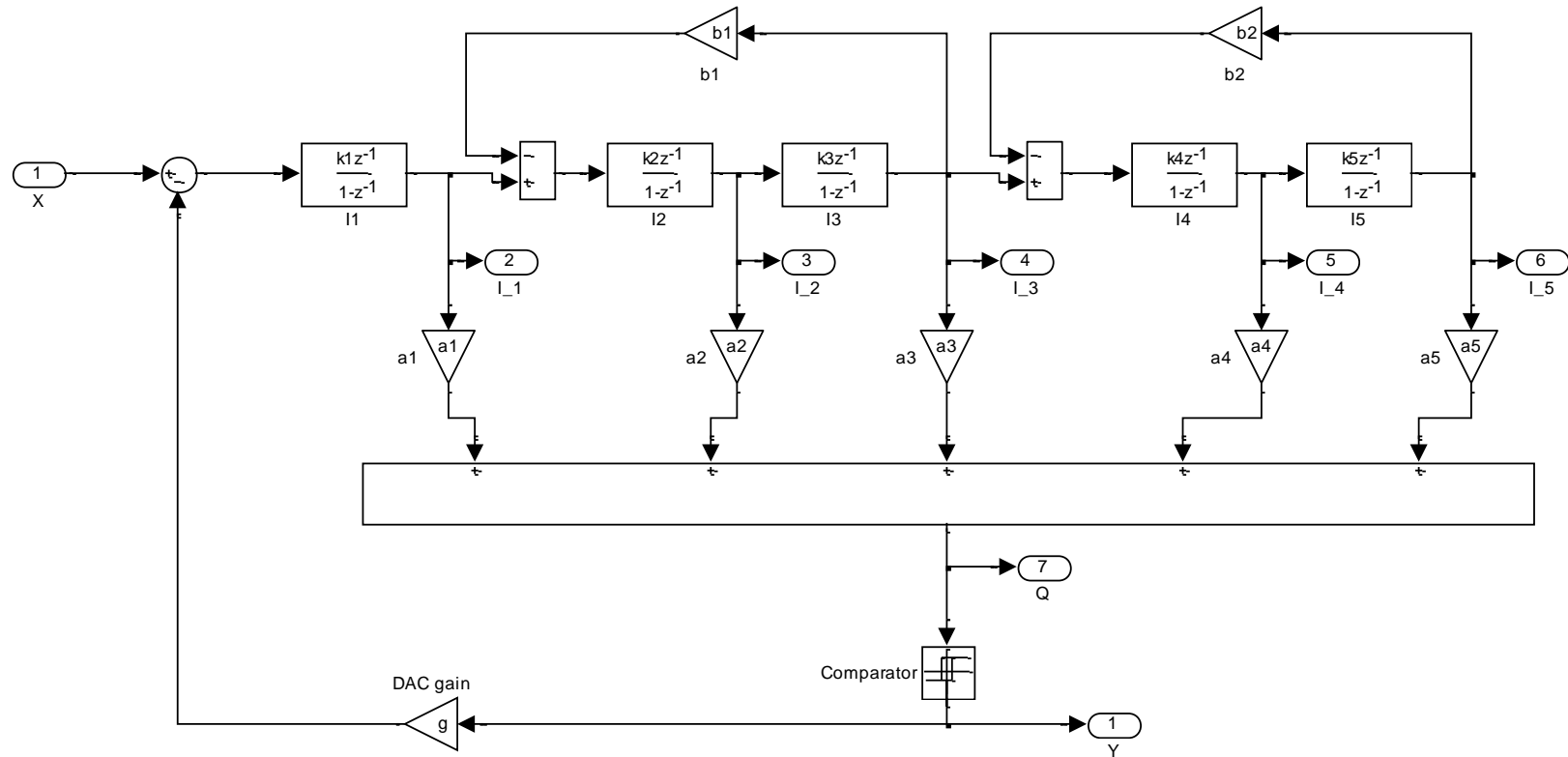

sigma_delta_L5_sim.mdl

Rounded Filter Coefficients

$$a_1=1;$$

$$a_2=1/2;$$

$$a_3=1/4;$$

$$a_4=1/8;$$

$$a_5=1/8;$$

$$k_1=1;$$

$$k_2=1;$$

$$k_3=1/2;$$

$$k_4=1/4;$$

$$k_5=1/8;$$

$$b_1=1/1024;$$

$$b_2=1/16-1/64;$$

$$g = 1;$$


Ref: Nav Souch, Don Kerth, Eric Swanson, and Tetsuro Sugimoto, "Phase Equalization System for a Digital-to-Analog Converter Using Separate Digital and Analog Sections", U.S. Patent 5061925, 1990, figure 3 and table 1.

EE 240C

Analog-Digital Interface Integrated Circuits

Noise Shaping


5th Order Noise Shaping

 

- Mostly quantization noise, except at low frequencies
- Let's zoom ...


sigma_delta_L5.m

5th Order Noise Shaping

 

sigma_delta_L5.m


5th Order Noise Shaping

 


sigma_delta_L5.m

- SQNR > 120dB
- Sigma-delta modulators are usually designed for negligible quantization noise
- Other error sources dominate, e.g. thermal noise

In-Band Noise Shaping

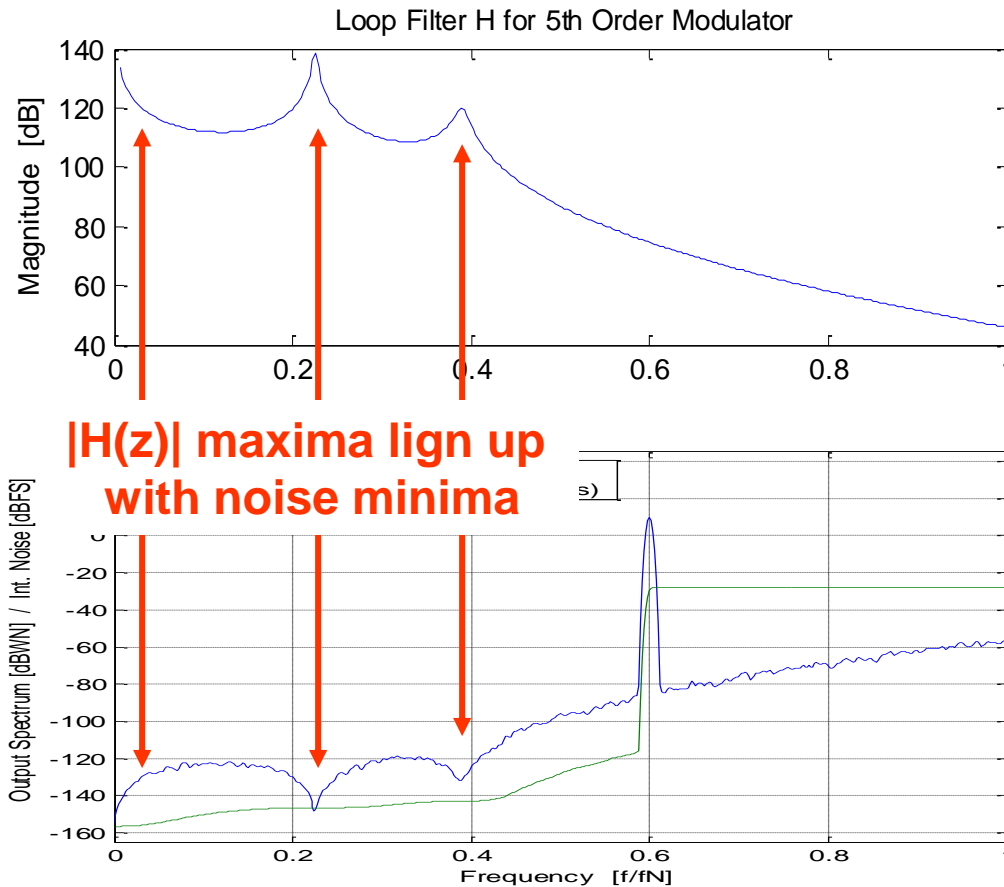

In-Band Noise Shaping

 

- Positive phase jumps indicates poles of $H(z)$ slightly outside unit circle
- Is the modulator stable?
- Let's analyze ...


EE 240C

Analog-Digital Interface Integrated

Circuits

Stability and Voltage Scaling

Stability Analysis

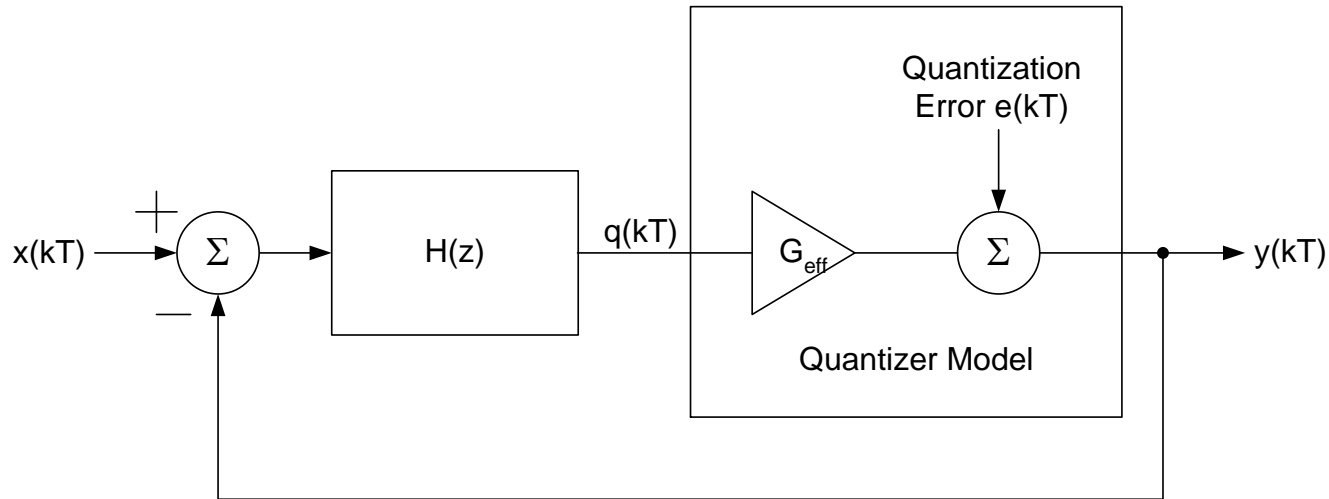


- Approach: linearize quantizer and use linear system theory!
- Effective quantizer gain

$$G_{\text{eff}}^2 = \frac{\overline{y^2}}{\overline{q^2}}$$

- Obtain G_{eff} from simulation


Modulator Root-Locus

 

sigma_delta_L5_H.m

- As G_{eff} increases, poles of STF move from
 - poles of $H(z)$ ($G_{\text{eff}} = 0$) to
 - zeros of $H(z)$ ($G_{\text{eff}} = \infty$)
- Pole-locations inside unit-circle correspond to stable modulator
- $G_{\text{eff}} > 0.45$ for stability


Effective Quantizer Gain, G_{eff}

 

sigma_delta_L5_peaks.m

- Large inputs \rightarrow comparator input grows
- Output is fixed (± 1)
- $\rightarrow G_{\text{eff}}$ drops
- \rightarrow modulator unstable for large inputs
- Solution:
 - Limit input amplitude
 - Detect instability (long sequence of +1 or -1) and reset integrators
 - Note: signals grow slowly for nearly stable systems \rightarrow use long simulations


Loop Voltages

 

- Internal signal amplitudes are weak function of input level (except near overload)
- Exceed supply voltage
- Solutions:
 - Reduce V_{ref} ??
 - Scaling

5th Order Modulator – Scaling

 Only the sign of Q matters: choose k_1 without changing the 1-Bit data at all




sigma_delta_L5_sim.mdl

Scaling Example


Integrator 3 Output times S:

K3 * S, b1 /S, a3 / S, K4 / S, b2 * S

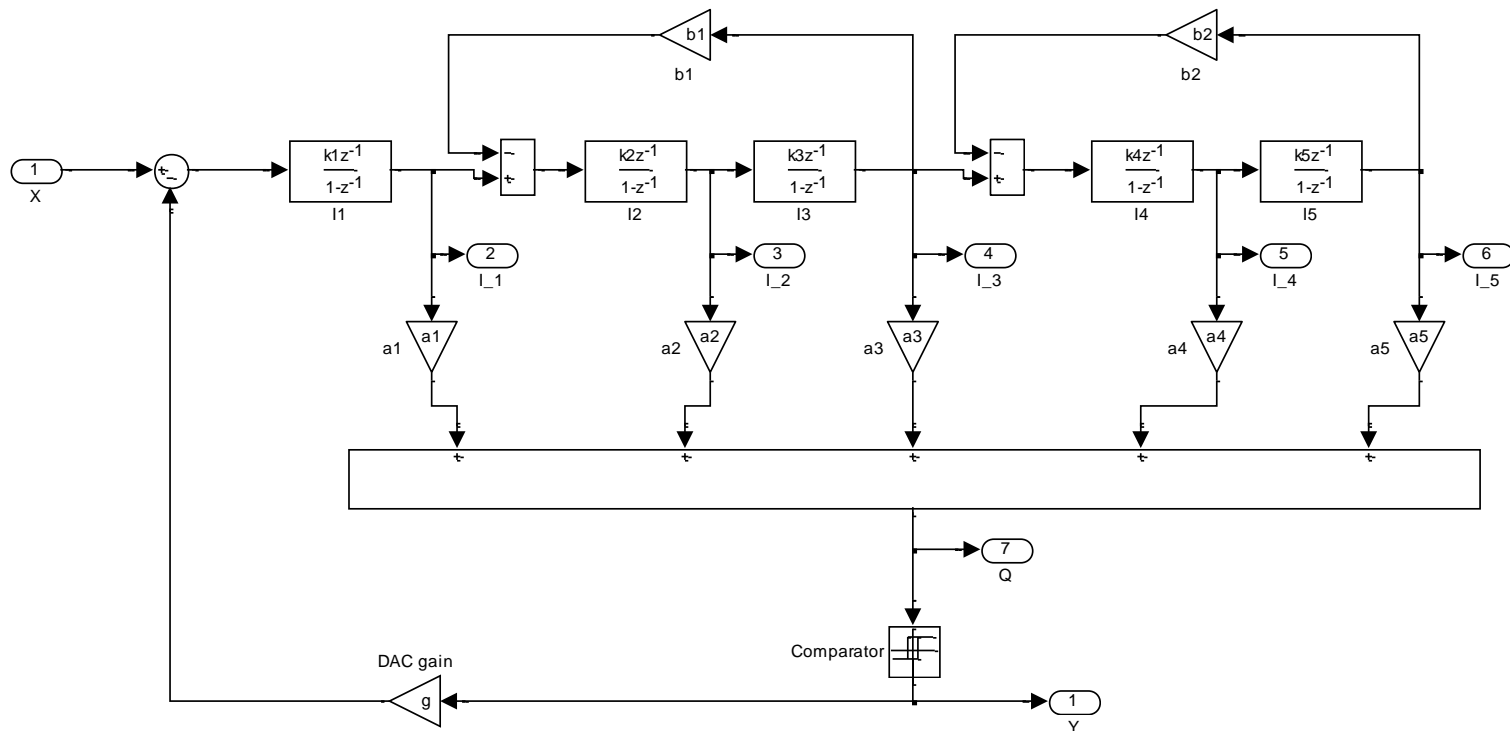

sigma_delta_L5_sim.mdl

Voltage Scaling

 


```
k1=1/10;  
k2=1;  
k3=1/4;  
k4=1/4;  
k5=1/8;  
a1= 1;  
a2=1/2;  
a3=1/2;  
a4=1/4;  
a5=1/4;  
b1=1/512;  
b2=1/16-1/64;  
g =1;
```

- Integrator output range is fine now
- But: maximum input signal limited to -5dB (-7dB with safety) – fix?

Input Range Scaling


Increasing the DAC levels by g reduces the analog to digital conversion gain:
 
$$\frac{D_{OUT}(z)}{V_{IN}(z)} = \frac{H(z)}{1 + gH(z)} \approx \frac{1}{g}$$




Increasing v_{IN} & DAC level (g) by the same factor
leaves 1-Bit data unchanged

Scaled Modulator Model

 

$g = 2.5;$

Scaled Model Overload

 

2dB safety margin for stability