

## Problem 1

Equation for a pulse:

$$p(t) := u(t) - u(t - \tau)$$

In the frequency domain:

$$H(s) := \frac{1}{s} - \frac{e^{-s \cdot \tau}}{s}$$

$$|H(j \cdot \omega)| = \frac{2 \sin\left(\frac{\omega \cdot \tau}{2}\right)}{\omega} \quad \text{[we ignore the pulse train scaling factor, since we normalize it out anyway]}$$

We normalize  $H(j\omega)$  by the gain at DC:

$$|H_{\text{norm}}(j \cdot \omega)| = \frac{|H(j \cdot \omega)|}{|H(0)|} = \frac{2 \sin\left(\frac{\omega \cdot \tau}{2}\right)}{\omega \tau}$$

The input frequency is  $f_s/2$ :

Define:

$$\omega = 2 \cdot \pi \frac{f_s}{2} = \frac{\pi}{T_s}$$

$$T_{\text{norm}} = \frac{\tau}{T_s} = \tau \cdot f_s \quad (\text{duty cycle})$$

$$\omega \cdot \tau = \pi \cdot T_{\text{norm}}$$

Set up the equation and solve:

$$\frac{2 \sin\left(\frac{\pi \cdot T_{\text{norm}}}{2}\right)}{\pi \cdot T_{\text{norm}}} = 10^{-20} \quad \text{solve} \rightarrow -0.52300039000913476872$$

[this function is symmetric around the y axis, and the numerical solver has trouble finding the positive solution]

Final answer:  $\tau = \frac{T_{\text{norm}}}{f_s} = \frac{0.523}{f_s}$  [Full credit for having a correct equation and the final answer for  $\tau$  in terms of the unknown, if you couldn't get the numerical solution.]

## Problem 2

Input signal:  $x(t) := \frac{1}{2} \cos(\omega \cdot t)$  1V peak to peak!!

Distortion function:  $\text{Dist}(V_{\text{in}}) := V_{\text{in}} + \beta \cdot V_{\text{in}}^3$

$$\text{Dist}(x(t)) \rightarrow \frac{\beta \cdot \cos(\omega \cdot t)^3}{8} + \frac{\cos(\omega \cdot t)}{2}$$

Apply trig identity:  $\frac{\beta}{8} \cdot \cos(\omega \cdot t)^3 + \frac{1}{2} \cdot \cos(\omega \cdot t) = \left(\frac{1}{2} + \frac{\beta}{8} \cdot \frac{3}{4}\right) \cdot \cos(\omega \cdot t) + \frac{\beta}{8} \cdot \frac{1}{4} \cdot \cos(3\omega \cdot t)$

$\beta := 0.05$

Calculate SFDR: 
$$\text{SFDR} := 20 \cdot \log \left( \frac{\frac{1}{2} + \frac{3 \cdot \beta}{32}}{\frac{\beta}{32}} \right) = 50.184 \quad (\text{dB})$$


### Problem 3

$$R_{\text{sh}}(x) := R_O \cdot (1 + \alpha \cdot x)$$

$$R(n) := \int_0^n \frac{R_{\text{sh}}(x)}{W} dx \rightarrow \frac{R_O \cdot n \cdot (\alpha \cdot n + 510)}{130050 \cdot W} \quad (\text{resistance to ground as a function of code})$$

$$V_o(n, \alpha) := \frac{R(n)}{R(255)} \rightarrow \frac{n \cdot (\alpha \cdot n + 510)}{255 \cdot (255 \cdot \alpha + 510)} \quad (\text{voltage divider})$$
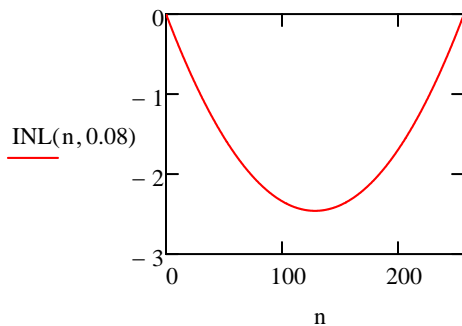
$$\text{INL}(n, \alpha) := \frac{V_o(n, \alpha) - \frac{n}{255}}{\frac{1}{256}} \quad \text{INL}(127, 0.08) = -2.462 \quad (\text{LSB, peak INL at midscale})$$




### Problem 4

The worst-case DNL will occur when the next unit element turns on in the MSB section, and all of the elements in the LSB section turn off. The expression is therefore:

$$\sigma_{\text{DNLmax}} = \sqrt{\sigma_1^2 + \left(2^{B_2} - 1\right) \cdot \sigma_2^2}$$

Note: depending on how you interpreted the problem, you may have multiplied  $\sigma_1$  by  $2^{B_2}$ . This answer will also be given full credit.

### Problem 5

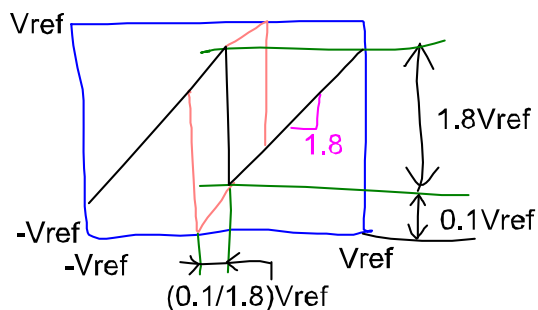

The ADC can tolerate up to  $0.056 \cdot V_{\text{ref}}$  of comparator offset (if  $V_{\text{ref}}$  is defined as shown in the picture) without the residue leaving the box.