

EE 240C


Analog-Digital Interface Integrated Circuits

Pipeline Design & Error Sources

Questions


- How to pick stage gain G for a given sub-ADC resolution?
- Impact and compensation of nonidealities?
 - Sub-ADC errors
 - Amplifier offset
 - Amplifier gain error
 - Sub-DAC error
- Begin to explore these questions using a simple example
 - First stage with 2-bit sub-ADC, followed by 2-bit backend

Comparator Offset

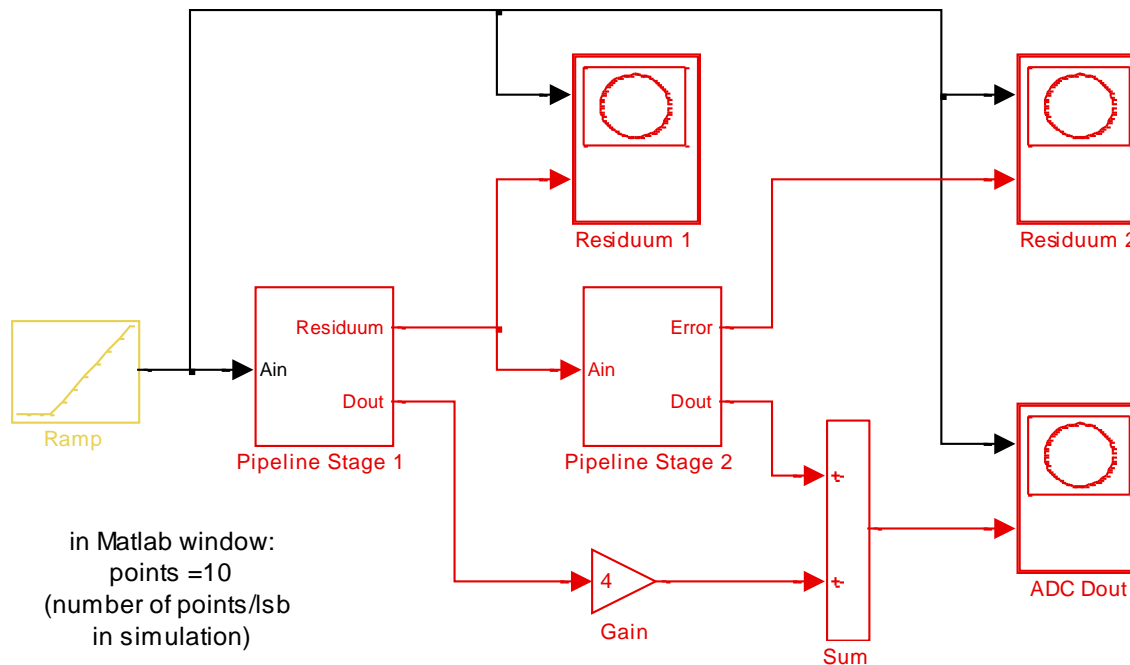


See Matlab/Simulink L18_pipe_2bps_error.mdl

Comparator Offset

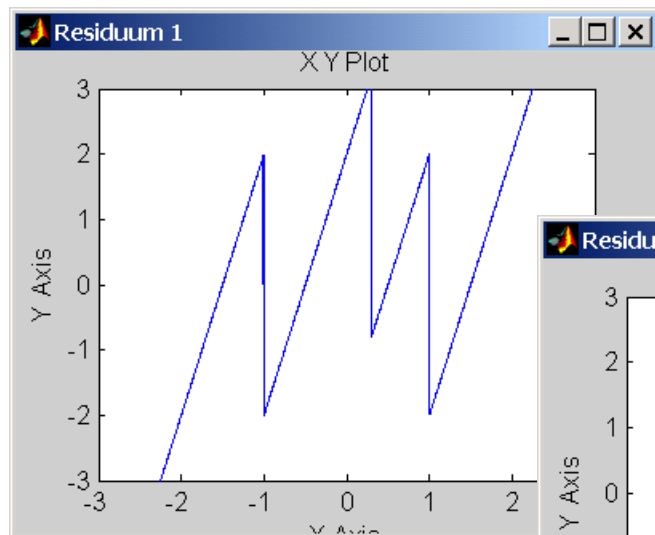

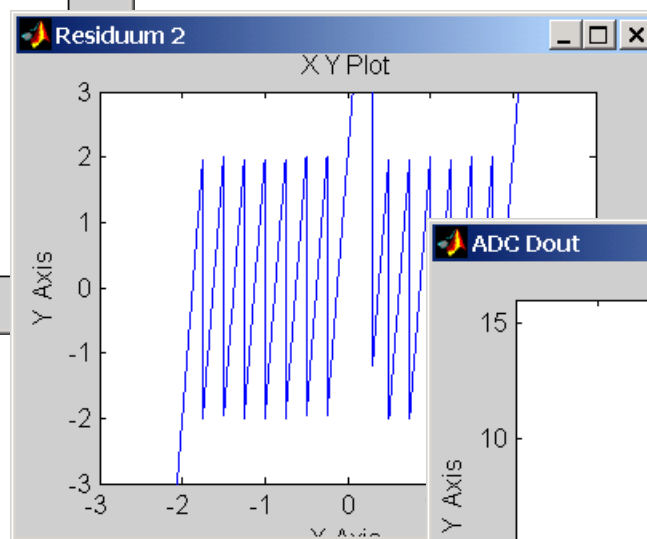← **Problem:** Residuum 1 overloads 2nd pipeline stage




First stage ADC Levels:

($\Delta = 1$)


Ideal: -1, 0, +1

Error: -1, 0.3, +1

 


Digital Correction

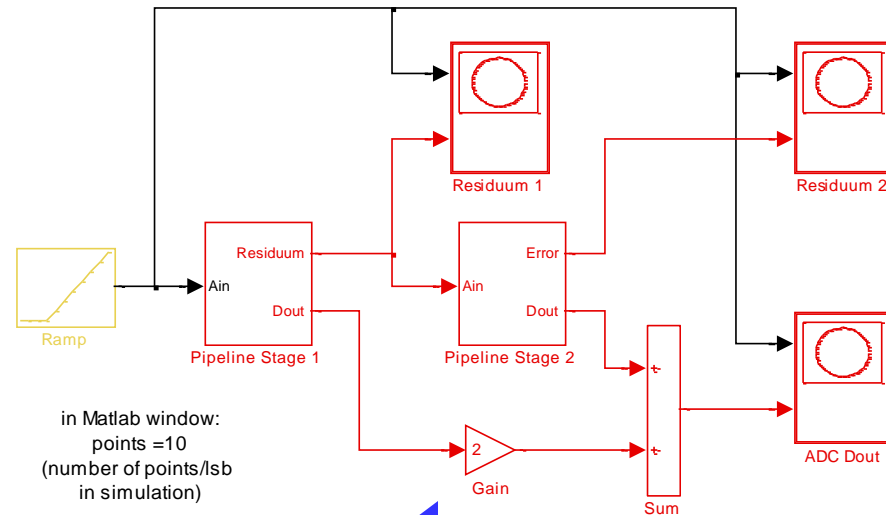Pipeline ADC, 2 bits per stage
Interstage gain = 2 for digital correction



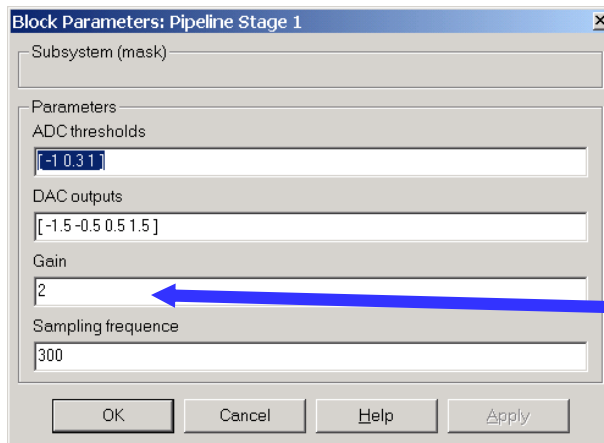
in Matlab window:
points =10
(number of points/lsb
in simulation)




Reduced interstage gain:

- No overload (due to comparator offset)
- Reduced input (only 1 bit resolution per stage)


Digital Correction

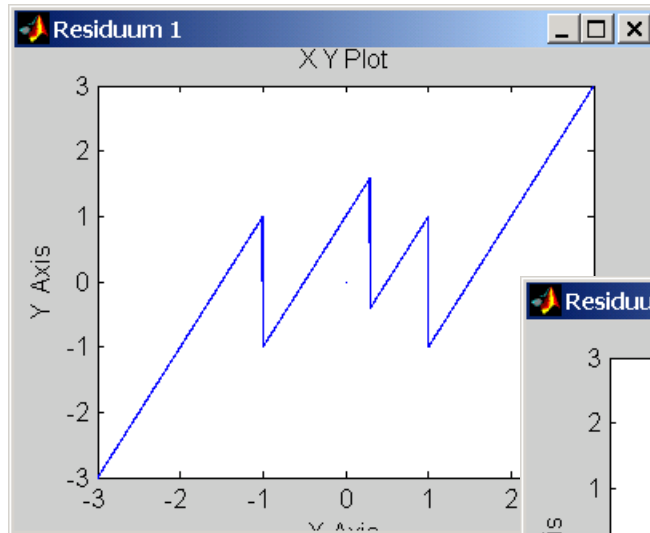

 
← “enlarged” residuum still within ± 2 input range of next stage



 Only 1 Bit resolution from first stage (3 Bit total) →




Issue with $G=2^B$

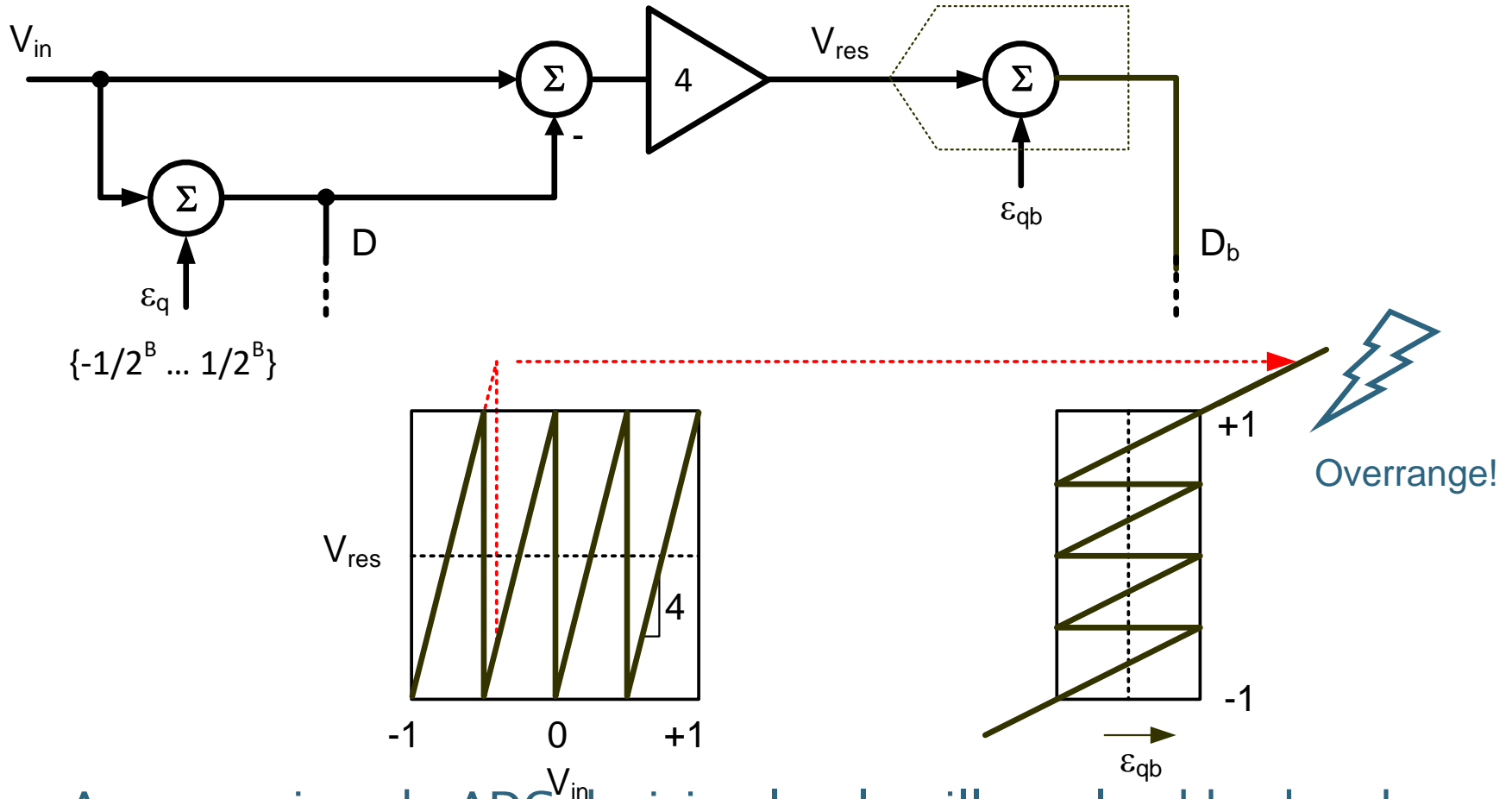


- Any error in sub-ADC decision levels will overload backend ADC and thereby deteriorate ADC transfer function

Idea #1: G slightly less than 2^B

 


- Effective stage resolution can be non-integer ($R = \log_2 G$)
 - E.g. $R = \log_2 3.2 = 1.68$ bits
- See e.g. [Karanicolas 1993]

Idea #2: $G < 2^B$, but Power of Two

 


- Effective stage resolution is an integer
 - E.g. $R = \log_2 2 = 1 = B-1$
 - Digital hardware requires only a few adders, no need to implement fractional weights
- See e.g. [Mehr 2000]

Idea #3: $G=2^B$, Extended Backend Range

 


- No redundancy in stage with errors
- Extra decision levels in succeeding stage used to bring residue "back into the box"
- See e.g. [Opris 1998]

Variant of Idea #2: "1.5-bit stage"

 





- Sub-ADC decision levels placed to minimize comparator count
- Can accommodate errors up to $\pm 1/4$
- $B = \log_2(2+1) = 1.589$ (sub-ADC resolution)
- $R = \log_2 2 = 1$ (effective stage resolution)
- See e.g. [Lewis 1992]

“1.5-bps” Stage

 

- A full bit of “overrange” is excessive for typical comparator offset
 - → use only 2 (rather than 3) comparators and $G=2$
- 3 DAC levels → $\log_2(3) = 1.585$ Bits
- Overall resolution:
 - 1 bps for all stages but last
 - 1.585 Bit for last

1.5-bps Pipeline

   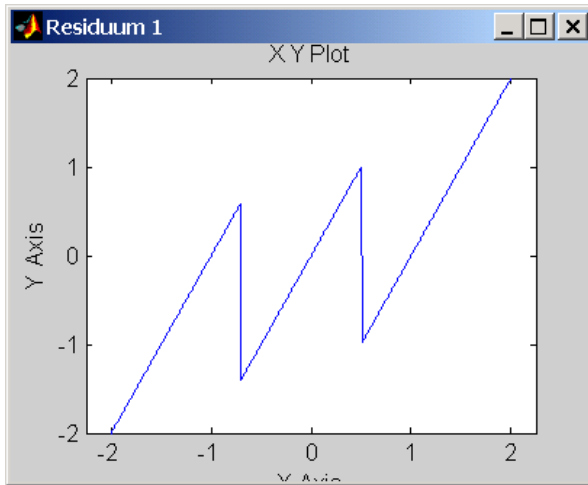

- What is the maximum offset that can be corrected?
- What is the offset of each comparator in this example?

Ref: S. Lewis et al, "A 10-b 20-Msample/s Analog-to-Digital Converter," J. Solid-State Circ., pp. 351-8, March 1992.

Summary on Sub-ADC Redundancy


- We can tolerate sub-ADC errors as long as
 - The residue stays "inside the box", or
 - Another stage downstream returns the residue "into the box" before it gets clipped or reaches the last quantizer
- This result applies to any stage in an n-stage pipeline
 - Can always decompose pipeline into single stage + backend ADC
- In literature, sub-ADC redundancy schemes are often called "digital correction"
- There is no explicit error correction!
 - Sub-ADC errors are absorbed in the same way as their inherent quantization error
 - Provided there is no clipping ...

EE 240C

Analog-Digital Interface Integrated Circuits


Pipeline Amplifier Errors

Amplifier Offset

 

- Amplifier offset can be referred toward stage input and results in
 - Global offset
 - Usually no problem, unless "absolute ADC accuracy" is required
 - Sub-ADC offset
 - Easily accommodated through redundancy

Gain Errors

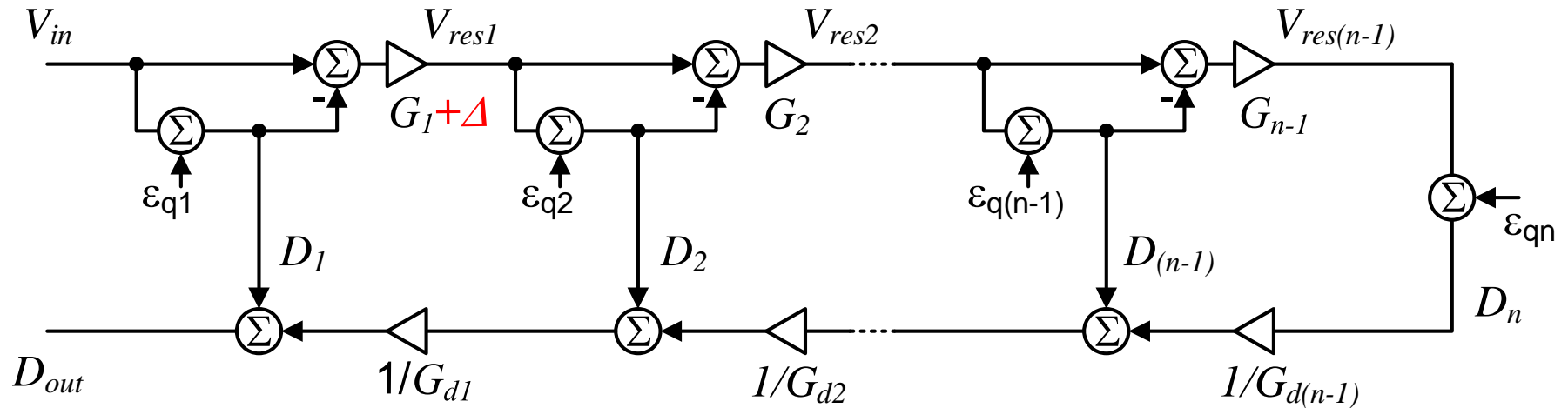



$$D_{out} = V_{in} + \epsilon_{q1} \left(1 - \frac{G_1 + \Delta}{G_{d1}} \right) + \dots + \frac{\epsilon_{qn}}{\prod_{j=1}^{n-1} G_{dj}}$$

- Want to make $G_{d1} = G_1 + \Delta$

Digital Gain Calibration (1)

- Error in analog gain is not a problem as long as "digital gain term" is adjusted appropriately
- Problem
 - Need to measure analog gain precisely
- Example
 - Digital calibration of a 1-bit first stage with 1-bit redundancy ($R=1$, $B=2$)
- Note
 - Even if all G_{dj} are perfectly adjusted to reflect the analog gains, the ADC will have non-zero DNL and INL, bounded by $\pm 0.5\text{LSB}$. This can be explained by the fact that the residue transitions may not correspond to integer multiples of the backend-LSB. This can cause non-uniformity in the ADC transfer function (DNL, INL) and also non-monotonicity (see [Markus, 2005]).
 - In case this cannot be tolerated
 - Add redundant bits to ADC backend (after combining all bits, final result can be truncated back), or
 - Calibrate analog gain terms

Digital Gain Calibration (2)

 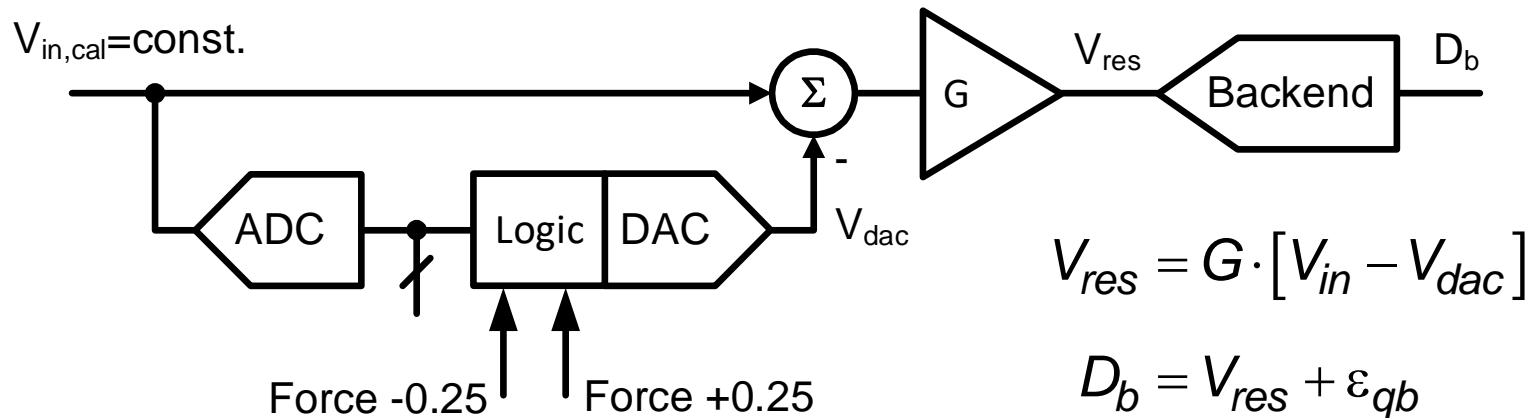

Digital Gain Calibration (3)


Step1: $D_b^{(1)} = G \cdot [V_{in} + 0.25] + \varepsilon_{qb}^{(1)}$

Step2: $D_b^{(2)} = G \cdot [V_{in} - 0.25] + \varepsilon_{qb}^{(2)}$

$$D_b^{(1)} - D_b^{(2)} = 0.5 \cdot G + \varepsilon_{qb}^{(1)} - \varepsilon_{qb}^{(2)}$$


- Can minimize impact of quantization error using
 - Averaging (thermal noise dither)
 - Extra backend resolution

DAC Calibration

 


- Essentially same concept as gain calibration
 - Step through DAC codes and use backend to measure errors
- Store coefficients for each DAC transition in a look-up table

Recursive Stage Calibration

 


- First few stages have most stringent accuracy requirements
 - Errors of later stages are attenuated by aggregate gain
- Commonly used algorithm [Karanicolas 1993]
 - Take ADC offline
 - Measure least significant stage that needs calibration first
 - Move to next significant stage and continue toward stage 1

Calibration Hardware Example

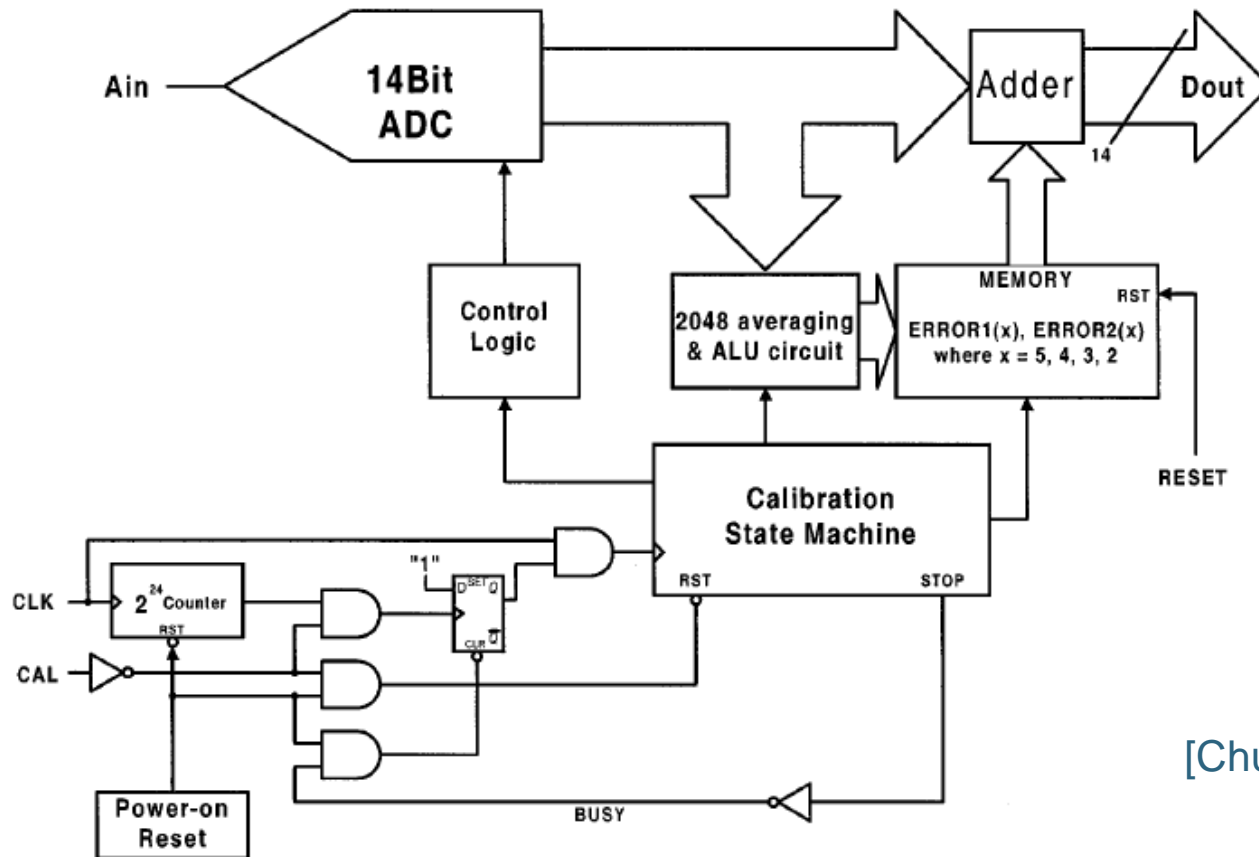

[Chuang 2002]

Non-Linear Gain Calibration

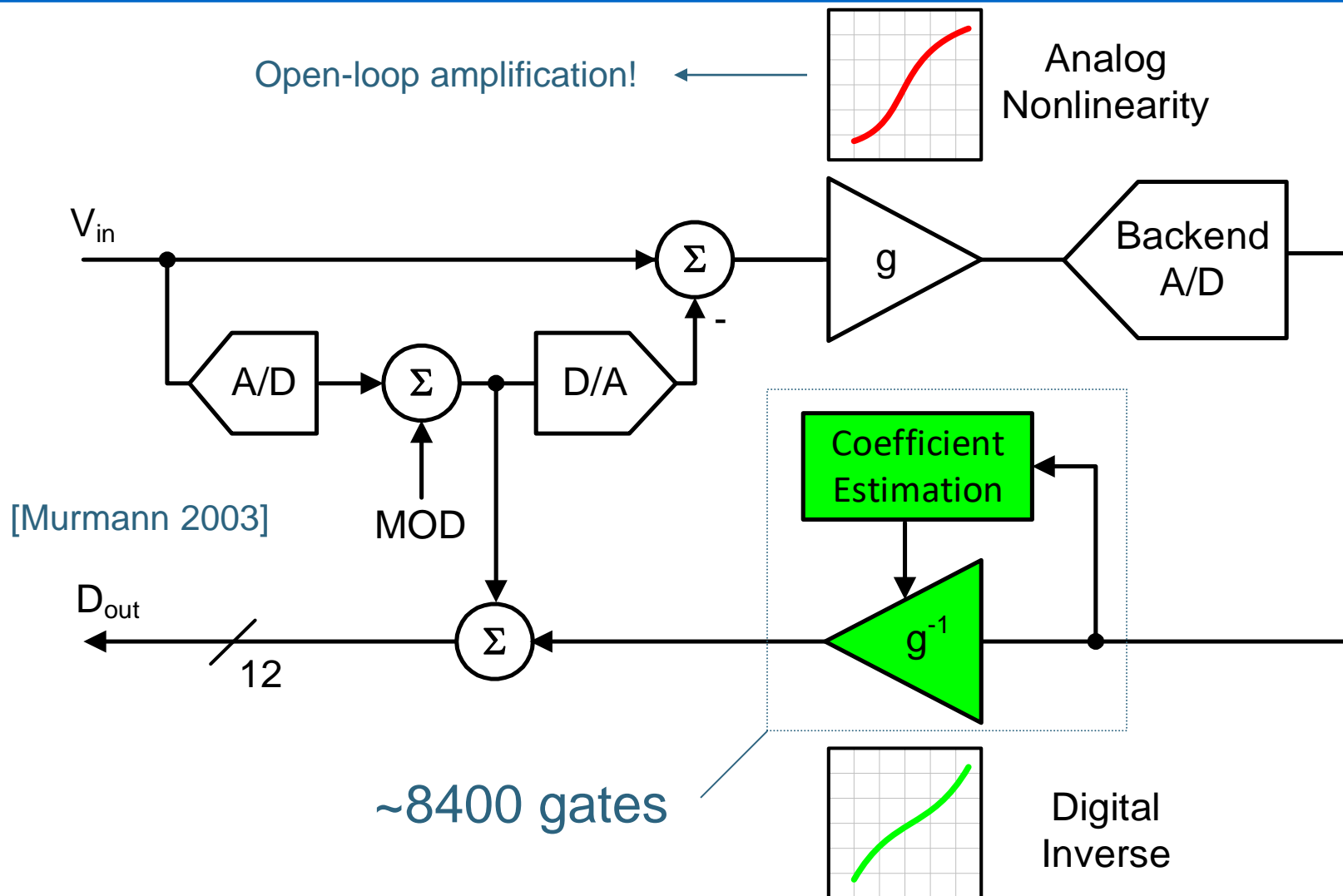

Alternative Schemes

- Other foreground calibration schemes
 - Calibrate ADC starting from first stage [Singer 2000]
 - Connect stages in a circular loop [Soenen 1995]
- Background calibration
 - See e.g. [Ming 2001]
 - Makes sense primarily when calibration parameters are expected to drift
 - Capacitor ratios do not drift!
 - Background calibration is justifiable e.g. when drift in OTA open-loop gain is an issue


EE 240C

Analog-Digital Interface Integrated Circuits

Pipeline Digital Backend

Combining the Bits (1)

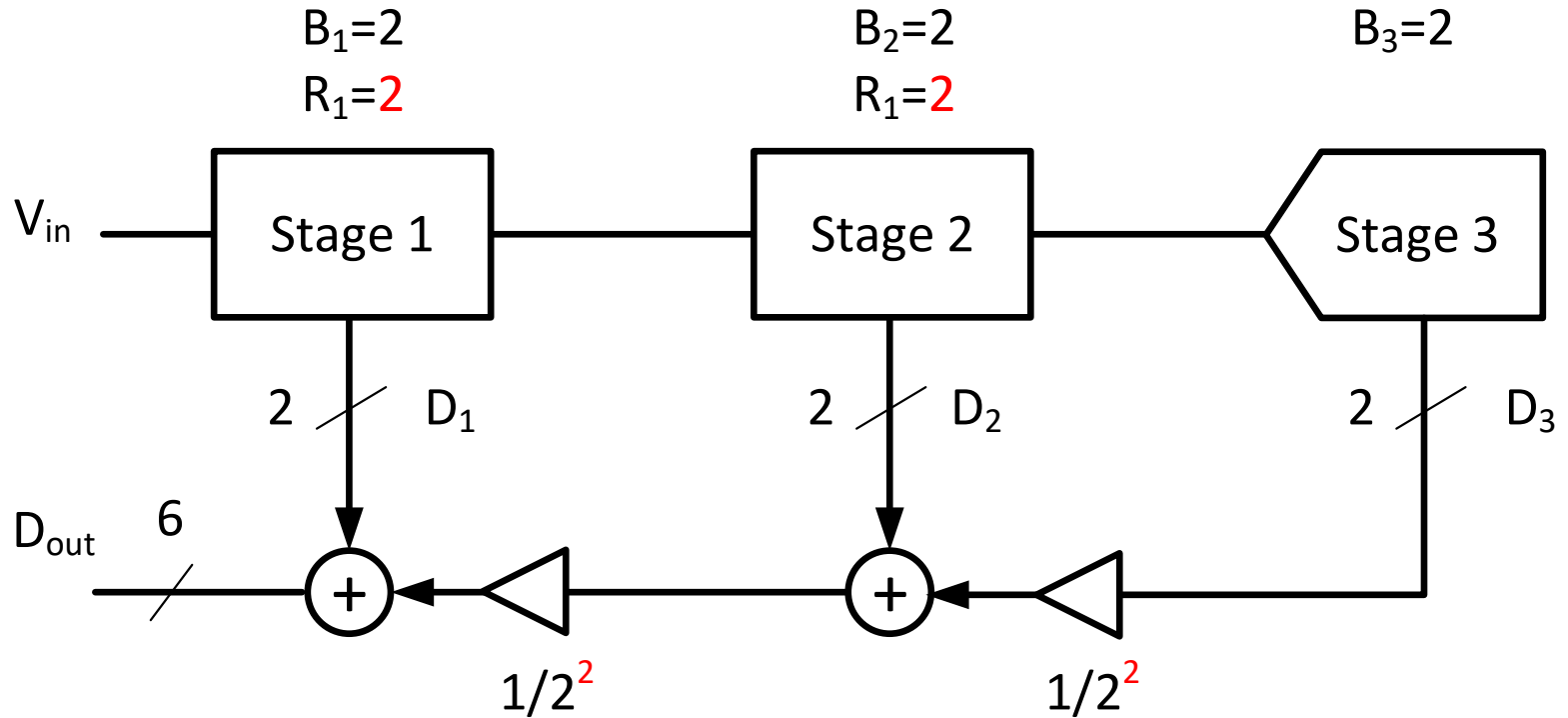- Example1: Three 2-bit stages, no redundancy




$$D_{out} = D_1 + \frac{1}{4} D_2 + \frac{1}{16} D_3$$

Combining the Bits (2)

D_1 **XX**
 D_2 **XX**
 D_3 **XX**


 D_{out} **DDDDDD**

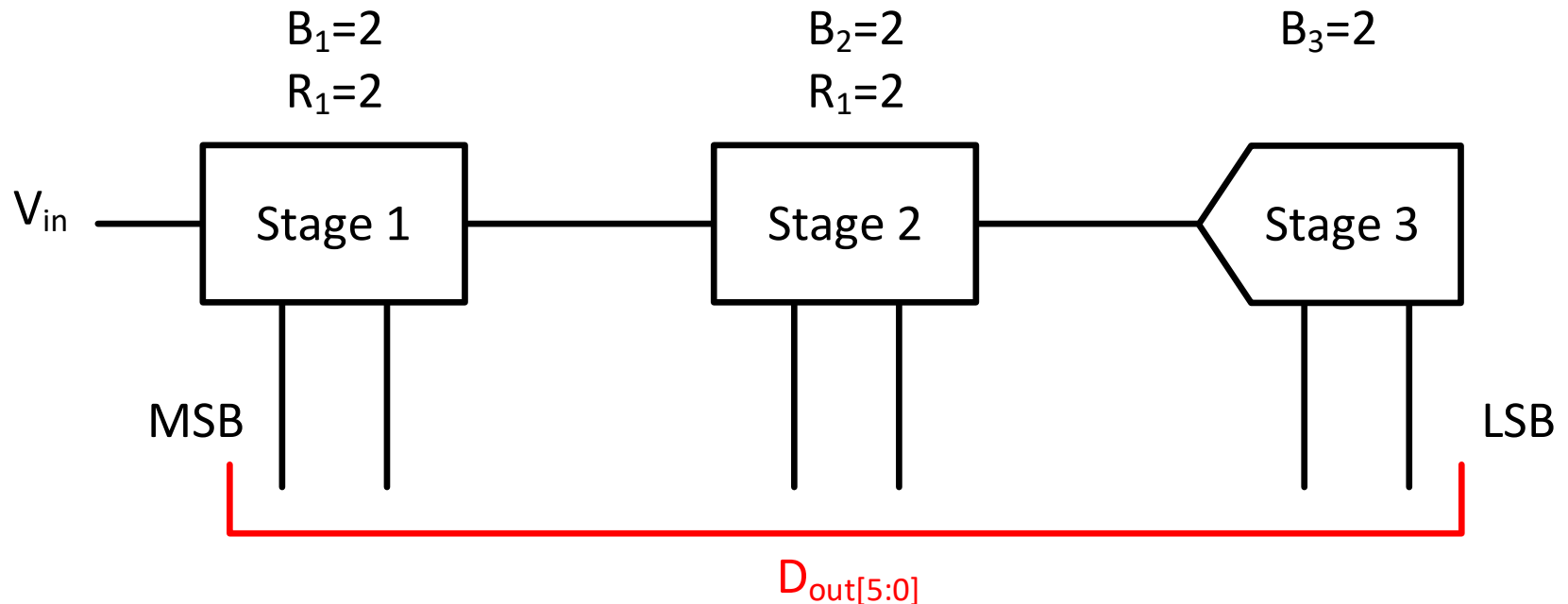- Only bit shifts
- No arithmetic circuits needed



Combining the Bits (3)

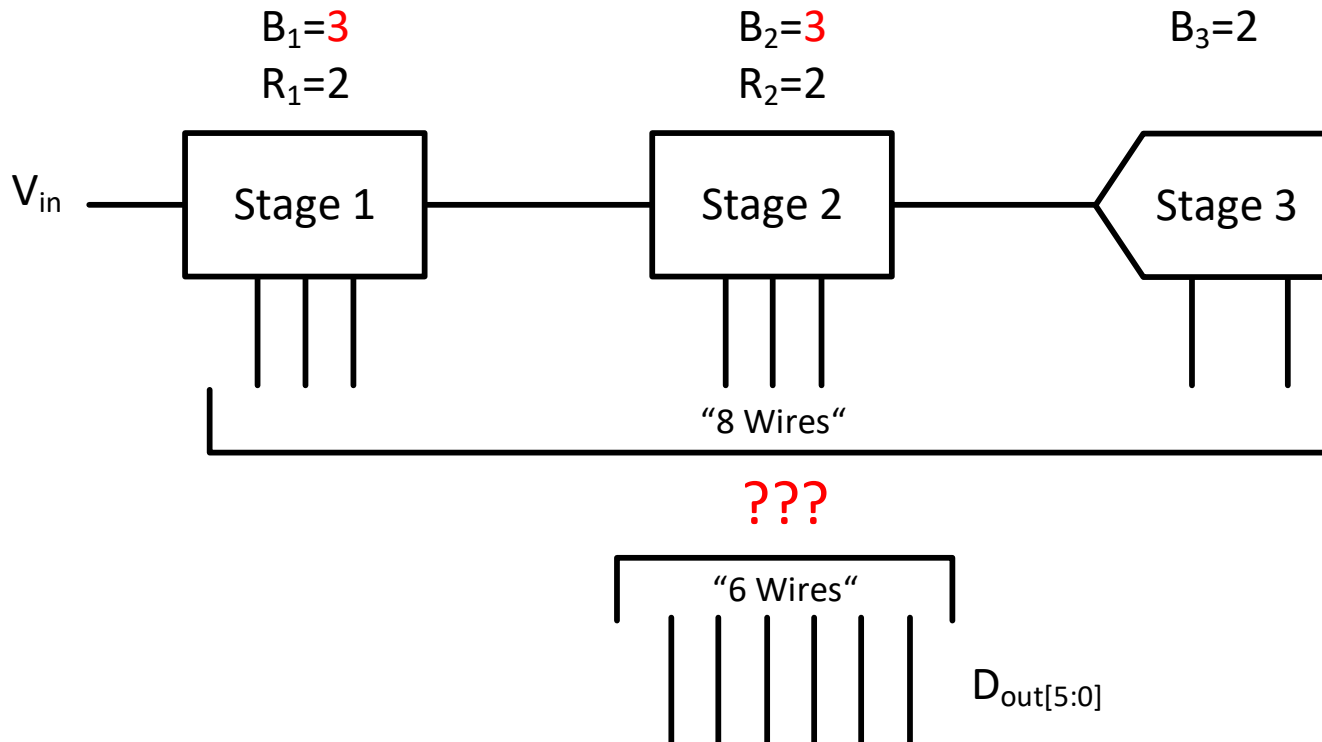- Example2: Three 2-bit stages, one bit redundancy in stages 1 and 2 (6-bit aggregate ADC resolution)




Combining the Bits (4)

$$D_{out} = D_1 + \frac{1}{4}D_2 + \frac{1}{16}D_3$$


D_1 **xxx**
 D_2 **xxx**
 D_3 **xx**

 D_{out} **DDDDDD**

- Bits overlap
- Need adders

 

Combining the Bits (5)

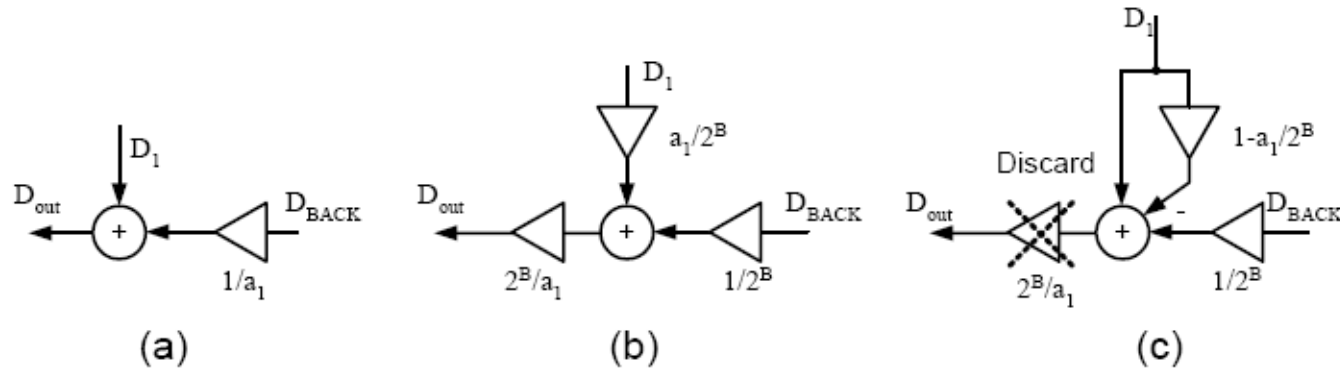

- For fractional weights (e.g. radix < 2), there is no need to implement complex multipliers
- Can still use simple bit shifts; push actual multiplication into low-resolution output
 - E.g. a 1x10 bit multiplication needs only one adder...
- See e.g. [Karanicolas 1993]

EE 240C


Analog-Digital Interface Integrated Circuits

Pipeline Implementation Considerations


Outline

- Background
 - History and state-of the art performance
 - General idea of multi-step A/D conversion
- Pipeline ADC basics
 - Ideal block diagram and operation, impact of block nonidealities
- Ways to deal with nonidealities
 - Redundancy, calibration
- CMOS implementation details
 - Stage scaling, MDAC design
- Architectural options
 - OTA sharing, SHA-less front-end
- Research topics

Stage Implementation

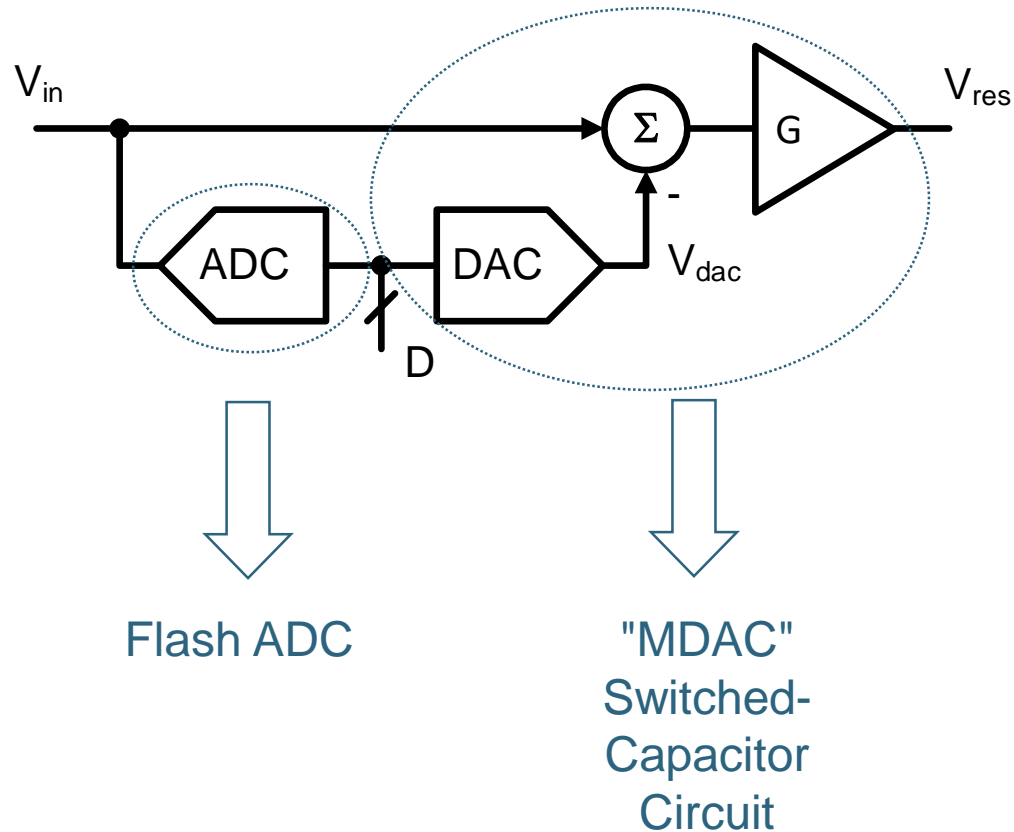

Generic Circuit

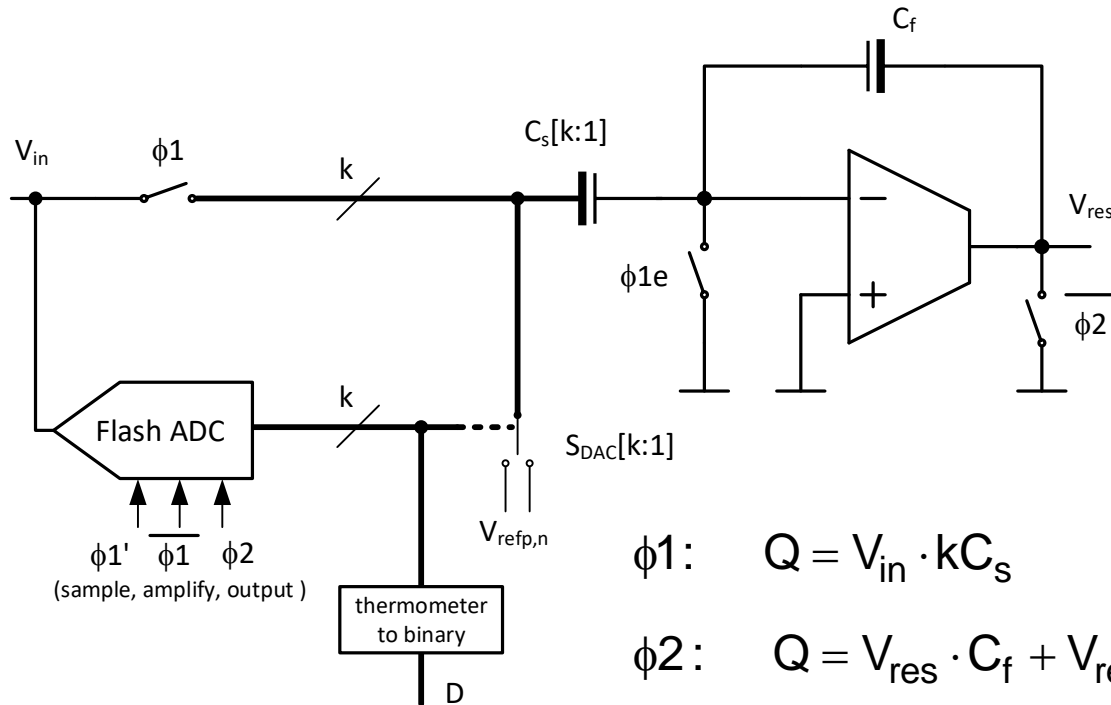

$$\phi1: \quad Q = V_{in} \cdot kC_s$$

$$\phi2: \quad Q = V_{res} \cdot C_f + V_{refp} \cdot mC_s + V_{refn} \cdot (k - m)C_s$$

$$\begin{aligned} \therefore -V_{res} &= \frac{kC_s}{C_f} V_{in} - \frac{mC_s}{C_f} V_{refp} + \frac{(k - m)C_s}{C_f} V_{refn} \\ &= G \cdot (V_{in} - V_{dac}) \end{aligned}$$

Endless List of Design Parameters


- Stage resolution, stage scaling factor
 - Stage redundancy
 - Thermal noise/quantization noise ratio
 - OTA architecture
 - OTA sharing?
 - Switch topologies
 - Comparator architecture
 - Front-end SHA vs. SHA-less design
 - Calibration approach (if needed)
 - Technology and technology options (e.g. capacitors)
- A very complex optimization problem!

Thermal Noise Considerations

- Total input referred noise
 - Thermal noise + quantization noise
 - Costly to make thermal noise smaller than quantization noise
- Example: $V_{FS}=1V$, 10-bit ADC
 - $N_{\text{quant}} = \text{LSB}^2 / 12 = (1V / 2^{10})^2 / 12 = (280\mu\text{Vrms})^2$
 - Design for total input referred thermal noise $\sim 280\mu\text{Vrms}$ or larger, if SNR target allows
- Total input referred thermal noise is the sum of noise in all stages
 - How should we distribute the total thermal noise budget among the stages?
 - Let's look at an example...

Stage Scaling (1)

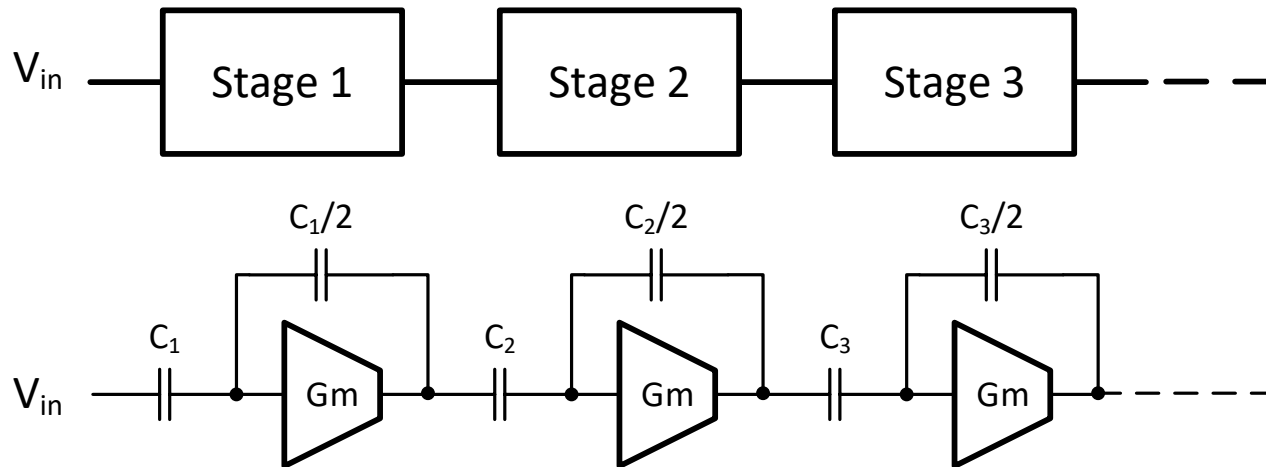
- Example: Pipeline using 1-bit (effective) stages ($G=2$)



- Total input referred noise power

$$N_{\text{tot}} \propto kT \left[\frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$$


Stage Scaling (2)

 

$$N_{\text{tot}} \propto kT \left[\frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$$

- If we make all caps the same size, backend stages contribute very little noise
- Wasteful, because Power $\sim G_m \sim C$

Stage Scaling (3)

 


$$N_{tot} \propto kT \left[\frac{1}{C_1} + \frac{1}{4C_2} + \frac{1}{16C_3} + \dots \right]$$


- How about scaling caps down by $2^2=4x$ per stage?
 - Same amount of noise from every stage
 - All stages contribute significant noise
 - Noise from first few stages must be reduced
 - Power $\sim G_m \sim C$ goes up!

Stage Scaling (4)

Extreme 1: All Stages the Same Size

 

Extreme 2: All Stages Contribute the Same Noise

 


[Cline 1996]

- Optimum capacitor scaling lies approximately midway between these two extremes


Shallow Optimum

[Chiu 2004]

 


Capacitor scaling factor = 2^{Rx} $x=1 \Rightarrow$ scaling exactly by stage gain

Stage Scaling Examples (1)

 


stage 0 comparators
stage 0 sampling capacitors
stage 0 opamp
stage 0 sampling switches



[Cline 1996]

 

Stage Scaling Examples (2)

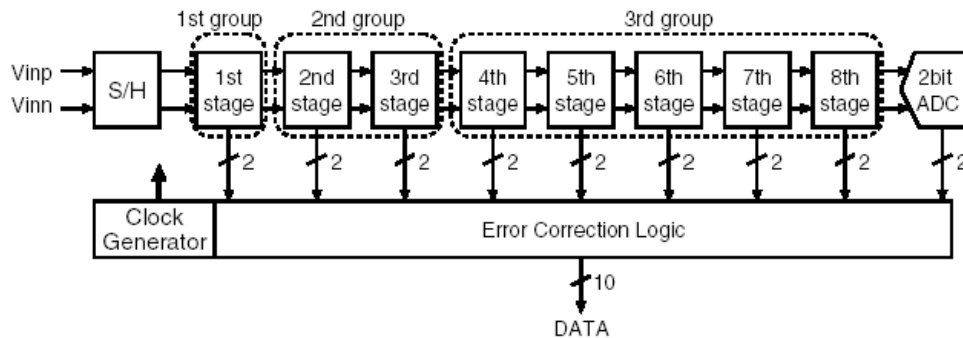


[Ishii 2005]

  

How Many Bits Per Stage?

- Low per-stage resolution (e.g. 1-bit effective)
 - Need many stages
 - + OTAs have small closed loop gain, large feedback factor
 - High speed
- High per-stage resolution (e.g. 3-bit effective)
 - + Fewer stages
 - OTAs can be power hungry, especially at high speed
 - Significant loading from flash-ADC
 - First stage output precision is significantly below overall ADC precision
- Qualitative conclusion
 - Use low per-stage resolution for very high speed designs
 - Try higher resolution stages when power efficiency is most important constraint

Power Tradeoff is Fairly Flat!

 

η = parasitic cap at output/total sampling cap in each stage (junctions, wires, switches, ...)

- ADC power varies by only $\sim 2\times$ across different stage resolutions!

EE 240C

Analog-Digital Interface Integrated Circuits

Pipeline Examples

Examples

Reference	[Yoshioka, 2007]	[Jeon, 2007]	[Loloe 2002]	[Bogner 2006]
Technology	90nm	90nm	0.18um	0.13um
Bits	10	10	12	14
Bits/Stage	1-1-1-1-1-1-1-3	2-2-2-4	1-1-1-1-1-1-1-1-1-1-2	3-3-2-2-4
SNDR [dB]	~56	~54	~65	~64
Speed [MS/s]	80	30	80	100
Power [mW]	13.3	4.7	260	224
mW/MS/s	0.17	0.16	3.25	2.24


- Low power is possible for a wide range of architectures!

Re-Cap

- Choosing the "optimum" per-stage resolution and stage scaling scheme is a non-trivial task
 - But – optima are shallow!
- Quality of transistor level design and optimization is at least as important (if not more important than) architectural optimization ...
- Next, look at circuit design details
 - Assume we're trying to build a 10-bit pipeline
 - Technology feature size $\sim 0.18\mu\text{m}$ or smaller
 - Moderate to high-speed $\sim 100\text{MS/s}$
 - 1-bit effective/stage, using "1.5-bit" stage topology
 - Dedicated front-end SHA

1.5-Bit Stage Implementation


[Abo 1999] [Lewis 1992]

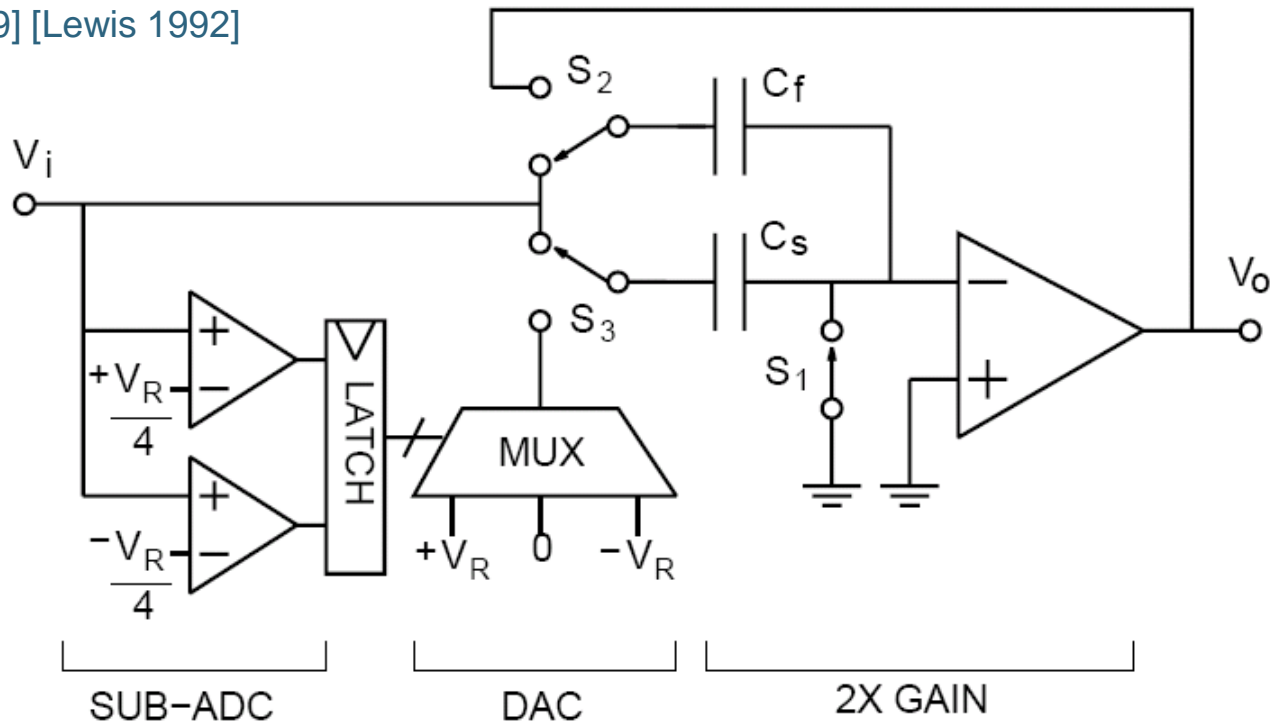

- C_f is used as sampling cap during acquisition phase, as feedback cap in redistribution phase
 - Helps improve feedback factor (max. $1/3 \rightarrow$ max. $1/2$)


Residue Plot

$$V_o = \begin{cases} \left(1 + \frac{C_s}{C_f}\right) V_i - \frac{C_s}{C_f} V_{ref} & \text{if } V_i > V_{ref}/4 \\ \left(1 + \frac{C_s}{C_f}\right) V_i & \text{if } -V_{ref}/4 \leq V_i \leq +V_{ref}/4 \\ \left(1 + \frac{C_s}{C_f}\right) V_i + \frac{C_s}{C_f} V_{ref} & \text{if } V_i < -V_{ref}/4 \end{cases}$$

 

[Abo 1999]

Stage 1 Matching Requirements

 


- Error in residue transition must be accurate to within a fraction of 9-bit backend LSB
 - Typically want $\Delta C/C \sim 0.1\%$ or better

Capacitor Matching

- 0.1% "easily" achievable in current technologies
 - Even with metal sandwich caps, see e.g. [Verma 2006]
 - Beware of metal density related issues
 - For MIMCap matching data see e.g. [Diaz 2003]
- What if we needed much higher resolution than 10 bits?
 - Digital calibration
 - Multi-bit first stage
 - Each extra bit resolved in the first stage alleviates precision requirements on residue transition by 2x
 - For fixed capacitor matching, can show that each (effective) bit moved into the first stage
 - Improves DNL by 2x
 - Improves INL by $\sqrt{2}$ x
 - Multi-bit examples: [Singer 1996] [Kelly 2001] [Lee 2007]

Typical Reference Generator

[Brooks 1994]

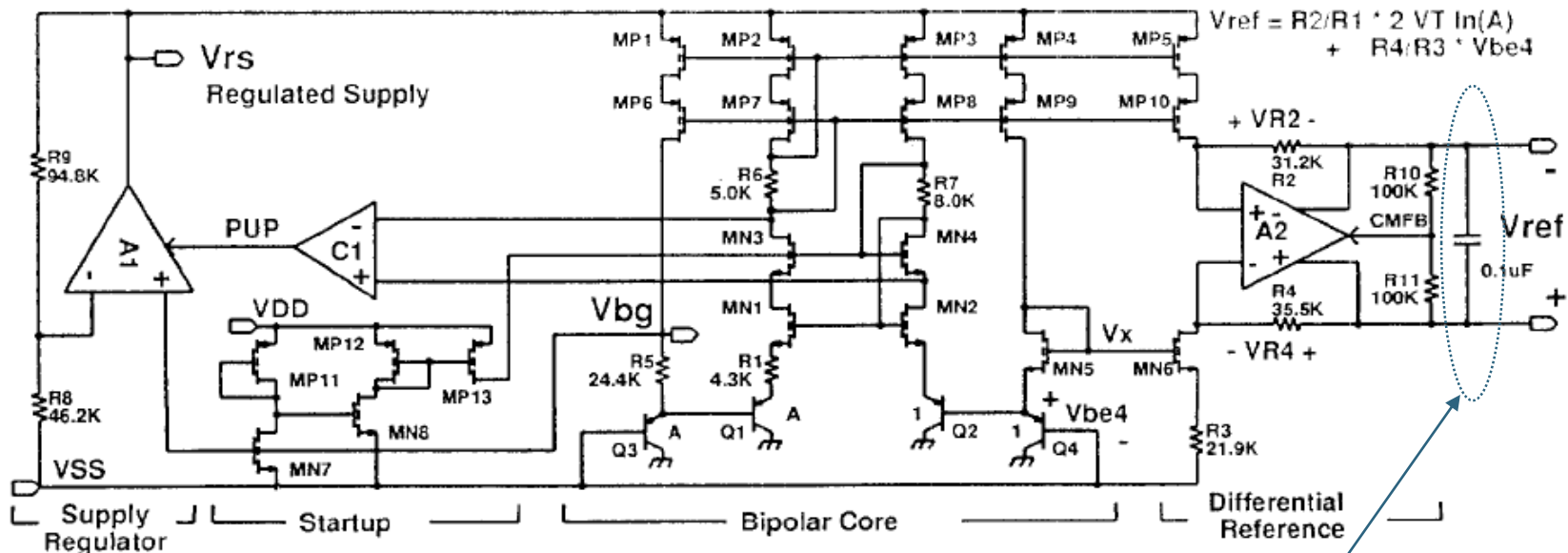




External decoupling caps provide dynamic currents
 \Rightarrow Low power reference buffer

Comparators

- Can tolerate large offsets and large noise with appropriate redundancy
- Consume negligible power in a good design
 - 50–100 μ W or less per comparator
- Lots of implementation options
 - Resistive/capacitive reference generation
 - Different pre-amp/latch topologies
 - ...

Comparator Examples

[Chiu 2004]

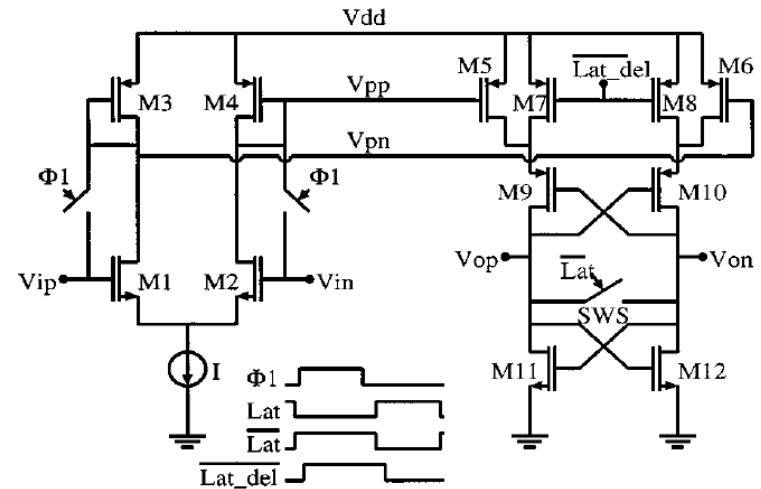  


[Mehr 2000]

OTA Design Considerations

- Static amplifier error = $1/(\text{DC Loop Gain})$
 - E.g. for 0.1% accuracy in first stage of 10-bit ADC, need loop gain $> 60\text{dB}$
- Dynamic settling error
 - Typically want to settle outputs to $\sim 1/8$ LSB accuracy within $1/2$ clock cycle
- Thermal noise
 - Size capacitors to satisfy kT/C noise requirement
- Start by picking an OTA topology that will deliver sufficient gain
 - Or think about ways to compensate finite gain error ...
- General references on OTA design
 - 240B [Boser 2005], [Murmamnn], [Alon]

Two-Stage Folded Cascode OTA

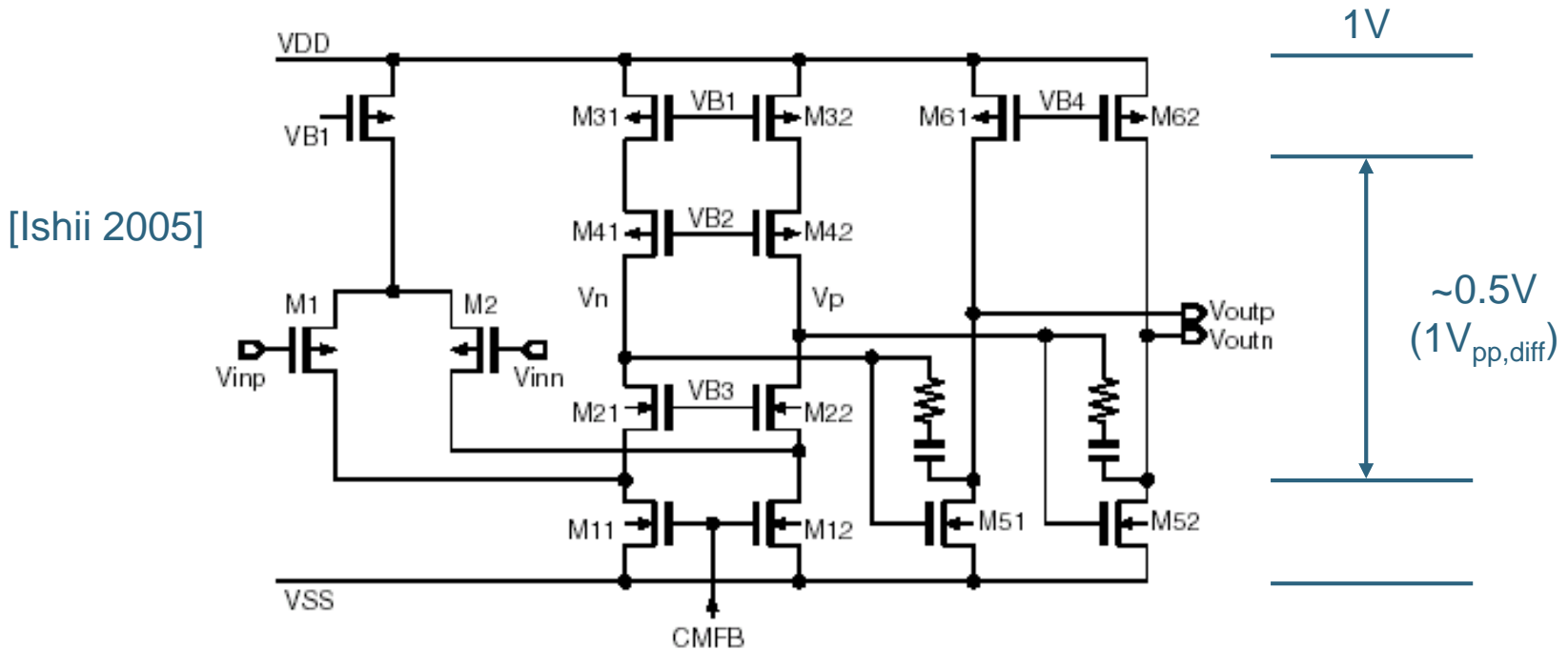

- Works down to $V_{DD}=1V$ with reasonable output swing
- Gain $\sim (g_m r_o)^3 \sim 10^3 = 60dB$
- Use gain boosting to achieve larger gain

How Fast Can We Go? (1)

- Non-dominant pole in two-stage amplifier hard to move past $f_T/5$
- For 73 degrees phase margin (optimum for fast settling), loop crossover frequency is 1/3 of non-dominant pole frequency
- Settling linearly to 0.1% precision takes 7 loop time constants; typically budget ~10 time constants
- Ideally, we'd have 1/2 clock cycle to settle linearly, but there is some time needed for slewing and non-overlap clock timing
 - Assume 60% of half cycle is available for linear settling
- In summary


$$f_{CLK,max} = \frac{f_T}{5} \frac{1}{3} \cdot 2\pi \cdot \frac{1}{10} 0.5 \cdot 0.6 = \frac{f_T}{80}$$

How Fast Can We Go? (2)

Technology	NMOS f_T (at moderate $V_{GS}-V_t \sim 150\text{mV}$)	$f_{\text{CLK,max}} = f_T/80$
0.35 μm	10GHz	125 MHz
0.18 μm	30GHz	375 MHz
90nm	90GHz	1.125GHz

- Sampling speeds of 200–300MHz are "easily" achievable modern technologies
 - f_T is no longer a showstopper
 - Speed ultimately constrained by power, power efficiency and/or clock jitter

Switches

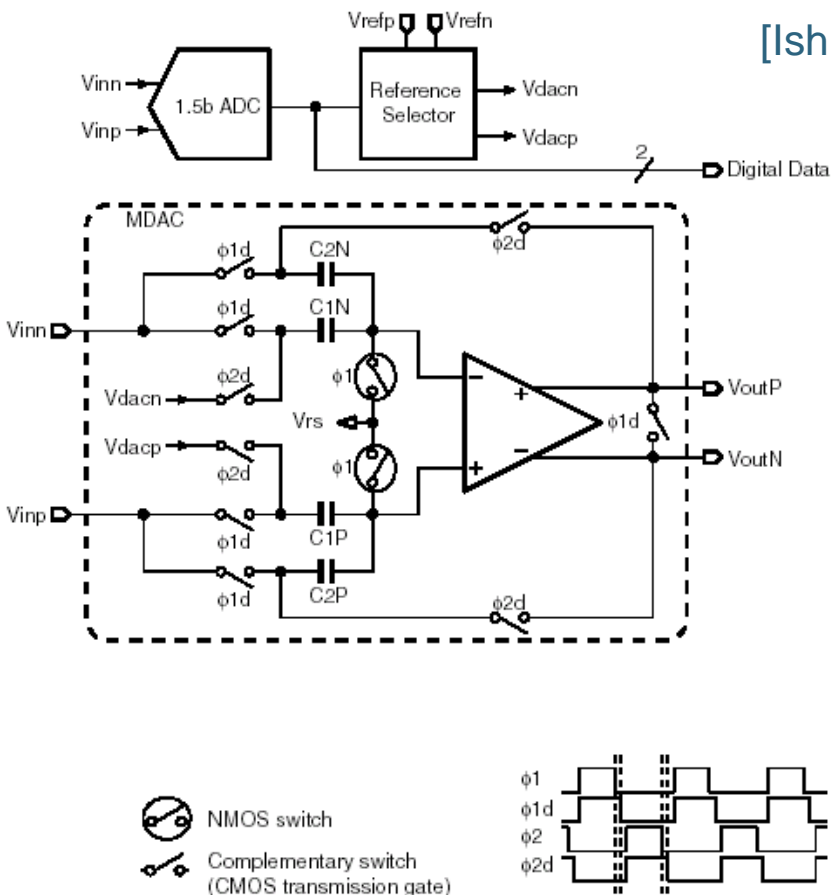

- Make switch RC ~ 10 times faster than OTA
 - Avoids speed degradation
 - Minimizes switch noise contribution
 - See e.g. [Schreier 2005]
 - Avoids stability issues due to poles in feedback network
- Three choices for switches
 - Single N or P device
 - Transmission gate
 - Bootstrapped NMOS
 - For high swing nodes that require constant R_{on}

EE 240C


Analog-Digital Interface Integrated Circuits

Pipeline SHA



Front-End SHA

Need constant R_{ON} here to minimize signal dependent charge injection from S_{1N} , S_{1P}


Minimize Jitter!

 

[Ishii 2005]

  

Total Integrated OTA Noise (1)

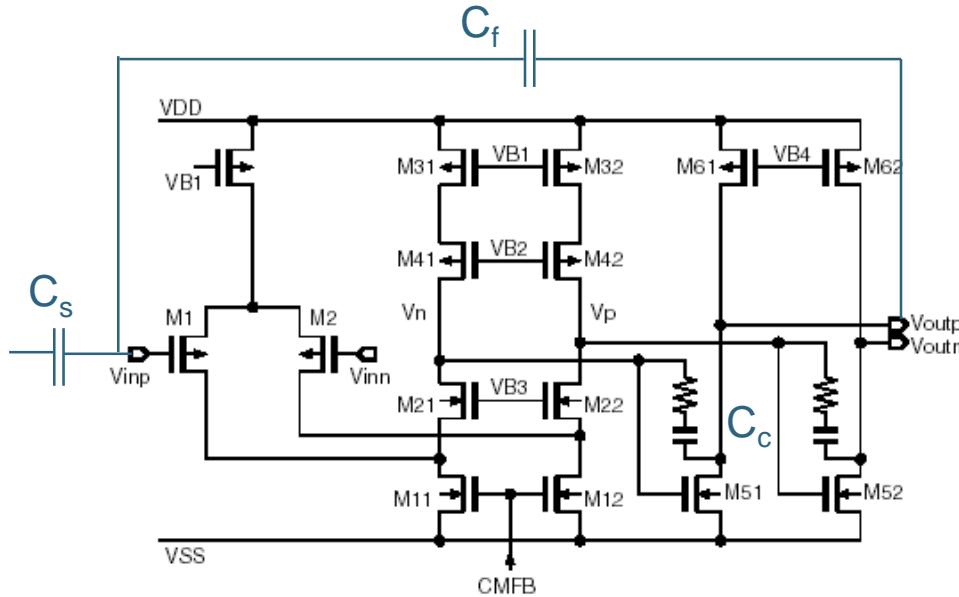

$$N_1 = 1 + \frac{g_{m11} + g_{m31}}{g_{m1}} \cong 2 \dots 4$$

$$N_2 = 1 + \frac{g_{m61}}{g_{m51}} \cong 2$$

$$\overline{V_{od}^2} = \underbrace{2 \frac{1}{\beta} \cdot \gamma \cdot N_1 \frac{kT}{C_c}}_{\text{OTA Stage 1}} + \underbrace{2(\gamma \cdot N_2 + 1) \frac{kT}{C_{Ltot}}}_{\text{OTA Stage 2}}$$

$$\beta = \frac{C_f}{C_f + C_s + C_{gs1}}$$

$$C_{Ltot} = C_L + (1 - \beta)C_f + C_{\text{parasitic}}$$

ignore in first
cut design

Total Integrated OTA Noise (2)

- Assuming $\gamma=1$, $N_1=N_2=2$


$$\overline{V_{od}^2} = 4 \frac{1}{\beta} \cdot \frac{kT}{C_c} + 6 \frac{kT}{C_{Ltot}}$$

- OTA noise partitioning problem
 - How should we split noise between stage1 and stage2 terms?
- In this design example we'll use a 2/3, 1/3 split
 - This is yet another design/optimization parameter
- With this assumption, we have

$$\overline{V_{od}^2} = 18 \frac{kT}{C_{Ltot}}$$

$$C_c = \frac{C_{Ltot}}{3\beta}$$

SHA Noise

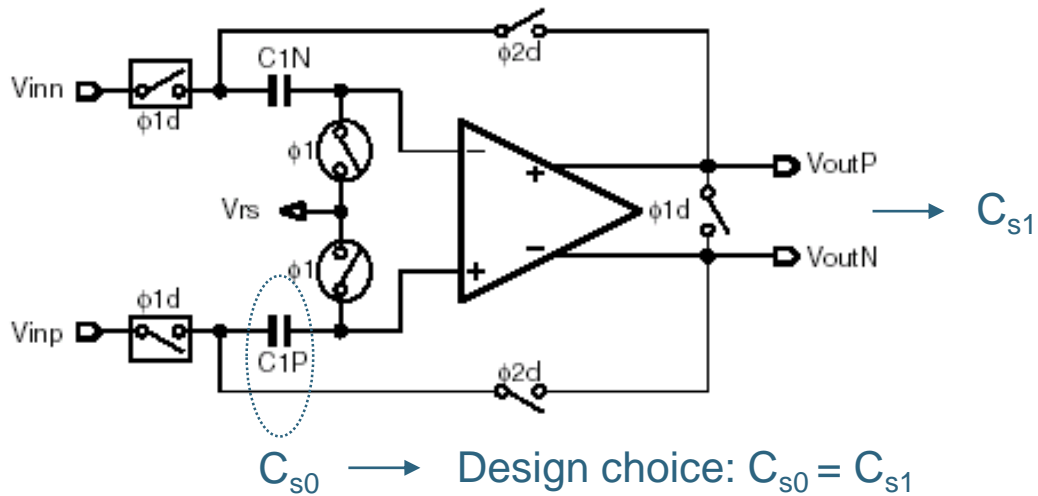


$$\beta = \frac{C_{s0}}{C_{s0} + C_{gs1}} \approx \frac{1}{2}$$

$$C_{Ltot} = C_{S1} + \left(1 - \frac{1}{2}\right) \frac{C_{S0}}{2}$$

From sample phase (ϕ_1)

$$\overline{V_{od,0}^2} = \overline{V_{id,0}^2} = 18 \frac{kT}{C_{s1} + C_{s0} / 4} + \frac{kT}{C_{s0}} \cong 16 \frac{kT}{C_{s1}}$$

Stage 1 Noise

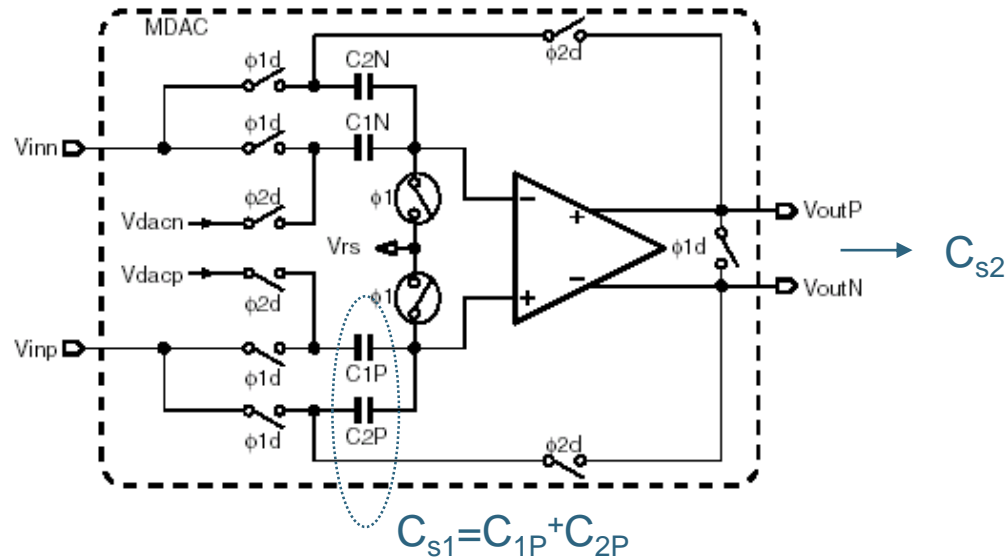

$$\beta = \frac{C_{s1} / 2}{C_{s1} + C_{gs1}} \cong \frac{1}{3}$$

$$\overline{V_{od,1}^2} = 18 \frac{kT}{C_{s2} + C_{s1} / 3}$$

$$C_{Ltot} = C_{s2} + \left(1 - \frac{1}{3}\right) \frac{C_{s1}}{2}$$

$$\overline{V_{id,1}^2} = \frac{18}{2^2} \frac{kT}{C_{s2} + C_{s1} / 3}$$



Noise Budgeting

- Total input referred noise budget, assuming $V_{FS,diff}=1V$
 - $N_{thermal} = N_{quant} = LSB^2/12 = (1V/2^{10})^2/12 = (280\mu V_{rms})^2$
- Reasonable "first cut" partitioning of input referred noise
 - SHA $\rightarrow 1/2$
 - Stage 1 $\rightarrow 1/4$
 - All remaining stages $\rightarrow 1/4$

$$\overline{V_{id,0}^2} = 16 \frac{kT}{C_{s1}} = \frac{1}{2} (280\mu V_{rms})^2 \Rightarrow C_{s1} = 1.66pF$$

$$\overline{V_{id,1}^2} = \frac{9}{2} \frac{kT}{C_{s2} + C_{s1}/3} = \frac{1}{4} (280\mu V_{rms})^2 \Rightarrow C_{s2} = 0.38pF$$

Capacitor Sizes

C_{s0}	1.66pF	
C_{s1}	1.66pF	
C_{s2}	0.38pF	 /2
C_{s3}	190fF	 /2
C_{s4}	85fF	 /2
C_{s5}	42.fF (minimum)	
...	...	
C_{s10}	42.fF (minimum)	

- Now refine these numbers using simulation and Excel spreadsheet
 - Iterate over assumptions/design choices to optimize design

Reality Check

[Honda 2007]

STAGE	C_s [pF]	Power [mW]
S/H	2.0	3.5
STAGE1	1.0	3.0
STAGE2	0.5	2.0
STAGE3	0.3	2.0
STAGE4	0.3	1.8
STAGE5	0.16	1.8
STAGE6	0.16	1.5
STAGE7-10	0.1	1.5
Others [Bias circuits, Clock gen.]		5.0
Total static power		26.6

Technology	90nm digital CMOS
Supply voltage	1.0 V
Resolution	10 bits
Sampling rate	100 MSample/s
Full scale analog input	0.8 V _{pp}
Maximum DNL	-0.7/+0.3 LSB
Maximum INL	-0.6/+0.7 LSB
SNDR ($F_{in} \cong 10\text{MHz}$)	55.3dB
SFDR ($F_{in} \cong 10\text{MHz}$)	71.5dB
Total power consumption	33mW
Packaging	Chip-on-board
Active area	1.3mm×3.1mm


- Not too far off from a practical design...

EE 240C



Analog-Digital Interface Integrated Circuits

Pipeline Optimizations

Amplifier Sharing (1)

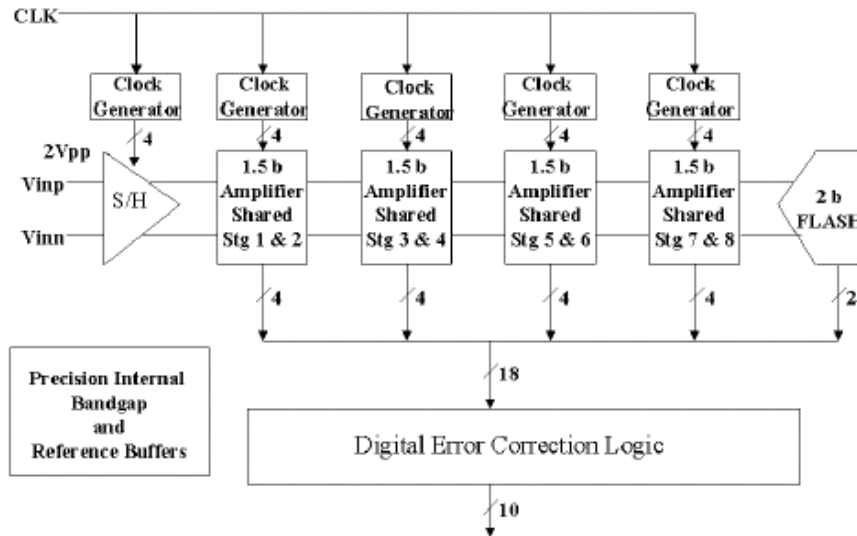


[Min 2003]

  

- Limited power savings because amplifiers have different specs

Amplifier Sharing (2)

[Kurose 2006]

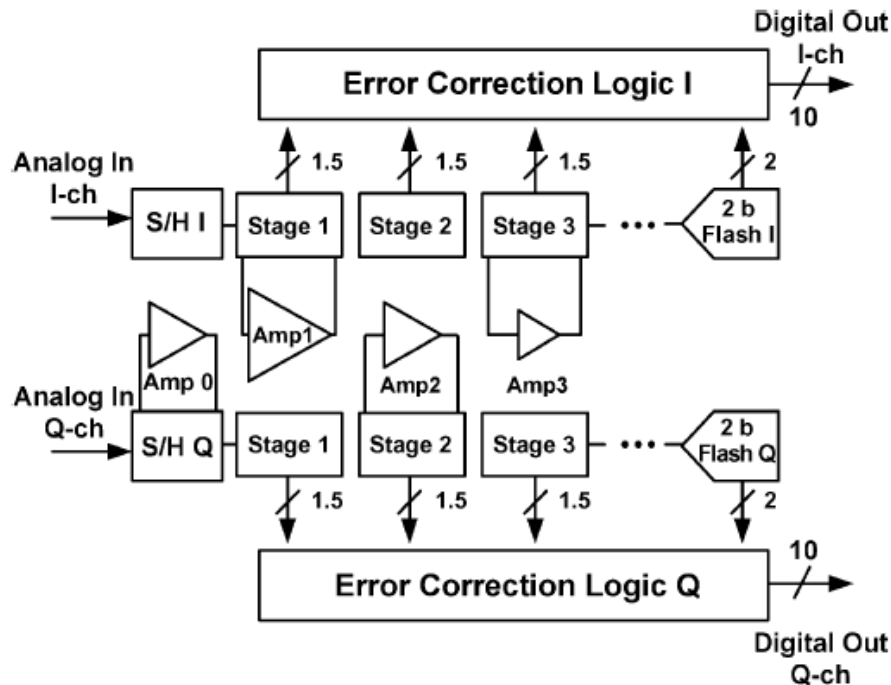


Technology	90-nm 1-P 7-M CMOS
Supply Voltage	1.2 V
Resolution	10 bit
Sampling Rate	200 MSPS
Full Scale	0.8V _{p-p}
DNL	+0.66/-0.61 LSB
INL	+0.90/-1.00 LSB
SFDR	66.5 dB
SNR	57.4 dB@Fin=9.9 MHz 55.6 dB@Fin=89.9 MHz
SNDR	54.4 dB@Fin=9.9 MHz 53.6 dB@Fin=89.9 MHz
ENOB	8.7 bit@Fin=9.9 MHz 8.6 bit@Fin=89.9 MHz
I/Q Isolation	>59 dB
Area	1.8 mm × 1.4 mm (2 ch)
Power	54.6 mW/ch

- Sharing of amplifiers is most efficiently done in a pair of converters that process I/Q signals

SHA-Less Architectures (1)


- Motivation
 - SHA can burn up to 1/3 of total ADC power
- Removing front-end SHA creates acquisition timing mismatch issue between first stage MDAC & Flash

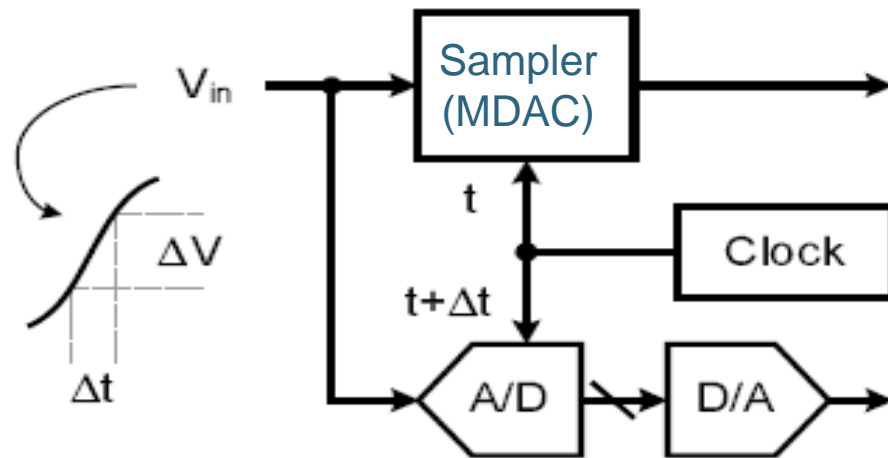

[Chiu 2004]

SHA-Less Architectures (2)

- Strategies
 - Use first stage with large redundancy; this can help absorb fairly large skew errors
 - Try to match sampling sub-ADC/MDAC networks
 - Bandwidth and clock timing

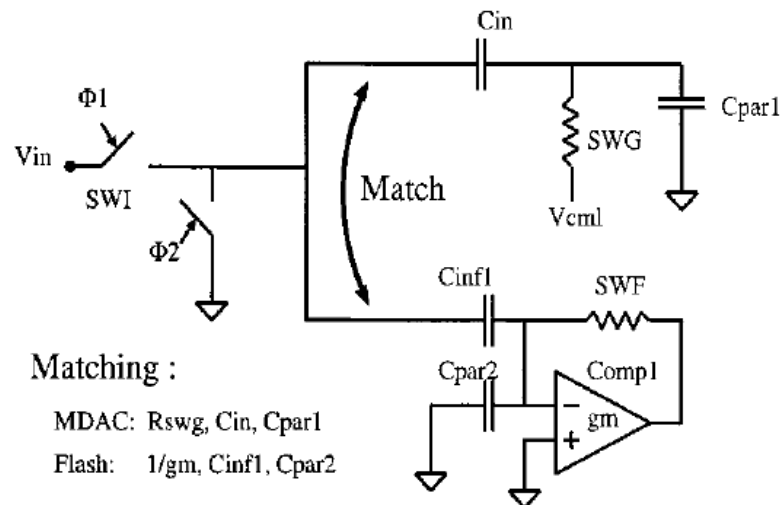

[Mehr 2000]

Fig. 5. Matching input networks for the MDAC and the flash comparators.

Selected References (1)

- General

- S. Kawahito, "Low-Power Design of Pipeline A/D Converters," Proc. CICC, pp. 505–512, Sep. 2006.

- Redundancy & Calibration

- S. H. Lewis et al., "A 10-b 20-Msample/s analog-to-digital converter," IEEE JSSC, pp. 351–358, Mar. 1992.
- A. N. Karanicolas et al. "A 15-b 1-Msample/s digitally self-calibrated pipeline ADC," IEEE J. Of Solid-State Circuits, pp. 1207–1215, Dec. 1993.
- E. G. Soenen et al., "An architecture and an algorithm for fully digital correction of monolithic pipelined ADCs," IEEE TCAS II, pp. 143–153, Mar. 1995.
- I. E. Opris et al., "A single-ended 12-bit 20 MSample/s self-calibrating pipeline A/D converter," IEEE JSSC, pp. 1898–1903, Dec. 1998.
- L. Singer et al., "A 12 b 65 MSample/s CMOS ADC with 82 dB SFDR at 120 MHz," ISSCC Dig. Techn. Papers, pp. 38–39, Feb. 2000.
- I. Mehr et al., "A 55-mW, 10-bit, 40-Msample/s Nyquist-rate CMOS ADC," IEEE JSSC, pp. 318–325, Mar. 2000.
- J. Ming et al., "An 8-bit 80-Msample/s pipelined analog-to-digital converter with background calibration," IEEE JSSC, pp. 1489–1497, Oct. 2001.
- S.-Y. Chuang et al., "A Digitally Self-Calibrating 14-bit 10-MHz CMOS Pipelined A/D Converter," IEEE JSSC, pp. 674–683, Jun. 2002.
- J. Markus et al., "On the monotonicity and linearity of ideal radix-based A/D converters," IEEE Trans. Instr. and Measurement, pp. 2454–2457, Dec. 2005.

Selected References (2)

- Implementation

- T. Cho, "Low-Power Low-Voltage Analog-to-Digital Conversion Techniques using Pipelined Architectures, PhD Dissertation, UC Berkeley, 1995, <http://kabuki.eecs.berkeley.edu/~tcho/Thesis1.pdf>.
- L. A. Singer et al., "A 14-bit 10-MHz calibration-free CMOS pipelined A/D converter," VLSI Circuit Symposium, pp. 94-95, Jun. 1996.
- A. Abo, "Design for Reliability of Low-voltage, Switched-capacitor Circuits," PhD Dissertation, UC Berkeley, 1999, <http://kabuki.eecs.berkeley.edu/~abo/abothesis.pdf>.
- D. Kelly et al., "A 3V 340mW 14b 75MSPS CMOS ADC with 85dB SFDR at Nyquist," ISSCC Dig. Techn. Papers, pp. 134-135, Feb. 2001.
- A. Loloee, et. al, "A 12b 80-MSs Pipelined ADC Core with 190 mW Consumption from 3 V in 0.18-um, Digital CMOS", Proc. ESSCIRC, pp. 467-469, 2002
- B.-M. Min et al., "A 69-mW 10-bit 80-MSample/s Pipelined CMOS ADC," IEEE JSSC, pp. 2031-2039, Dec. 2003.
- Y. Chiu, et al., "A 14-b 12-MS/s CMOS pipeline ADC with over 100-dB SFDR," IEEE JSSC, pp. 2139-2151, Dec. 2004.
- S. Limotyrakis et al., "A 150-MS/s 8-b 71-mW CMOS time-interleaved ADC," IEEE JSSC, pp. 1057-1067, May 2005.
- T. N. Andersen et al., "A Cost-Efficient High-Speed 12-bit Pipeline ADC in 0.18-um Digital CMOS," IEEE JSSC, pp. 1506-1513, Jul 2005.

Selected References (3)

- P. Bogner et al., "A 14b 100MS/s digitally self-calibrated pipelined ADC in 0.13 μ m CMOS," ISSCC Dig. Techn. Papers, pp. 832–833, Feb. 2006.
- D. Kurose et al., "55-mW 200-MSPS 10-bit Pipeline ADCs for Wireless Receivers," IEEE JSSC, pp. 1589–1595, Jul. 2006.
- S. Bardsley et al., "A 100-dB SFDR 80-MSPS 14-Bit 0.35 μ m BiCMOS Pipeline ADC," IEEE JSSC, pp. 2144–2153, Sep. 2006.
- A. M. A. Ali et al., "A 14-bit 125 MS/s IF/RF Sampling Pipelined ADC With 100 dB SFDR and 50 fs Jitter," IEEE JSSC, pp. 1846–1855, Aug. 2006.
- S. K. Gupta, "A 1-GS/s 11-bit ADC With 55-dB SNDR, 250-mW Power Realized by a High Bandwidth Scalable Time-Interleaved Architecture," IEEE JSSC, 2650–2657, Dec. 2006.
- M. Yoshioka et al., "A 0.8V 10b 80MS/s 6.5mW Pipelined ADC with Regulated Overdrive Voltage Biasing," ISSCC Dig. Techn. Papers, pp. 452–453, Feb. 2007.
- Y.-D. Jeon et al., "A 4.7mW 0.32mm² 10b 30MS/s Pipelined ADC Without a Front-End S/H in 90nm CMOS," ISSCC Dig. Techn. Papers, pp. 456–457, Feb. 2007.
- K.-H. Lee et al., "Calibration-free 14b 70MS/s 0.13 μ m CMOS pipeline A/D converters based on highmatching 3D symmetric capacitors," Electronics Letters, pp. 35–36, Mar. 15, 2007.
- K. Honda et al., "A Low-Power Low-Voltage 10-bit 100-MSample/s Pipeline A/D Converter Using Capacitance Coupling Techniques," IEEE JSSC, pp. 757–765, Apr. 2007.

Selected References (4)

- Per-Stage Resolution and Stage Scaling
 - D. W. Cline, "Noise, Speed, and Power Tradeoffs in Pipelined Analog to Digital Converters", PhD Dissertation, UC Berkeley, November, 1995, <http://kabuki.eecs.berkeley.edu/~cline/thesis/thesis.pdf>.
 - D. W. Cline et al., "A power optimized 13-b 5 MSamples/s pipelined analog-to-digital converter in 1.2 μ m CMOS," IEEE JSSC, Mar. 1996
 - Y. Chiu, "High-Performance Pipeline A/D Converter Design in Deep-Submicron CMOS," PhD Dissertation, UC Berkeley, 2004.
 - H. Ishii et al., "A 1.0 V 40mW 10b 100MS/s pipeline ADC in 90nm CMOS," Proc. CICC, pp. 395–398, Sep. 2005.
- OTA Design, Noise
 - B. E. Boser, "Analog Circuit Design with Submicron Transistors," Presentation at IEEE Santa Clara Valley, May 19, 2005, <http://www.ewh.ieee.org/r6/scv/ssc/May1905.htm>
 - B. Murmann, EE315A Course Material, <http://ccnet.stanford.edu/cgi-bin/handouts.cgi?cc=ee315a>
 - R. Schreier et al., "Design-oriented estimation of thermal noise in switched-capacitor circuits," IEEE TCAS I, pp. 2358–2368, Nov. 2005.

Selected References (5)



- Capacitor Matching Data
 - C. H. Diaz et al., "CMOS technology for MS/Rf SoC," IEEE Trans. Electron Devices, pp. 557–566, Mar. 2003.
 - A. Verma et al., "Frequency-Based Measurement of Mismatches Between Small Capacitors," Proc. CICC, pp. 481–484, Sep. 2006.
- Reference Generator
 - T. L. Brooks et al., "A low-power differential CMOS bandgap reference," ISSCC Dig. Techn. Papers, pp. 248–249, Feb. 1994.
- Research
 - B. Murmann et al., "A 12-bit 75-MS/s Pipelined ADC using Open-Loop Residue Amplification," IEEE JSSC, pp. 2040–2050, Dec. 2003.
 - J. Fiorenza et al., "Comparator-Based Switched-Capacitor Circuits for Scaled CMOS Technologies," IEEE JSSC, pp. 2658–2668, Dec. 2006.
 - E. Iroaga et al. "A 12b, 75MS/s Pipelined ADC Using Incomplete Settling," IEEE JSSC, pp. 748–756, Apr. 2007.
 - J. Hu, N. Dolev and B. Murmann, "A 9.4-bit, 50-MS/s, 1.44-mW Pipelined ADC using Dynamic Residue Amplification," VLSI Circuits Symposium, June 2008.

EE 240C

Analog-Digital Interface Integrated Circuits

Time Interleaved ADCs


Time Interleaved ADCs

 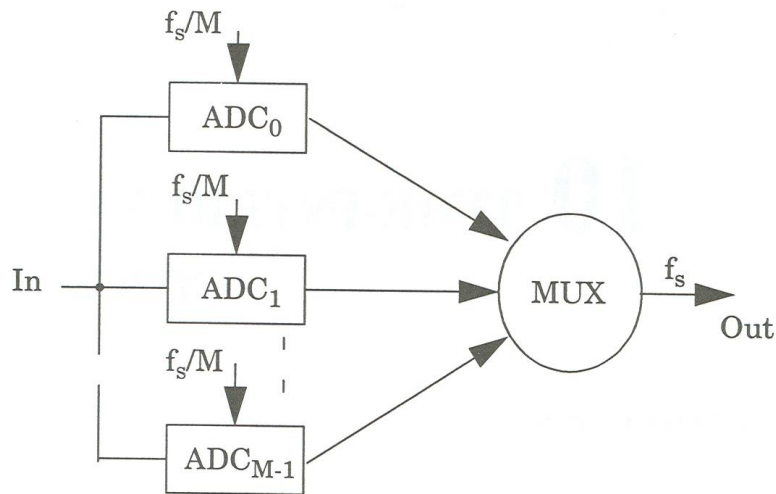

- Idea: Run M ADCs in parallel to obtain an aggregate throughput rate of $M \cdot f_s$
- Catch: Each ADC still needs an acquisition bandwidth that is commensurate with maximum input frequency


Example (1)

[Draxelmayr, ISSCC 2004]

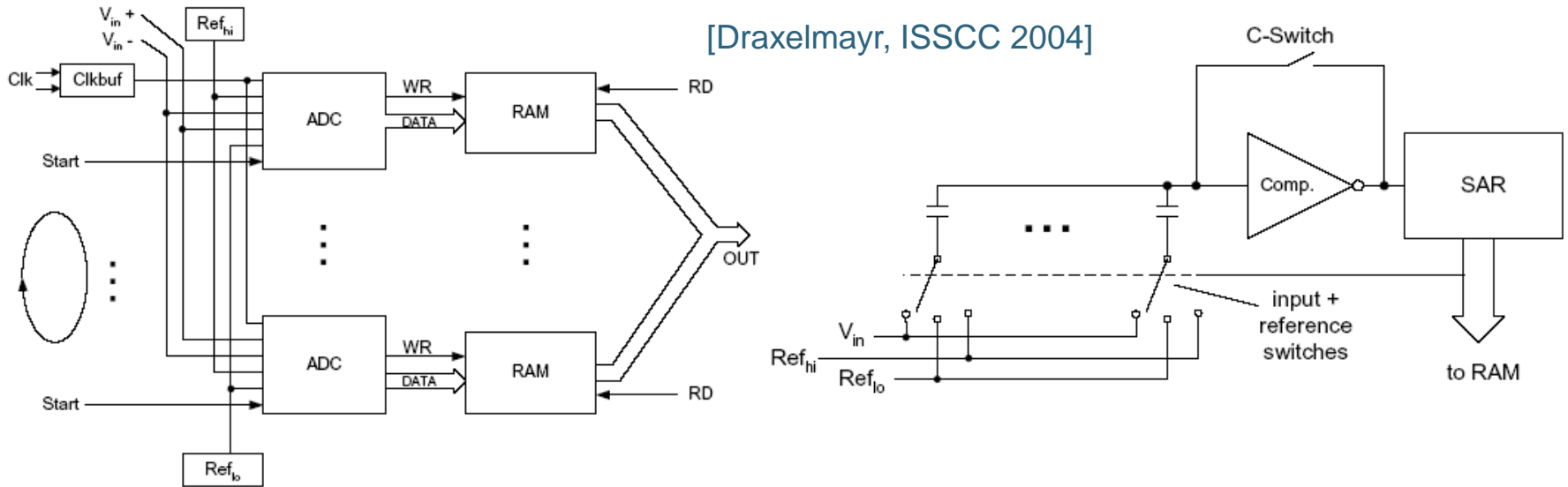


- Idea
 - Interleave several "slow" SAR ADCs to get high throughput while maintaining low complexity and good power efficiency
- Array consists of eight 6-bit ADCs, each running at 75 MS/s
 - 8 cycles per ADC (2 for acquisition, 6 for conversion)
 - Aggregate throughput is 600MS/s, power=10mW in 90-nm CMOS technology


Example (2)

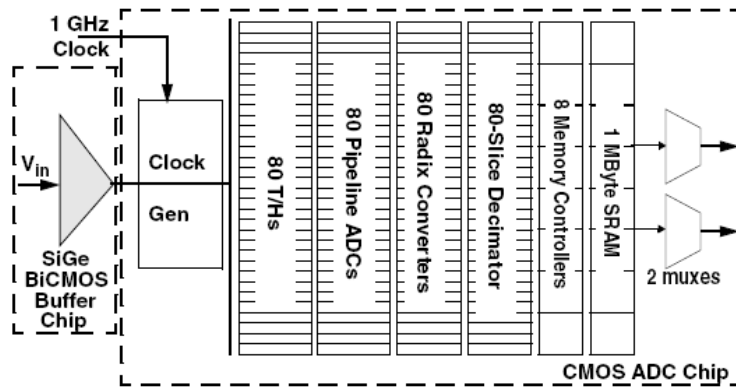

[Poulton, ISSCC 2003]

 


Sample Rate	20 GSA/s	
Resolution	8 bits	
INL		
Intrinsic	± 1.7 LSBs	
With linearity correction	± 0.4 LSBs	
DNL	± 0.3 LSBs	
Bandwidth	6.6 GHz	
Accuracy		
@ 500 MHz input	6.5 effective bits	
@ 6 GHz input	4.6 effective bits	
Jitter	0.7 ps rms	
Input Range	0.25 V _{pk} differential	
	Buffer Chip	ADC Chip
Input Capacitance	0.2 pF	4 pF
Power	1 W	9 W
Chip Size	1.2 x 2.6 mm	14 x 14 mm
Technology	40-GHz SiGe BiCMOS	0.18- μ m CMOS
Transistors	1000	50M
Package	438-ball BGA	

 


Issues with Time Interleaving

- Offset mismatch → easy to calibrate
 - Each channel will have a different offset
 - Output will contain a periodic error sequence that manifest itself as spurs in the output spectrum
- Gain mismatch → easy to calibrate
 - Channels may also have slightly different gain
 - Results in amplitude modulation
- Phase skew / Timing mismatch
 - Hard to guarantee precise phase relationship between individual channel clocks
 - Results in phase modulation (similar to aperture uncertainty)
- Bandwidth mismatch
 - Results in phase and amplitude modulation
- Solutions
 - "Careful design"
 - Analog or digital calibration (See e.g. [Jamal, JSSC 12/2002])

Tones due to channel mismatch

 

 M channels with
offset differences
→ tones at $m f_s/M$
for $m = 0, 1, \dots, M-1$



M channels with
gain or timing differences
→ tones at $m f_s/M \pm f_{in}$

[S. Louwsma, E. van Tuijl, and B. Nauta,
Time-interleaved Analog-to-Digital Converters
Springer Netherlands, 2011]

-
- Mismatch \rightarrow periodic with period $M T_s$
 \rightarrow frequency domain: tones at multiples of f_s / M


- Offset mismatch: additive

$$x[n] + \text{offset}[n] \rightarrow X(f) + \sum O_m \left(f - m \frac{f_s}{M} \right)$$

- Gain mismatch: multiplicative in time domain

$$x[n] (1 + \text{gain}[n]) \rightarrow X(f) \star \left(\delta(f) + \sum G_m \left(f - m \frac{f_s}{M} \right) \right)$$

Impact of Offset Mismatch

 

[Gustavsson, p.262]

$$\text{SNDR}_{\text{offset}} \leq 10 \log_{10} \frac{M}{M-1} \frac{A^2}{2\sigma_{\text{offset}}^2}$$


M: interleaving factor

A: amplitude

σ_{offset} : offset std dev

- E.g. FS=1V, $\sigma_{OS}=1\text{mV} \Rightarrow \text{ENOB} \sim 9\text{bits!}$

Impact of Gain Mismatch

 

[Gustavsson, p.266]

$$\text{SNDR}_{\text{gain}} \leq 10 \log_{10} \frac{M}{M-1} \frac{G^2}{\sigma_G^2}$$


M: interleaving factor

G: gain

σ_{offset} : gain std dev


- E.g. $\sigma_{\text{Gain}} = 0.1\% \Rightarrow \text{ENOB} \sim 10\text{bits}$

Impact of Phase Skew / Timing Mismatch

 

- Above chart is for $M=4$ channels
- E.g. $f_{in}=100\text{MHz}$, phase skew=3ps \Rightarrow ENOB~9bits!

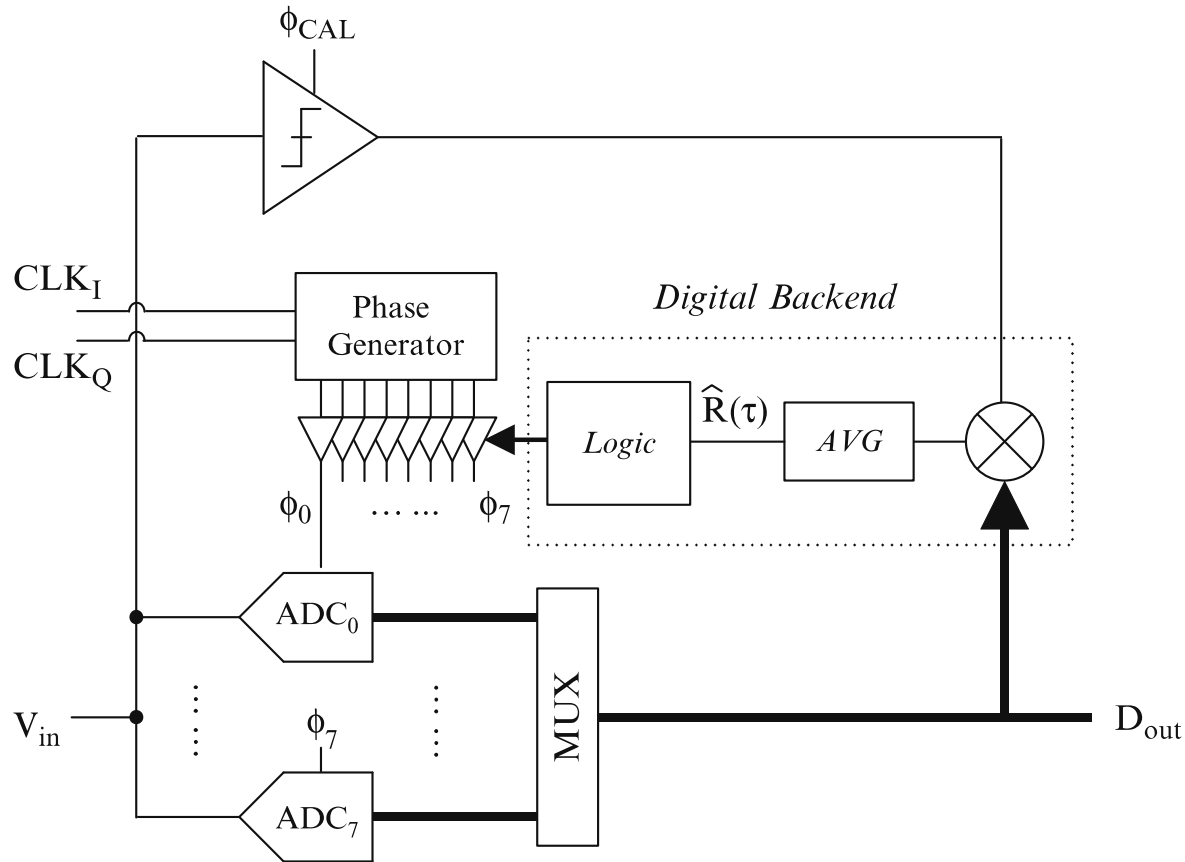Example of Background Calibration for Timing Mismatch



[M. El-Chammas and B. Murmann,
Background Calibration of Time-Interleaved Data Converters.
Springer-Verlag New York, 2012]