



**IEEE SOLID-STATE  
CIRCUITS SOCIETY**  
Where ICs are in IEEE

# Solid-State Circuits Society

“Where ICs are in the IEEE”



# Professional Organization

- ▶ 10,000 members
- ▶ 70+ chapters located worldwide
- ▶ Foster information exchange in electronics
  - Distinguished Lectures
  - Online tutorials
  - International and regional conferences
  - Journals & magazines
- ▶ Part of IEEE with 400,000 members



**IEEE SOLID-STATE  
CIRCUITS SOCIETY**  
Where ICs are in IEEE

## Publications & Conferences


### Journal of Solid-State Circuits (JSSC)

- #1 technical source for circuits
- Most downloaded IEEE journal articles
- Top cited reference in US Patent applications


 
### Solid-State Circuits Magazine

- Discusses historical milestones, trends and future developments
- Articles by leaders from industry and academia in a tutorial and editorial style



### International and Regional Conferences

- 4 International Sponsored Conferences
- Technically co-sponsored conferences







**IEEE SOLID-STATE  
CIRCUITS SOCIETY**  
Where ICs are in IEEE

## Chapter & DL Events



Swedish SOC Conference (May 2011)



Annual SSCS DL Tour



Individual DL  
Presentations

SSCS-Italy: International  
Analog VLSI Workshop  
(September 2011)





# Why join IEEE and SSCS?

## Knowledge ...

staying current with the fast changing world of solid-state circuit technology

## Community ...

local and global activities, unparalleled networking opportunities, chapter activities, electing IEEE SSCS leadership

## Profession ...

empowering members to build and own their careers, mentoring, making the world a better place

## Recognition ...

Best Paper Awards, IEEE Fellow & Field Awards,  
Student Travel Grants & Pre-doctoral Achievement Award

...



## Getting Involved

- ▶ Organize chapter events
- ▶ Participate in & organize conferences
- ▶ As an author
- ▶ As a reviewer
- ▶ Compete in a student design contest
- ▶ Nominate senior members & fellows




# Energy Limits in A/D Converters

August 29, 2012

Boris Murmann

 [murmann@stanford.edu](mailto:murmann@stanford.edu)



# A/D Converter ca. 1954

◆ 19" × 15" × 26"

◆ 150 lbs

◆ 500W

◆ \$8,500.00

$$P/f_s = 500W/50kS/s = 10mJ$$



Courtesy,  
Analogic Corporation  
8 Centennial Drive  
Peabody, MA 01960


<http://www.analogic.com>

*Figure 4.3: 1954 "DATRAC" 11-bit, 50-kSPS SAR ADC  
Designed by Bernard M. Gordon at EPSCO*

[http://www.analog.com/library/analogDialogue/archives/39-06/data\\_conversion\\_handbook.html](http://www.analog.com/library/analogDialogue/archives/39-06/data_conversion_handbook.html)




# ADC Landscape in 2004

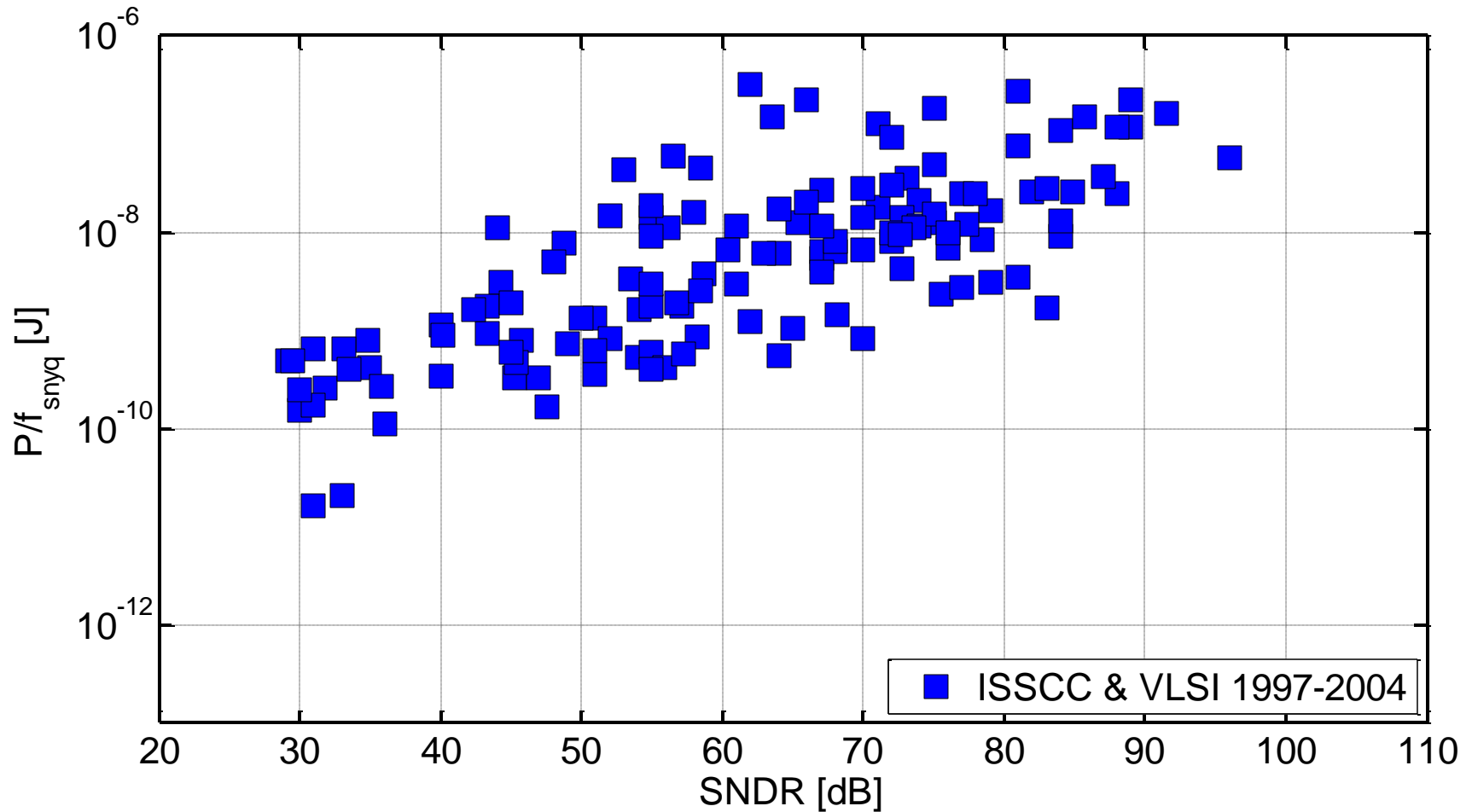

B. Murmann, "ADC Performance Survey 1997-2012," [Online]. Available: <http://www.stanford.edu/~murmman/adcsurvey.html>

# ADC Landscape in 2012

 

B. Murmann, "ADC Performance Survey 1997-2012," [Online]. Available: <http://www.stanford.edu/~murmman/adcsurvey.html>

# Observation


- **ADCs have become substantially “greener” over the years**
- **Questions**
  - **How much more improvement can we hope for?**
  - **What are the trends and limits for today’s popular architectures?**
  - **Can we benefit from further process technology scaling?**



# Outline

- **Fundamental limit**
- **General trend analysis**
- **Architecture-specific analysis**
  - **Flash**
  - **Pipeline**
  - **SAR**
  - **Delta-Sigma**
- **Summary**

# Fundamental Limit

 

$$SNR = \frac{\frac{1}{2} \left( \frac{V_{FS}}{2} \right)^2}{\frac{kT}{C}} \frac{f_s}{f_{snyq}} \cdot \frac{1}{OSR}$$


$$P_{min} = CV_{FS} f_s \cdot V_{DD}$$

$$V_{DD} = V_{FS}$$

$$E_{min} = \frac{P_{min}}{f_{snyq}} = 8kT \cdot SNR$$


[Hosticka, Proc. IEEE 1985; Vittoz, ISCAS 1990]

# ADC Landscape in 2004

 




# ADC Landscape in 2012

 

# Normalized Plot

 

# Aside: Figure of Merit Considerations

- There are (at least) two widely used ADC figures of merit (FOM) used in literature

- **Walden FOM**

- Energy increases 2x per bit (ENOB)
- Empirical

$$\text{FOM} = \frac{\text{Power}}{2^{\text{ENOB}} \cdot f_{\text{snyq}}}$$


- **Schreier FOM**

- Energy increases 4x per bit (DR)
- Thermal
- Ignores distortion

$$\text{FOM} = \text{DR}(\text{dB}) + 10 \log \left( \frac{\text{BW}}{P} \right)$$




# FOM Lines

 


- Best to use thermal FOM for designs above 60dB

# Walden FOM vs. Speed

 


- FOM “corner” around 100...300MHz



# Schreier FOM vs. Speed

 

# Energy by Architecture

 


# Flash ADC

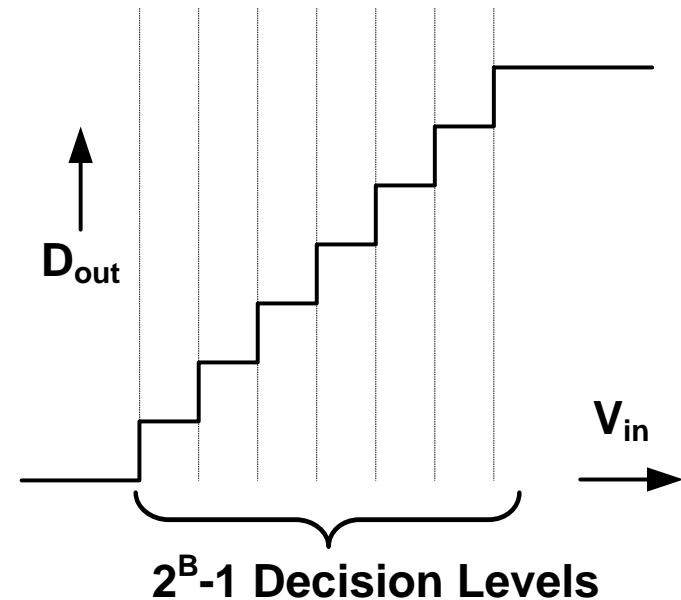 

- **High Speed**
  - Limited by single comparator plus encoding logic
- **High complexity, high input capacitance**
  - Typically use for resolutions up to 6 bits
 
# Encoder


- Assume a Wallace encoder (“ones counter”)
- Uses  $\sim 2^B - B$  full adders, equivalent to  $\sim 5 \cdot (2^B - B)$  gates



$$E_{\text{enc}} \cong 5 \cdot (2^B - B) \cdot E_{\text{gate}}$$



# Matching-Limited Comparator

 

**Simple Dynamic Latch**

Assuming  $C_{\text{cmin}} = 5\text{fF}$   
for wires, clocking, etc.

$$\sigma_{\text{VOS}}^2 \cong \frac{A_{\text{VT}}^2}{\text{WL}} = A_{\text{VT}}^2 \frac{C_{\text{c}}}{C_{\text{ox}}}$$

**Offset**

$$C_{\text{c}} = \frac{A_{\text{VT}}^2 C_{\text{ox}}}{\sigma_{\text{VOS}}^2} + C_{\text{cmin}}$$

**Required  
capacitance**

$$3\sigma_{\text{VOS}} = \frac{1}{4} \frac{V_{\text{inpp}}}{2^B}$$

**Confidence  
interval**

$$B \cong \frac{\text{SNR}[\text{dB}] + 3}{6}$$


**3dB penalty  
accounts for  
“DNL noise”**

$$E_{\text{comp}} \cong \left( 144 \cdot 2^{2B} \cdot \underbrace{C_{\text{ox}} A_{\text{VT}}^2}_{\text{Matching Energy}} \cdot \frac{V_{\text{DD}}^2}{V_{\text{inpp}}^2} + C_{\text{cmin}} V_{\text{DD}}^2 \right) \cdot (2^B - 1)$$

# Typical Process Parameters

Process [nm]	$A_{VT}$ [mV- $\mu$ m]	$C_{ox}$ [fF/ $\mu$ m <sup>2</sup> ]	$A_{VT}^2 C_{ox} / kT$	$E_{gate}$ [fJ]
250	8	9	139	80
130	4	14	54	10
65	3	17	37	3
32	1.5	43	23	1.5


# Comparison to State-of-the-Art

 


[1] Van der Plas, ISSCC 2006  
 [2] El-Chammas, VLSI 2010  
 [3] Verbruggen, VLSI 2008

[4] Daly, ISSCC 2008  
 [5] Chen, VLSI 2008  
 [6] Geelen, ISSCC 2001 (!)

# Impact of Scaling

 


# Impact of Calibration (1)

 

- Important to realize that only comparator power reduces

$$3\sigma_{\text{vos}} = \frac{1}{4} \frac{V_{\text{inpp}}}{2(B - B_{\text{cal}})} \quad B_{\text{cal}} \approx 3$$


# Impact of Calibration (2)

 

# Ways to Approach $E_{\min}$ (1)

- **Offset calibrate each comparator**
  - Using trim-DACs

[El-Chammas, VLSI 2010]

 





# Ways to Approach $E_{\min}$ (2)

- Find ways to reduce clock power
- Example: resonant clocking


[Ma, ESSCIRC 2011]

 


(54% below  $CV^2$ )

 
 
# Raison D'Être for Architectures Other than Flash...



# Pipeline ADC

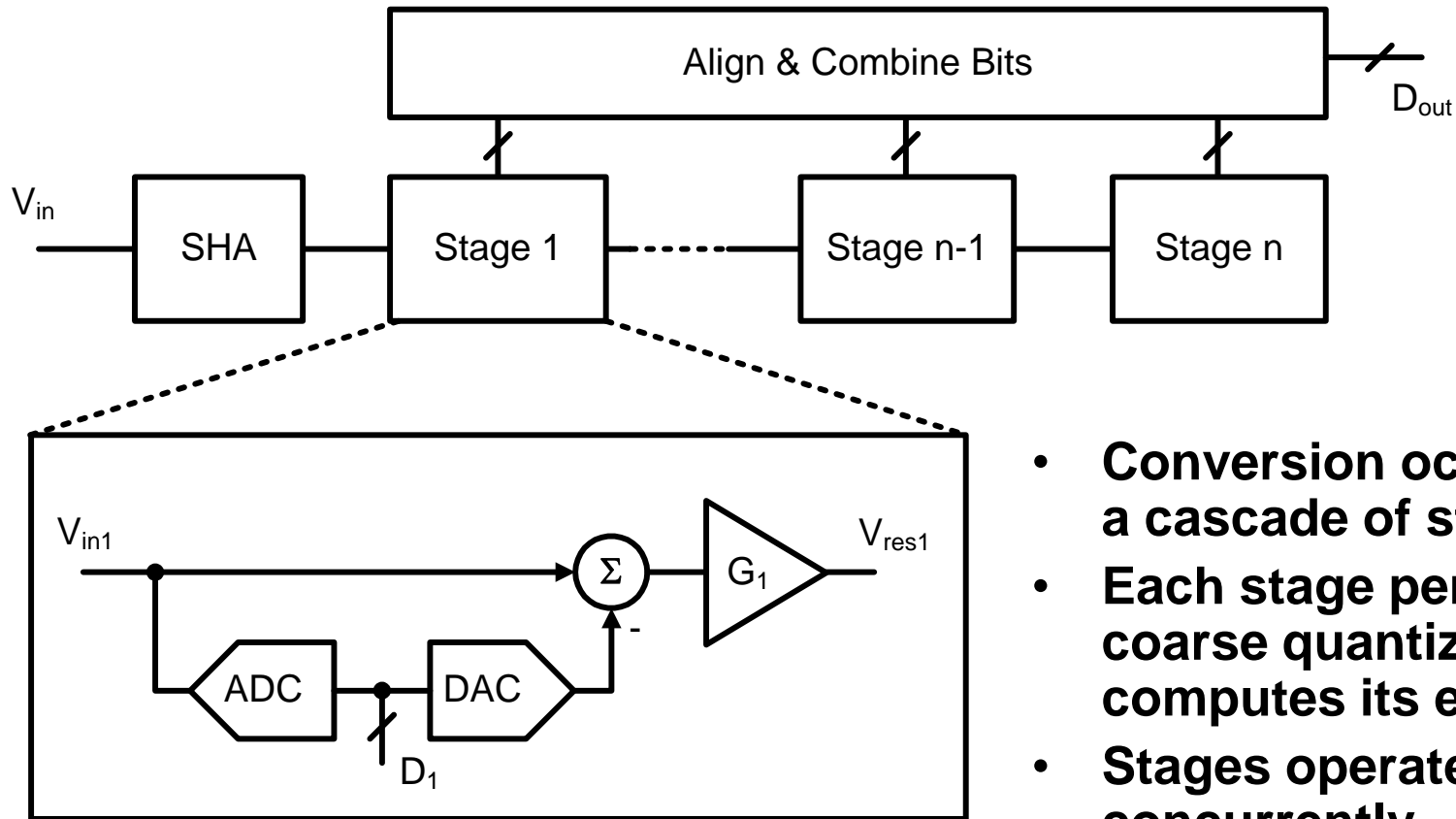


- **Conversion occurs along a cascade of stages**
- **Each stage performs a coarse quantization and computes its error ( $V_{res}$ )**
- **Stages operate concurrently**
  - Throughput is set by the speed of one single stage

# Pipelining – A Very Old Idea




U.S. DEPARTMENT OF THE INTERIOR, NATIONAL PARK SERVICE, EDISON NATIONAL HISTORIC SITE

# Typical Stage Implementation

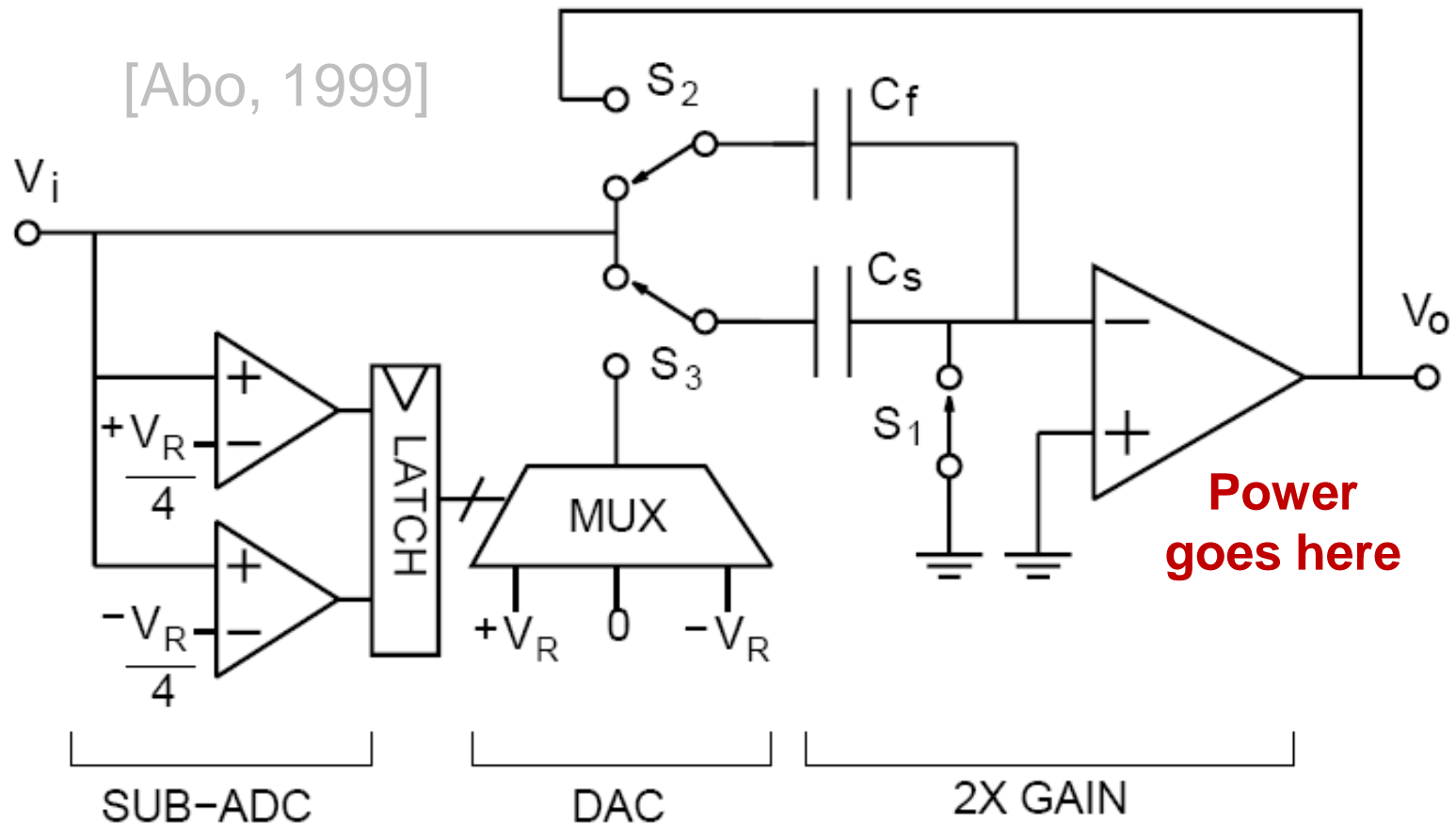
 
# Simplified Model for Energy Calculation




- **Considering the most basic case**
  - Stage gain = 2  $\rightarrow$  1 bit resolution per stage
  - Capacitances scaled down by a factor of two from stage to stage (first order optimum)
  - No front-end track-and-hold
  - Neglect comparator energy

# Simplified Gain Stage Model
 
## Feedback factor

$$\beta = \frac{\frac{C}{2}}{C + \frac{C}{2}} = \frac{1}{3}$$



$$C_{\text{eff}} = \frac{C}{2}(1 - \beta) + \frac{C}{2} = \frac{5}{6}C$$

Effective load capacitance

## Assumptions

Closed-loop gain = 2

Infinite transistor  $f_T$  ( $C_{gs}=0$ )

Thermal noise factor  $\gamma = 1$ ,  
no flicker noise

Bias device has same  
noise as amplifier device

Linear settling only (no  
slewing)

$$N_{\text{out}} = 2 \frac{1}{\beta} \frac{kT}{C_{\text{eff}}} = 6 \frac{kT}{C_{\text{eff}}} = 5 \frac{kT}{C}$$

Total integrated output noise



# Total Pipeline Noise

$$\begin{aligned} N_{\text{in,tot}} &= \underbrace{\frac{kT}{C} \left( 1 + \frac{1}{2} \right)}_{\text{First sampler}} + 5 \frac{kT}{C} \left\{ \frac{1}{2^2} + \frac{1}{\frac{1}{2} 4^2} + \frac{1}{\frac{1}{4} 8^2} + \dots \right\} \\ &= \frac{3}{2} \frac{kT}{C} + 5 \frac{kT}{C} \left\{ \frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \dots \right\} \\ &\cong 4 \frac{kT}{C} \end{aligned}$$

# Key Constraints

$$\text{SNR} \cong \frac{\frac{1}{2} \left( \frac{V_{\text{inpp}}}{2} \right)^2}{4 \frac{kT}{C}}$$

**Thermal noise  
sets C**

$$\tau = \frac{C_{\text{eff}}}{\beta g_m} = \frac{T_s / 2}{\ln \left( \frac{1}{\epsilon_d} \right)} \cong \frac{T_s / 2}{\ln(\sqrt{\text{SNR}})}$$

**Settling time  
sets  $g_m$**

$$P = V_{\text{DD}} \left( \frac{g_m}{I_D} \right)$$

**$g_m$  sets power**

# Pulling It All Together

$$E_{\text{pipe}} = 640 \cdot kT \cdot \text{SNDR} \cdot \overbrace{\ln(\sqrt{\text{SNDR}})}^{\text{Settling "Number of } \tau"} \cdot \underbrace{\left(\frac{V_{DD}}{V_{inpp}}\right)^2}_{\text{Supply utilization}} \cdot \frac{1}{V_{DD}} \cdot \frac{1}{\frac{g_m}{I_D}} \cdot \overbrace{\phantom{\frac{1}{V_{DD}}}}^{V_{DD} \text{ penalty}}$$

Excess noise  
 Non-unity feedback  
 factor

Transconductor  
 efficiency

- For SNDR = {60..80}dB,  $V_{DD}=1V$ ,  $g_m/I_D=1/(1.5kT/q)$ ,  $V_{inpp}=2/3V$ , the entire expression becomes

$$E_{\text{pipe}} \cong \{388...517\} \cdot kT \cdot \text{SNDR}$$

- For realistic numbers at low resolution, we must introduce a bound for minimum component sizes


# Energy Bound

- Assume that in each stage  $C_{\text{eff}} > C_{\text{effmin}} = 50\text{fF}$
- For  $n$  stages, detailed analysis shows that this leads to a minimum energy of

$$E_{\text{pipe,min}} = 2n \cdot C_{\text{eff min}} V_{\text{DD}} \frac{\ln(\sqrt{\text{SNDR}})}{\beta \left( \frac{g_m}{I_D} \right)}$$

- Adding this overhead to  $E_{\text{pipe}}$  gives the energy curve shown on the next slide

# Comparison to State-of-the-Art

 

[1] Verbruggen, ISSCC 2012

[2] Chu, VLSI 2010


[3] Lee, VLSI 2010

[4] Anthony, VLSI 2008

[5] Lee, ISSCC 2012

[6] Hershberg, ISSCC 2012


# Ways to Approach $E_{\min}$ (1)

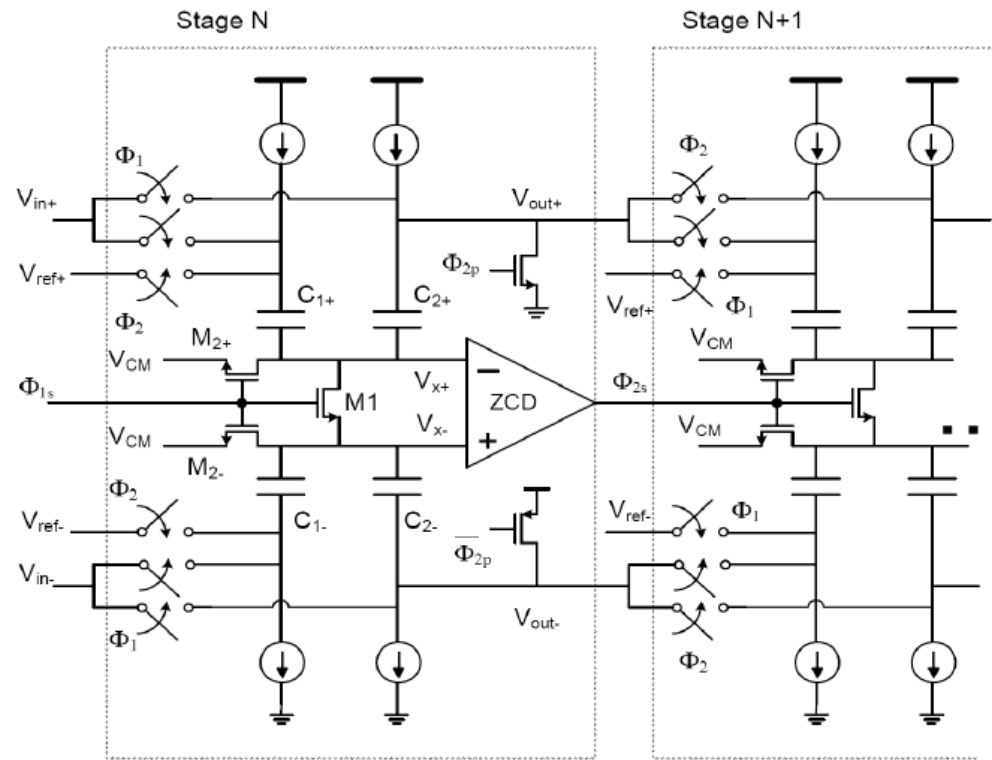

[Chu, VLSI 2010]

- **Comparator-based SC circuits replace op-amps with comparators**
- **Current ramp outputs**
  - **Essentially “class-B” (all charge goes to load)**

# Ways to Approach $E_{\min}$ (2)

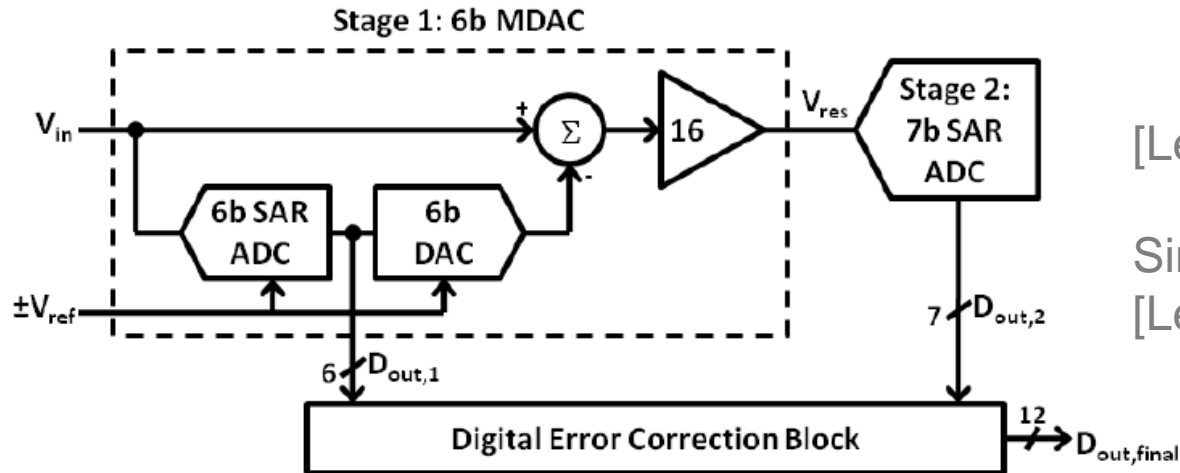


[Lee, VLSI 2010]

Similar:  
[Lee, ISSCC 2012]

- Use only one residue amplifier
- Build sub-ADCs using energy efficient SAR ADCs
- Essential idea: minimize overhead as much as possible




# Ways to Approach $E_{\min}$ (3)

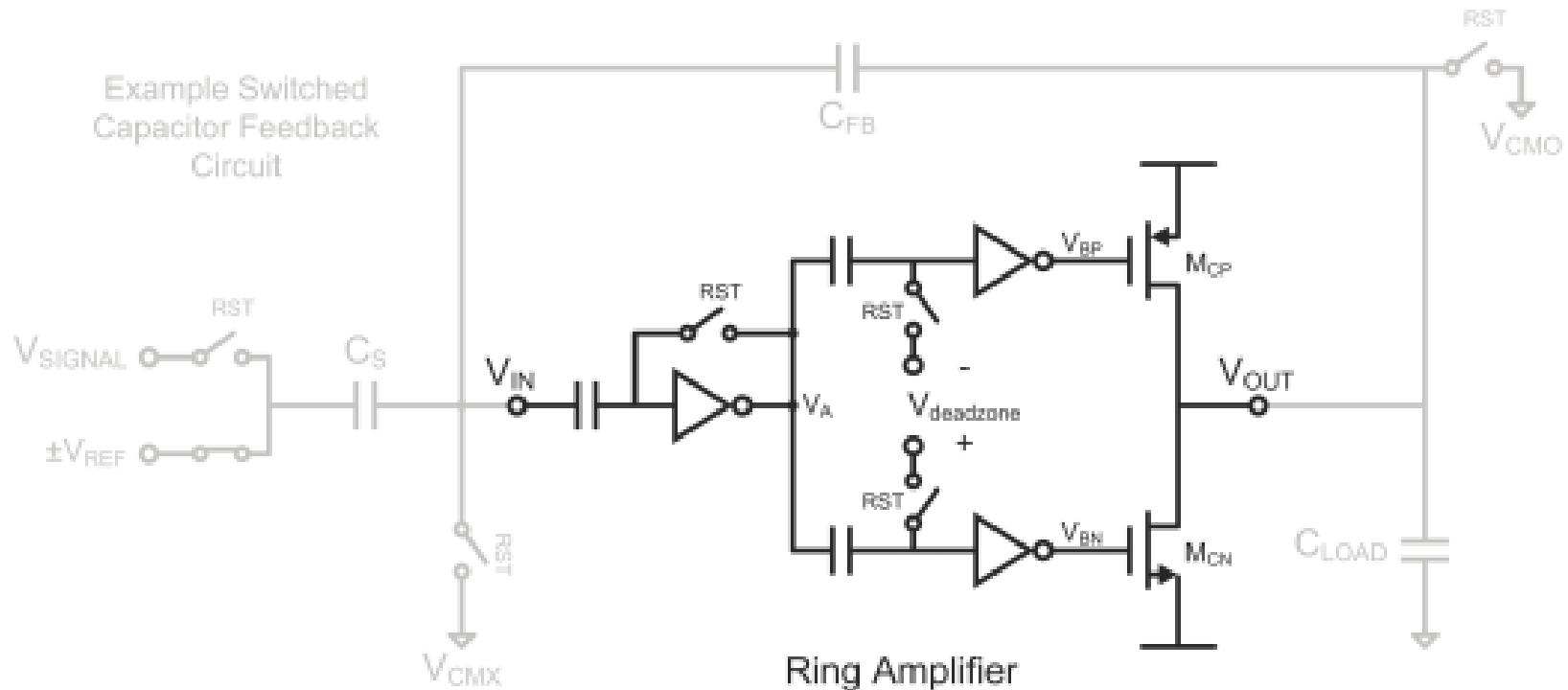

[Hershberg, ISSCC 2012]

- **Completely new idea: ring amplifier**
  - As in “ring oscillator”

# Ways to Approach $E_{\min}$ (4)

 

- **Class-C-like oscillations until charge transfer is complete**
  - Very energy efficient

# Expected Impact of Technology Scaling

- **Low resolution (SNDR ~ 40-60dB)**
  - Continue to benefit from scaling
  - Expect energy reductions due to reduced  $C_{\min}$  and reduction of  $CV^2$ -type contributors
- **High resolution (SNDR ~ 70dB+)**
  - It appears that future improvements will have to come from architectural innovation
  - Technology scaling will not help much and is in fact often perceived as a negative factor in noise limited designs (due to reduced  $V_{DD}$ )
    - Let's have a closer look at this...


# A Closer Look at the Impact of Technology Scaling

- As we have shown

$$E \propto \frac{1}{V_{DD}} \cdot \left( \frac{V_{DD}}{V_{inpp}} \right)^2 \cdot \frac{1}{\left( \frac{g_m}{I_D} \right)}$$


- Low  $V_{DD}$  hurts, indeed, but one should realize that this is not the only factor
- Designers have worked hard to maintain (if not improve)  $V_{inpp}/V_{DD}$  in low-voltage designs
- How about  $g_m/I_D$ ?

# $g_m/I_D$ Considerations (1)

 


- Largest value occurs in subthreshold  $\sim (1.5 \cdot kT/q)^{-1}$
- Range of  $g_m/I_D$  does not scale (much) with technology

# $g_m/I_D$ Considerations (2)

 


- $f_T$  is small in subthreshold region
- Must look at  $g_m/I_D$  for given  $f_T$  requirement to compare technologies

# $g_m/I_D$ Considerations (3)

 


- **Example**
  - $f_T = 30\text{GHz}$
  - 90nm:  $g_m/I_D = 18\text{S/A}$
  - 180nm:  $g_m/I_D = 9\text{S/A}$
- **For a given  $f_T$ , 90nm device takes less current to produce same  $g_m$** 
  - Helps mitigate, if not eliminate penalty due to lower  $V_{DD}$  (!)

# ADC Energy for 90nm and Below

 




# Successive Approximation Register ADC

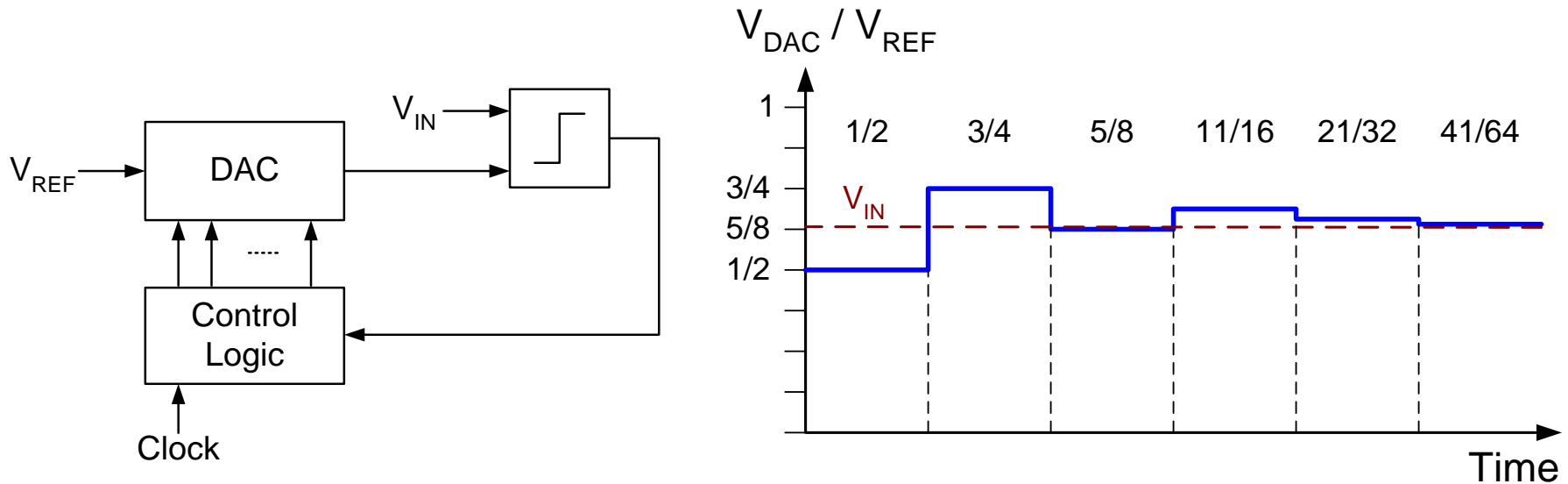

- Input is approximated via a binary search
- Relatively low complexity
- Moderate speed, since at least  $B+1$  clock cycles are needed for one conversion
- Precision is determined by DAC and comparator

# Classical Implementation

 

[McCreary, JSSC 12/1975]


$$E_{logic} \cong 8 \frac{\text{gates}}{\text{bit}} \cdot \frac{2fJ}{\text{gate}} \cdot B$$

(somewhat optimistic)

# DAC Energy

- Is a strong function of the switching scheme
- Excluding adiabatic approaches, the “merged capacitor switching” scheme achieves minimum possible energy

[Hariprasath, Electronics Lett., 4/2010]

 

$$E_{dac} \cong \sum_{i=1}^{n-1} 2^{n-3-2i} (2^i - 1) CV_{ref}^2$$

**For 10 bits:**

$$E_{dac} \cong 85 CV_{ref}^2$$


# DAC Unit Capacitor Size (C)

- Is either set by noise, matching, or minimum realizable capacitance (assume  $C_{\min} = 0.5\text{fF}$ )
- We will exclude matching limitations here, since these can be addressed through calibration
- Assuming that one third of the total noise power is allocated for the DAC, we have

$$\text{SNR} \cong \frac{\frac{1}{2} \left( \frac{V_{\text{inpp}}}{2} \right)^2}{\frac{kT}{2^B C} + N_{\text{comp}} + N_{\text{quant}}}$$

$$C = 24kT \cdot \text{SNR} \cdot \frac{1}{2^B \cdot V_{\text{inpp}}^2} + C_{\min}$$

# Comparator

 

**Simple Dynamic Latch**

(Assuming  $C_{\text{cmin}} = 5\text{fF}$ )

$$N_{\text{in}} \cong \frac{kT}{C_c} \quad \text{Thermal Noise}$$


$$C_c = 24kT \cdot \text{SNR} \cdot \frac{1}{V_{\text{inpp}}^2} + C_{\text{cmin}}$$

$$B \cong \frac{\text{SNR}[\text{dB}] - 3}{6}$$

$$E_{\text{comp}} \cong \left( 24kT \cdot \text{SNR} \cdot \frac{V_{\text{DD}}^2}{V_{\text{inpp}}^2} + C_{\text{cmin}} V_{\text{DD}}^2 \right) \cdot \frac{1}{2} \cdot B$$

**Switching  
probability**

# Comparison to State-of-the-Art

 


- [1] Shikata, VLSI 2011
- [2] Van Elzakker, ISSCC 2008
- [3] Harpe, ISSCC 2012
- [4] Liu, VLSI 2010

- [5] Liu, ISSCC 2010
- [6] Hurrell, ISSCC 2010
- [7] Hesener, ISSCC 2007
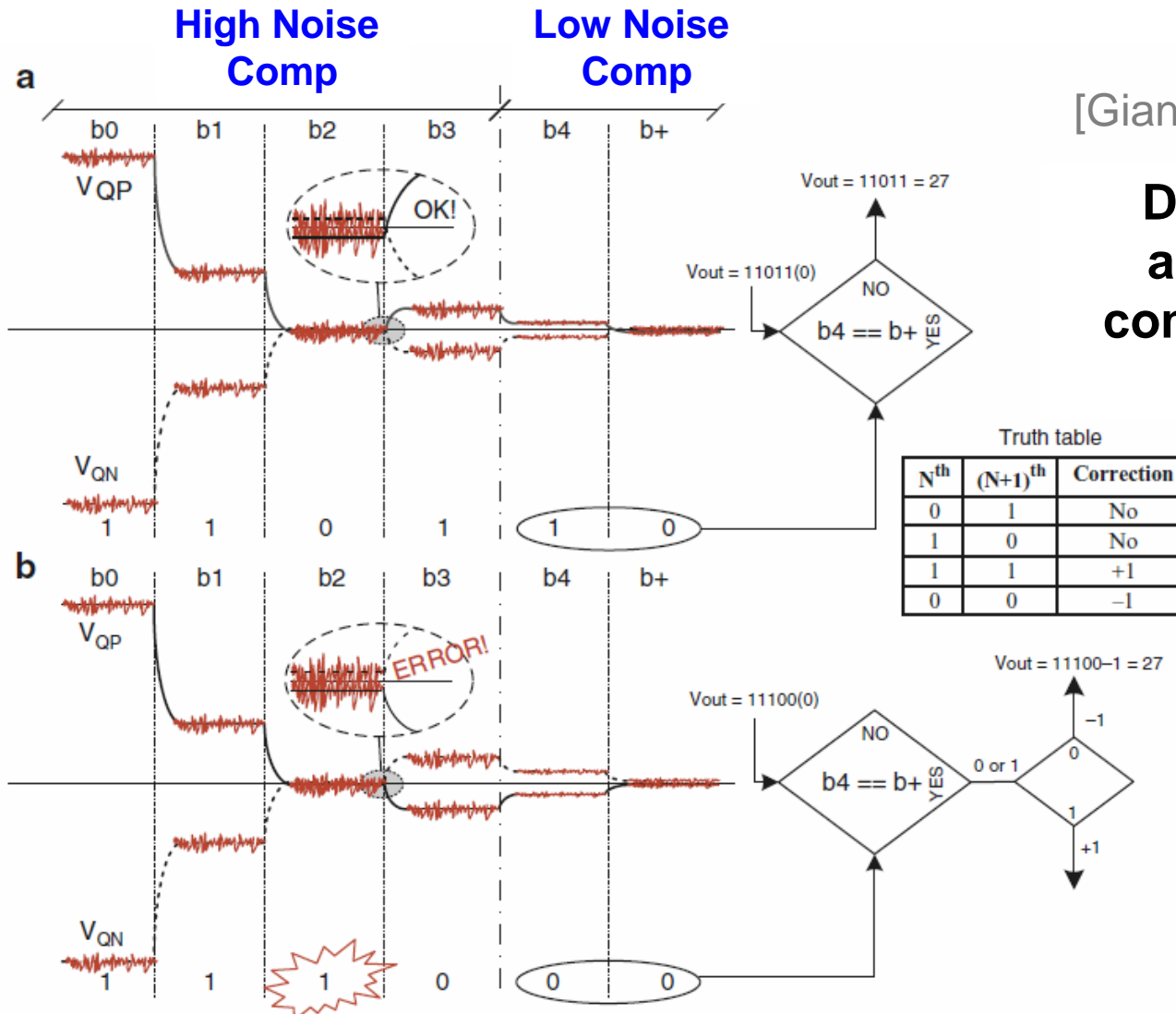
# Ways to Approach $E_{\min}$ (1)

[Giannini, ISSCC 2008]


**Dynamic Noise  
adjustment for  
comparator power  
savings**



# Ways to Approach $E_{\min}$ (2)

- Minimize unit caps as much as possible for moderate resolution designs
  - Scaling helps!

## 0.5fF unit capacitors

 


[Shikata, VLSI 2011]



# Delta-Sigma ADCs

- **Discrete time**
  - Energy is dominated by the first-stage switched-capacitor integrator
  - Energy analysis is similar to that of a pipeline stage
- **Continuous time**
  - Energy is dominated by the noise and distortion requirements of the first-stage continuous time integrator
  - Noise sets resistance level, distortion sets amplifier current level
  - Interestingly, this leads to about the same energy limits as in a discrete-time design

# Overall Picture

 

# Summary


- No matter how you look at it, today's ADCs are extremely well optimized
- The main trend is that the “thermal knee” shifts very rapidly toward lower resolutions
  - Thanks to process scaling and creative design
- At high resolution, we seem to be stuck at  $E/E_{\min} \sim 100$ 
  - The factor 100 is due to architectural complexity and inefficiency: excess noise, signal < supply, non-noise limited circuitry, class-A biasing, ...
- This will be very hard to change
  - Scaling won't help (much)
  - Some of the recent data points already use class-B-like amplification
  - Can we somehow recycle the signal charge?
- Are there completely new ways to approach A/D conversion?

# Darpa Has Seen the Future of Computing ... And It's Analog

BY ROBERT MCMILLAN 

08.22.12 6:30 AM

 Like 773  
 Tweet 740  
 +1 270

 

<http://www.wired.com/wiredenterprise/2012/08/upside/>