

Homework #2

(due Wed 10/2/2019; submit through bCourses)

*Instructor: Johan Vanderhaegen (jpv@berkeley.edu)***Problem 1. Spectral Analysis**

Download the file `hw2_p1_data.mat` from the course website assignments folder. It contains the output of a 12-bit ADC with a sampling frequency of 25 MHz and a full-scale range of $[-1, +1]$. The input was a full-scale sinusoidal signal.

- Plot the spectrum from 0 to $f_s/2$ using FFT without averaging. The y axis should be in dBFS while the x axis should be in MHz.
- What is the frequency f_{in} of the sinusoidal signal at the input of the ADC?
- Compute the following metrics: SNR, SNDR, ENOB, THD, SFDR.
- Which non-ideality is limiting the SFDR in this case?

Problem 2. Current Steering DACs

- Read the following paper: C.-H. Lin and K. Bult, "A 10-b, 500-MSample/s CMOS DAC in 0.6 mm²," IEEE J. Solid-State Circuits, Vol.33, pp. 1948–1958, Dec. 1998.
- In the above reference, it was found that for the given objectives, a thermometer/ binary partition of 8/2 is most suitable. Your task in this problem is to re-optimize this DAC for 65nm technology with a different set of process parameters, without altering its basic structure. The design variables to be optimized are:

Parameter	Description
B_t	Number of bits in thermometer section
A_{unit}	Area of unit current source

Your target specs and process parameters are:

Parameter	Description	Value
B	Resolution	12 bits
INLspec	Worst case integral nonlinearity	< 2 LSB
DNLspec	Worst case differential nonlinearity	< 0.5 LSB
Y	Target yield	99%
A_{decode}	Approximate decoder and routing area	$2^{B_t} 200 \mu\text{m}^2$
A_{total}	Total DAC area (to be minimized)	$2^B A_{\text{unit}} + A_{\text{decode}}$
k_u	Unit element matching parameter	3 %um
σ_u	Standard deviation of unit element mismatch	$k_u / \sqrt{A_{\text{unit}}}$

- (a) Following the procedure outlined in the reference, answer the following **using only hand calculations** (After the equations are written by hand, it is ok to use Matlab to perform a sweep across **integer** values of B_t):
- What values of A_{unit} and B_t actually minimize the total area?
 - What is the minimum total area (in mm^2)?
- (b) Create a plot similar to Fig. 9 of the reference paper to illustrate the “minimum area” design. In this diagram, plot the total DAC area in mm^2 (log scale) versus the design parameter B_t (linear scale in bits).

Problem 3. Flash ADC

Consider a 6-bit flash ADC with an ideal reference resistor string and $V_{\text{REF}} = 1.8 \text{ V}$. Assume that the pre-amps have an offset voltage with standard deviation $\sigma_{\text{offset}} = 3 \text{ mV}$ and the comparators are ideal. For simplicity, assume that the first and last preamp have zero offset.

- What are the standard deviations of the converter’s DNL and INL? (Note that DNL and INL are always stated in terms of LSB).
- How will the σ_{DNL} and σ_{INL} be affected by 4x interpolation ($M=4$)? (For a constant LSB)

Problem 4. kT/C Noise

Shown below in figure 1 is the schematic of an NMOS sampler used in the front-end of a B -bit ADC. The RC time constant of this circuit was chosen such that it settles to within 1 LSB in one half clock period.

Derive an expression for the total thermal noise of the sampler in terms of the switch resistance R , the number of bits B , the sampling rate f_s , the Boltzmann constant k , and the absolute temperature T .

 


Figure 1: NMOS sampling switch