

# **EE 240C**

## **Analog-Digital Interface Integrated Circuits**

### **Multistage Decimation Filters**

# Multistage Decimation Filters

---

- Decimation filter #2 can be realized with a accumulator rate of 57MHz, shift register, and coefficient ROM
  - A multiplier is not needed
- Multi-rate decimators can achieve the same result with even lower processing cost
- We will:
  - Illustrate how multistage decimation requires substantially lower multiply-accumulate rates than single stage decimation
  - Introduce very specific filter architectures that are specialized just for decimation/interpolation and can further reduce hardware complexity

# Multistage Decimation Filters

---

- In multistage decimation, implement the sharpest transition bands at the lowest sampling frequency
- For our 3MHz audio modulator, we'll decimate by 64 in 3 stages
  - 8X in the first stage
  - 4X in the second stage
  - 2X in the third stage

# Multistage Decimation Filters

---

- Datapath precision is important here
  - Stage 1 has 1-bit input data and doesn't need a hardware multiplier
  - Intermediate rounding operations between stages 1 and 2 and between stages 2 and 3 add quantization noise which must be modeled in a “bit true” fashion
  - Final rounding to the 20-bit ADC output adds negligible noise
- Coefficient precision is also important
  - 24b precision for 135dB stopband attenuation

# Parks-McClellan Decimation

---

- In the first pass with synthesize the three stages with the Parks–McClellan algorithm and stick with floating point numbers
  - The results provide an estimate of aggregate multiply accumulate rates
- Each stage will specify  $0.0000 \pm 0.0033$  dB ripple from 0–20kHz
  - Passband ripple in the 3 stages may add
  - The goal is a “fair” comparison to filter #2

# Parks-McClellan Decimation

---

- Stages 1 and 2 prevent decimation from aliasing noise and tones into frequencies below 27kHz
- Stage 1 stopbands:
  - $375 \pm 27\text{kHz}$ ,  $750 \pm 27\text{kHz}$ ,  $1125 \pm 27\text{kHz}$ ,  $1473\text{--}1500\text{kHz}$
- Stage 2 stopbands:
  - $93.75 \pm 27\text{kHz}$ ,  $160.5\text{--}187.5\text{kHz}$
- Stage 3 stopband:  $27\text{--}46.875\text{kHz}$
- For each stage we specify 135dB stopband attenuation

# Parks-McClellan Decimation

---

- MATLAB's Parks-McClellan front end doesn't handle lowpass filters like stage 1 very easily
  - The low pass filter we want has a single passband, multiple stopbands, and interspersed don't care bands
- We'll waste zeroes and implement stages 1 and 2 as single-stopband LPFs:
  - Stage 1 stopband 348–1500kHz
  - Stage 2 stopband 66.75–187.5kHz
  - Stage 3 stopband still 27–46.875kHz

# Parks-McClellan Decimation

---

- These Parks–McClellan designs yield:
  - Stage 1: Length 57 (21.375MHz)
  - Stage 2: Length 50 (4.688MHz)
  - Stage 3: Length 84 (3.938MHz)
- Multiply–accumulate rates are shown in red above
  - Total multiply–accumulate frequency is 30MHz
  - Exploiting linear phase coefficient symmetry can reduce this to 15MHz
  - The filter #2 design required 57MHz



# **EE 240C**

## **Analog-Digital Interface Integrated Circuits**

### **Comb Filters**

# Comb Filters

---

- Let's look at the a “rectangular” transfer function,

$$\begin{aligned} H(z) &= \sum_{i=0}^{N-1} z^{-i} \\ &= 1 + z^{-1} + z^{-2} + z^{-3} + z^{-4} + z^{-5} + z^{-6} + z^{-7} + \dots \\ &= \frac{1 - z^{-N}}{1 - z^{-1}} \end{aligned}$$

- This filter has  $N-1$  evenly spaced zeros on the unit circle, except at  $z=1 \rightarrow$  LPF
- A  $N=8$  rectangular window is the simplest filter candidate for a decimate-by-8 stage 1 design


# Comb Filters

- A single comb filter obviously will not meet the specification ... but a cascade of K of them might
- The resulting filter is not very good (significant in-band droop), but a “trick” due to Hogenauer leads to an extraordinarily simple implementation

$$\begin{aligned} H(z) &= \left[ \sum_{i=0}^{N-1} z^{-i} \right]^K = \left[ \frac{1 - z^{-N}}{1 - z^{-1}} \right]^K \\ &= \left[ \frac{1}{1 - z^{-1}} \right]^K [1 - z^{-N}]^K \end{aligned}$$


- Let's see how this looks in hardware ...

# Hogenauer Filter, K=5

 

- The integrators operate at  $f_{\text{SIN}}$ , the differentiators at  $f_{\text{SOUT}}$
- The decimate block throws away  $N-1$  of every  $N$  integrator output samples
- $z^{-1}$  at  $f_{\text{SOUT}}$  is equivalent to  $z^{-N}$  at  $f_{\text{SIN}}$

# Hogenuer K=5 Cascade

 

[Eric Swanson]

# Hogenauer Filters

---

- The Hogenauer 5-cascade doesn't come close to meeting our 135dB antialiasing specification near 375kHz
  - A higher value of  $K$  is needed (typically  $L+1$  or more)
- Hogenauer implementations aren't without difficulty
  - The high-speed integrators integrate offsets to infinity and must “roll over” gracefully
  - Word-width requirements grow through the cascade

Ref: Eugene Hogenauer, “An Economical Class of Digital Filters for Decimation and Interpolation”, IEEE Trans. Acoustics, Speech, and Signal Processing, ASSP-29, April 1981.


# **EE 240C**

## **Analog-Digital Interface Integrated Circuits**

### **Other $\Sigma\Delta$ Topics**
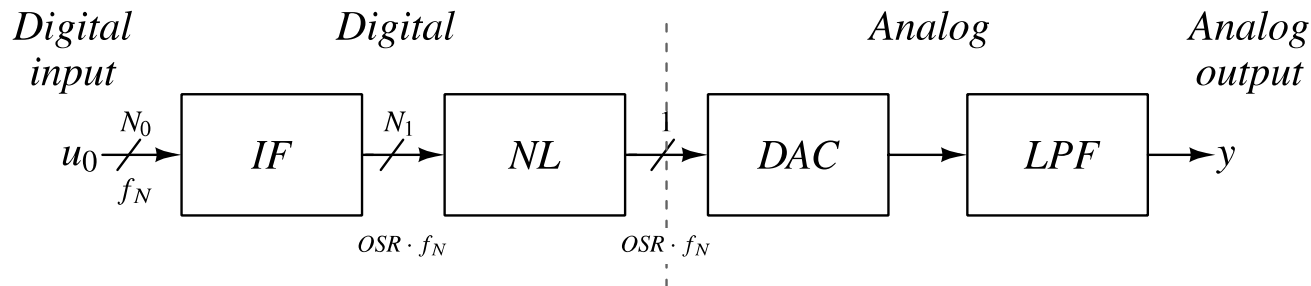
# $\Sigma\Delta$ DACs

- Can build high-SNDR DAC using:
  - Digital interpolator (to increase sample rate by OSR)
  - Digital  $\Sigma\Delta$  DAC modulator
    - Often error-feedback sigma-delta modulator
  - 1 bit DAC
  - Low-pass reconstruction filter




*IF: Interpolation filter*  
*NL: Noise-shaping Loop*

*DAC: Digital-to-Analog Converter*  
*LPF: Lowpass Filter*



 
# $\Sigma\Delta$ DACs: Error-Feedback Modulator



- Quantize to 1 bit  $\rightarrow$  keep MSB  
Quantization error  $\rightarrow$  LSBs
- $V(z) = U(z) + (1 - H_e(z)) E(z)$
- For 1<sup>st</sup> order loop:  $H_e(z) = z^{-1}$   
For 2<sup>nd</sup> order loop:  $H_e(z) = z^{-1}(2 - z^{-1})$
- Error-feedback structure not practical for analog  $\Sigma\Delta$  ADCs
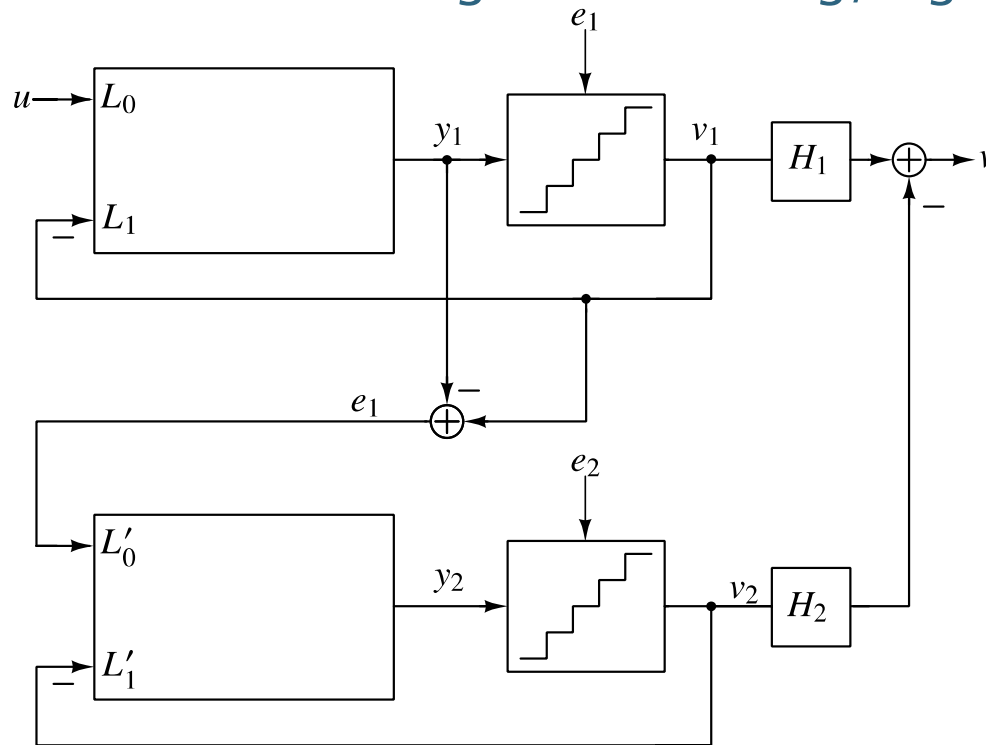
# Multi-Stage $\Sigma\Delta$ ADCs

- Cancel quantization noise of first stage(s) using additional stages
- Issue: noise leakage from analog/digital mismatch



$$\begin{aligned} V_1(z) &= STF_1(z) U(z) + NTF_1(z) E_1(z) \\ V_2(z) &= STF_2(z) E_1(z) + NTF_2(z) E_2(z) \\ V(z) &= H_1(z) V_1(z) - H_2(z) V_2(z) \end{aligned}$$

$E_1(z)$  term in is canceled if:  
 $H_1(z) NTF_1(z) = H_2(z) STF_2(z)$


→  $H_1(z) = STF_2(z)$   
 and  $H_2(z) = NTF_2(z)$

→  $V(z) = \begin{matrix} STF_1(z) STF_2(z) \\ -NTF_1(z) NTF_2(z) \end{matrix}$   
 → Higher order noise shaping

**Figure 5.3** A two-stage MASH structure.
 
# Quantization Noise Leakage


- If actual analog STF and NTF do not match digital H:
- $STF_{2a}(z) \neq STF_2(z) = H_1(z)$   
 $NTF_{1a} \neq NTF_1(z) = H_2(z)$
- Result:  $H_{l1}(z) = H_1(z) STF_{2a}(z) - H_2(z) NTF_{1a}(z)$   
→ First stage quantization error leakage:  $H_{l1}(z) E_1(z)$




2-2 MASH  $\Sigma\Delta$  ADC
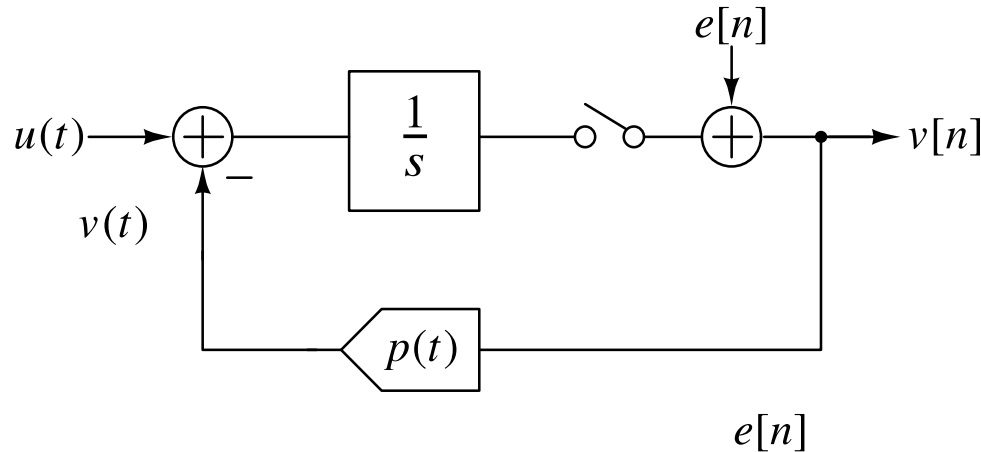
# Continuous-Time $\Delta\Sigma$ ADCs

- Continuous-time integrators instead of discrete-time



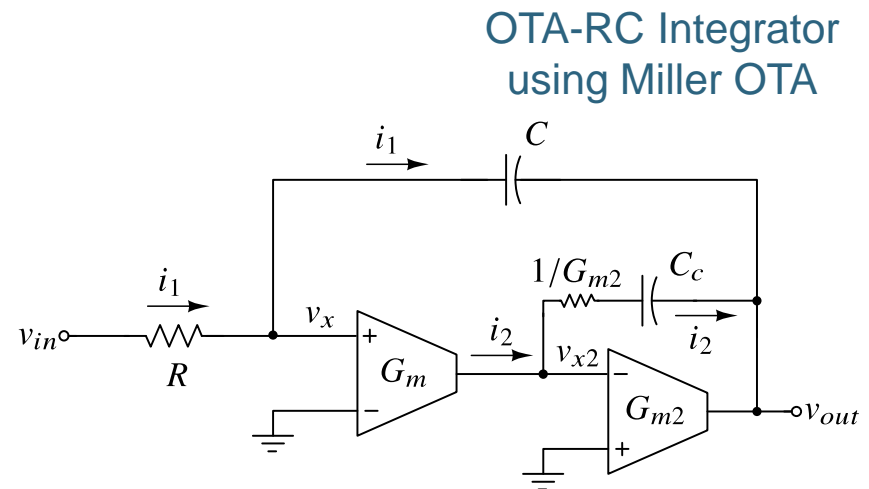
- Design using impulse invariant transform  $CT \leftrightarrow DT$



- CT typically lower power compared to DT
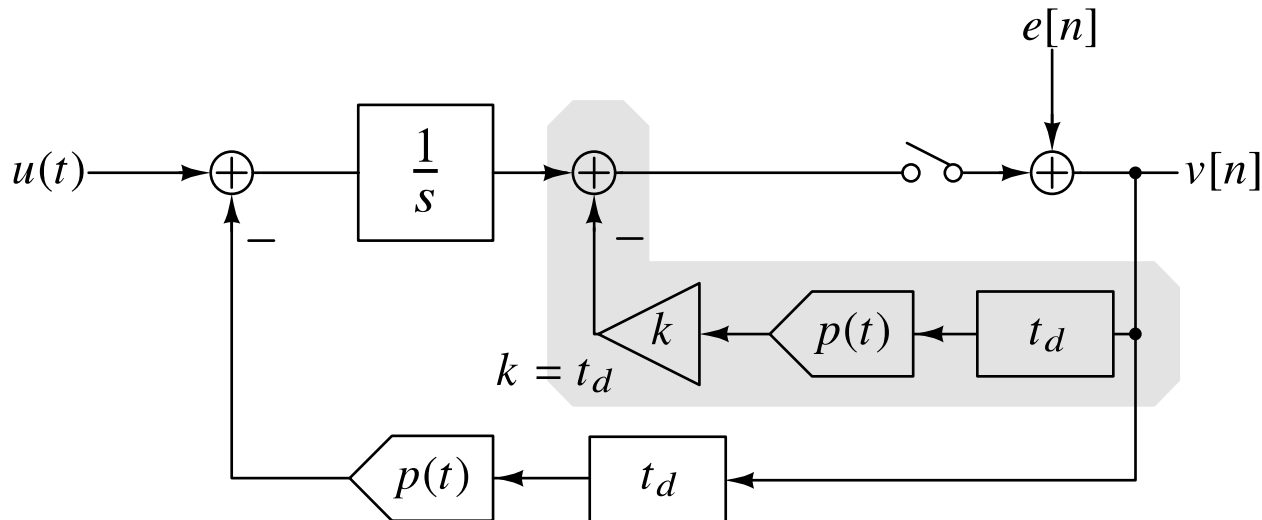
# Continuous-Time $\Delta\Sigma$ ADC Non-Idealities

- Excess loop delay from quantizer to feedback DAC
  - Comparator needs time to resolve input
  - Requires loop modifications



- RC time-constant variations  $\rightarrow \Sigma\Delta$  loop variations
- Clock jitter sensitivity


# Multi-Bit $\Sigma\Delta$ ADCs/DACs

---

- Multi-bit quantizer & multi-bit feedback DAC
  - Lower quantization with same loop filter & OSR
  - Lower jitter sensitivity in CT loops
    - Smaller feedback steps
- 3-level DAC requires 0.01% matching for  $-90\text{dB}$  distortion
- Solution
  - Calibration (but aging, drift, package shifts, ...)
  - Digital correction (but aging, drift, package shifts, ...)
  - Mismatch shaping

# Mismatch-Shaping for Multi-Bit $\Sigma\Delta$ ADCs/DACs (1/3)

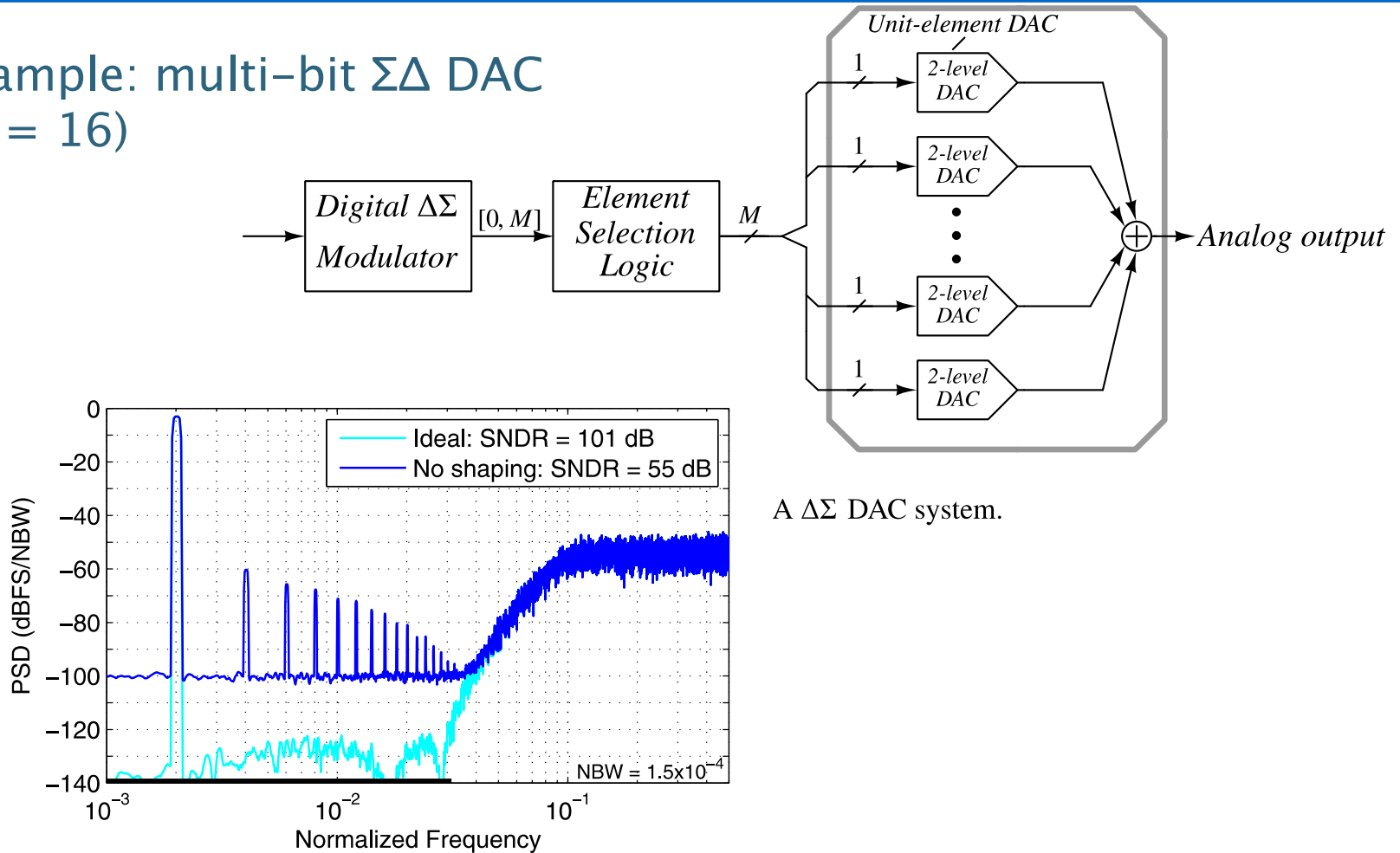- Example: multi-bit  $\Sigma\Delta$  DAC  
( $M = 16$ )




A  $\Sigma\Delta$  DAC system.

**Figure 6.4** Average PSD for a 16-element DAC with 1% element mismatch – no shaping.

# Mismatch-Shaping for Multi-Bit $\Sigma\Delta$ ADCs/DACs (2/3)

- Random element selection  
→ removes tones, but does not lower noise floor

 


**Figure 6.5** Average PSD for a 16-element DAC with 1% element mismatch– random selection.



# Mismatch-Shaping for Multi-Bit $\Sigma\Delta$ ADCs/DACs (3/3)


- Element rotation
  - Data-weighted averaging
  - Shapes mismatch-induced noise floor

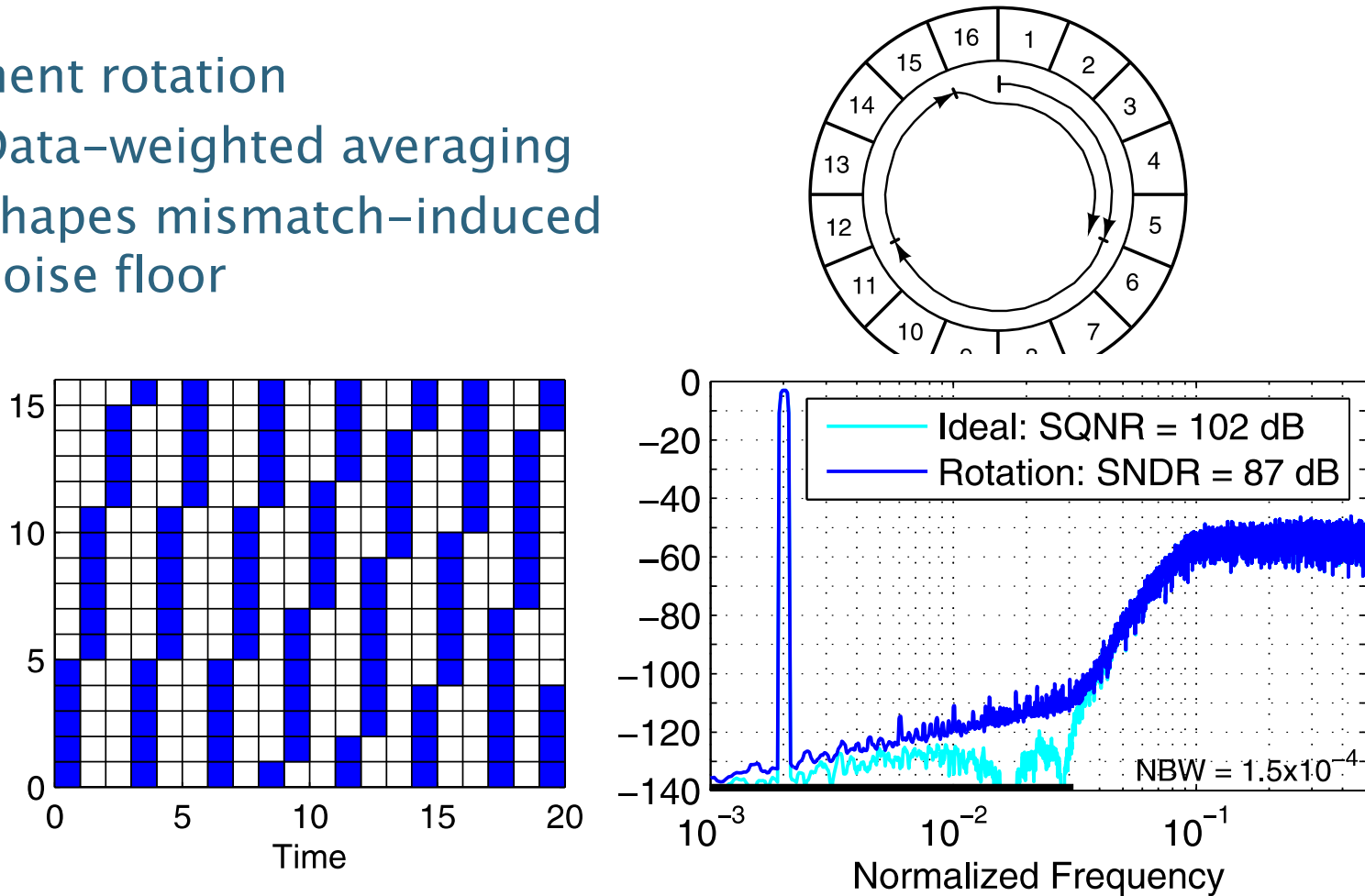

**Figure 6.7** Example usage pattern and spectrum for rotation.
 
# Bandpass $\Delta\Sigma$ ADCs

- Band-stop NTF instead of high-pass NTF
- Applications: wireless communications; resonant sensors


 


**Figure 11.5** (a) Pole-zero and (b) NTF/STF magnitude plots for an  $f_s/6$  bandpass modulator.

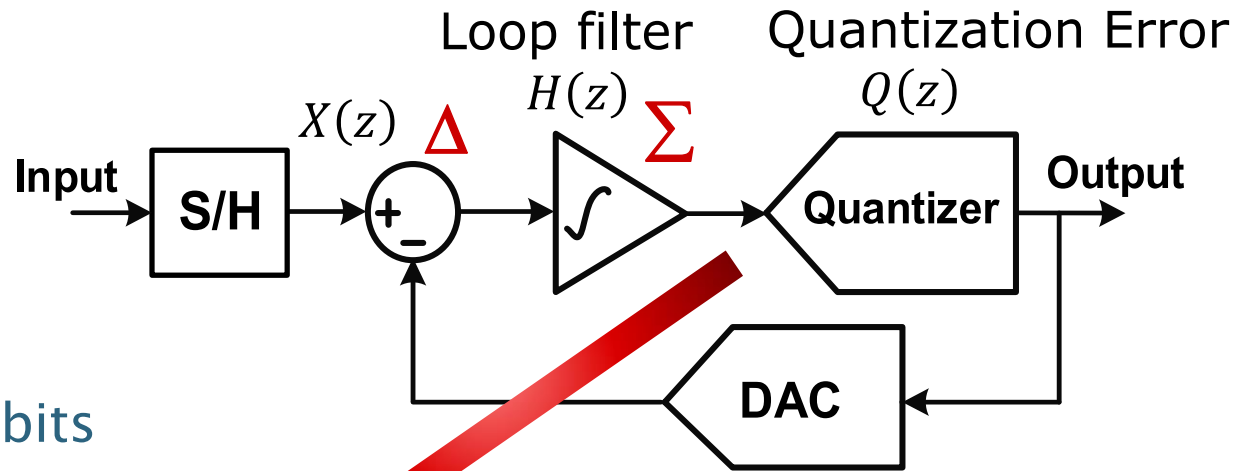
# Hybrid Oversampling ADCs

- Increased quantizer resolution with limited OSR

- Flash quantizer not efficient for higher number of bits





# VCO-based Quantizer

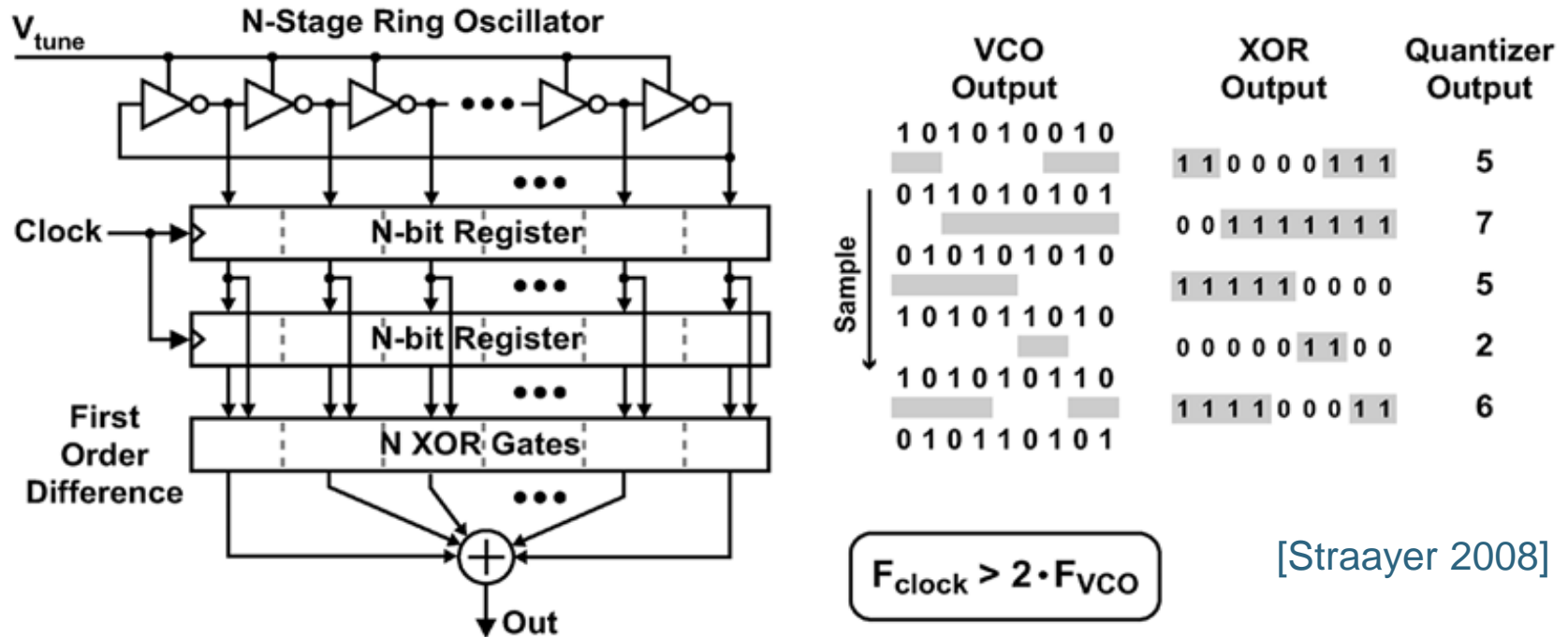

- Free running VCO:  
quantized value = number of VCO stages changing over  $T_{clk}$   
– Calculated using registers and XOR gates
- $K_{VCO}$  limits linearity
- Thermometer code at output of XOR gates rotates  $\rightarrow$  DEM

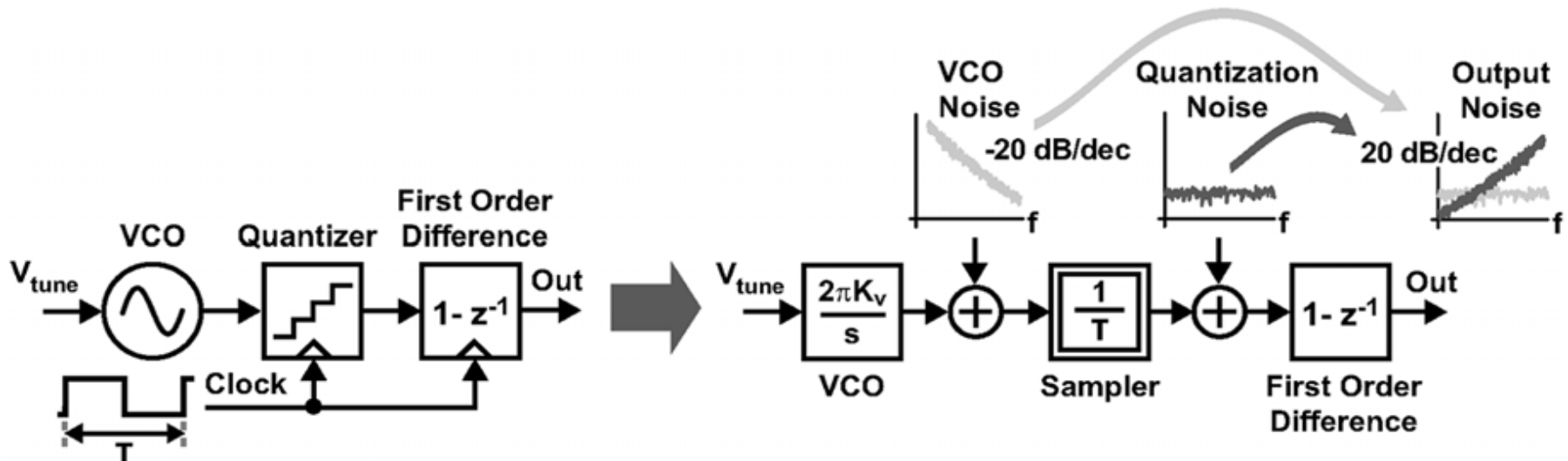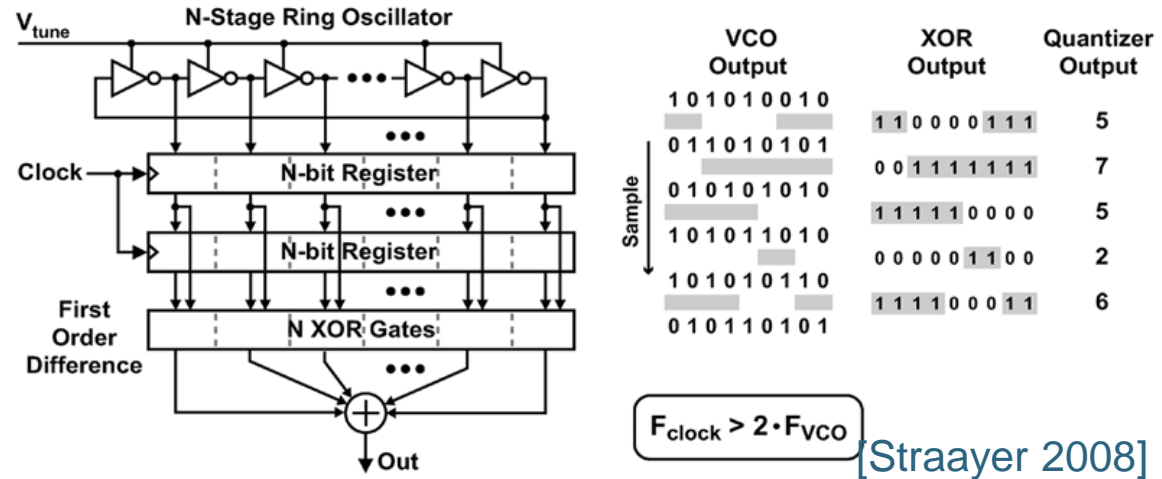
# VCO-based Quantizer: Noise Shaping

- Quantization noise is shaped  
→ additional order of noise shaping




# VCO-based Quantizer: Implicit DEM

- Thermometer code at output of XOR gates rotates → DEM

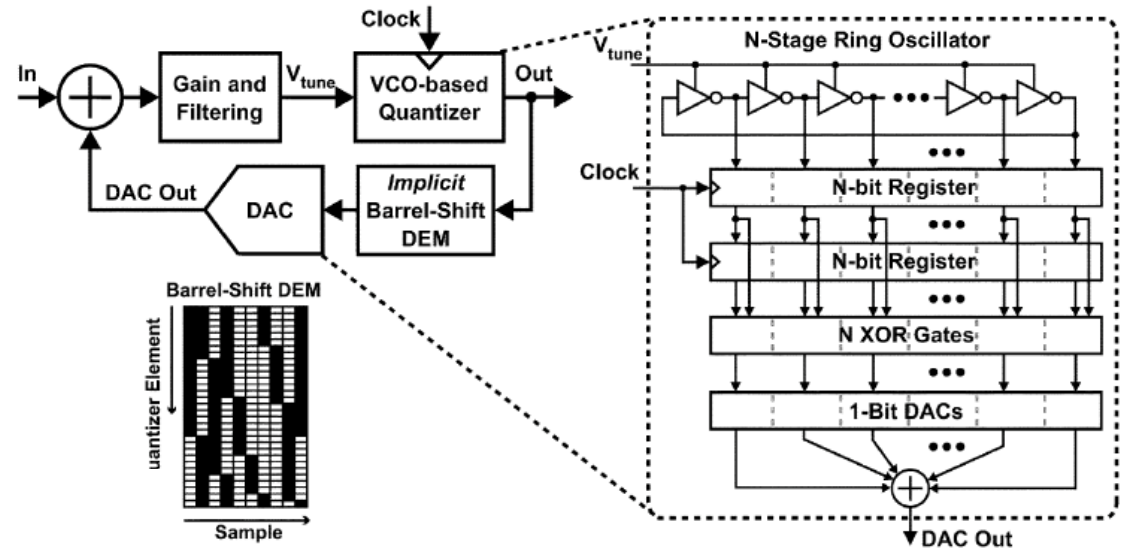


[Straayer 2008]

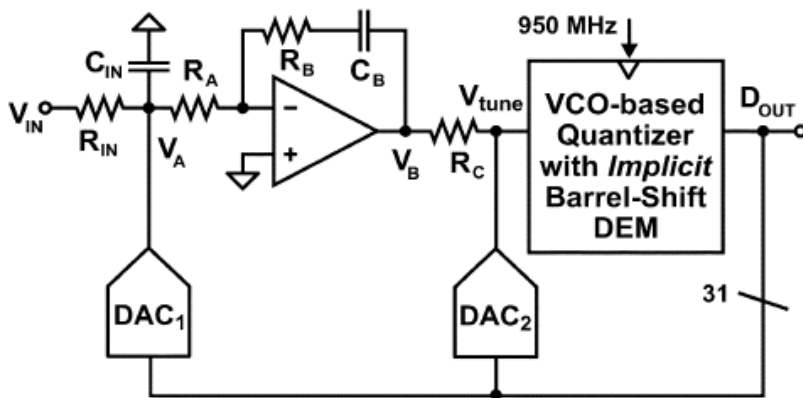12b 86dB SNDR  
10 MHz BW, 950 MS/s, 40 mW



# Noise Shaping SAR

- Use SAR residue as quantization error

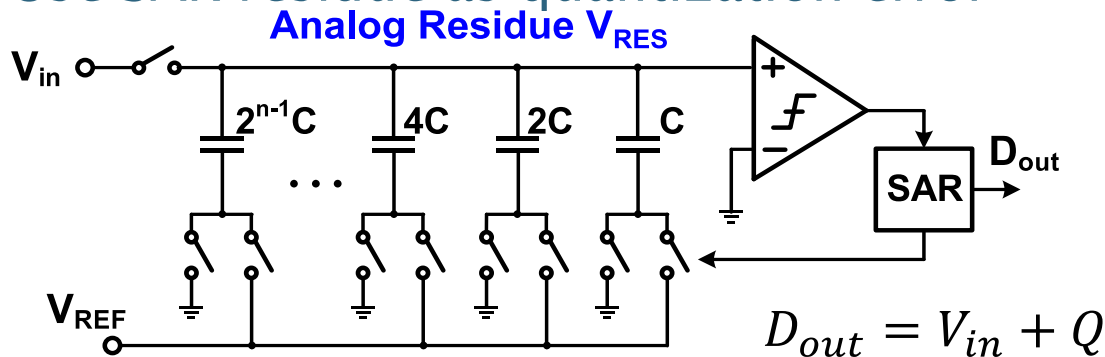

[Fredenburg 2012]


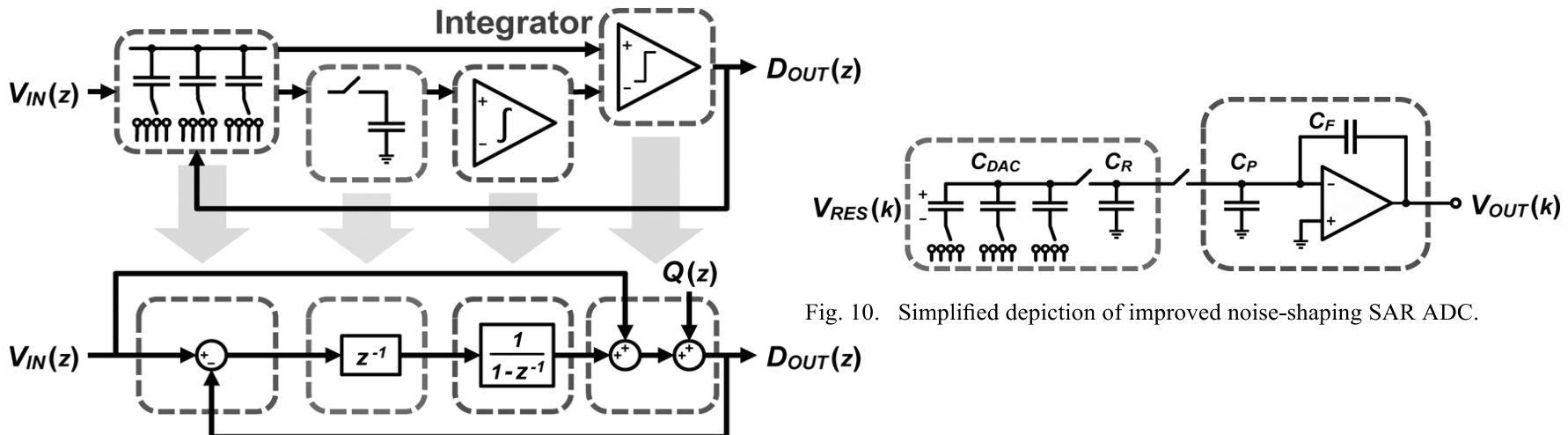


Fig. 10. Simplified depiction of improved noise-shaping SAR ADC.

# Incremental ADCs

- Incremental ADC = resettable  $\Sigma\Delta$  ADC (& resettable decimation)
  - Multiplexed operation
  - Duty-cycled <sup>(a)</sup> operation

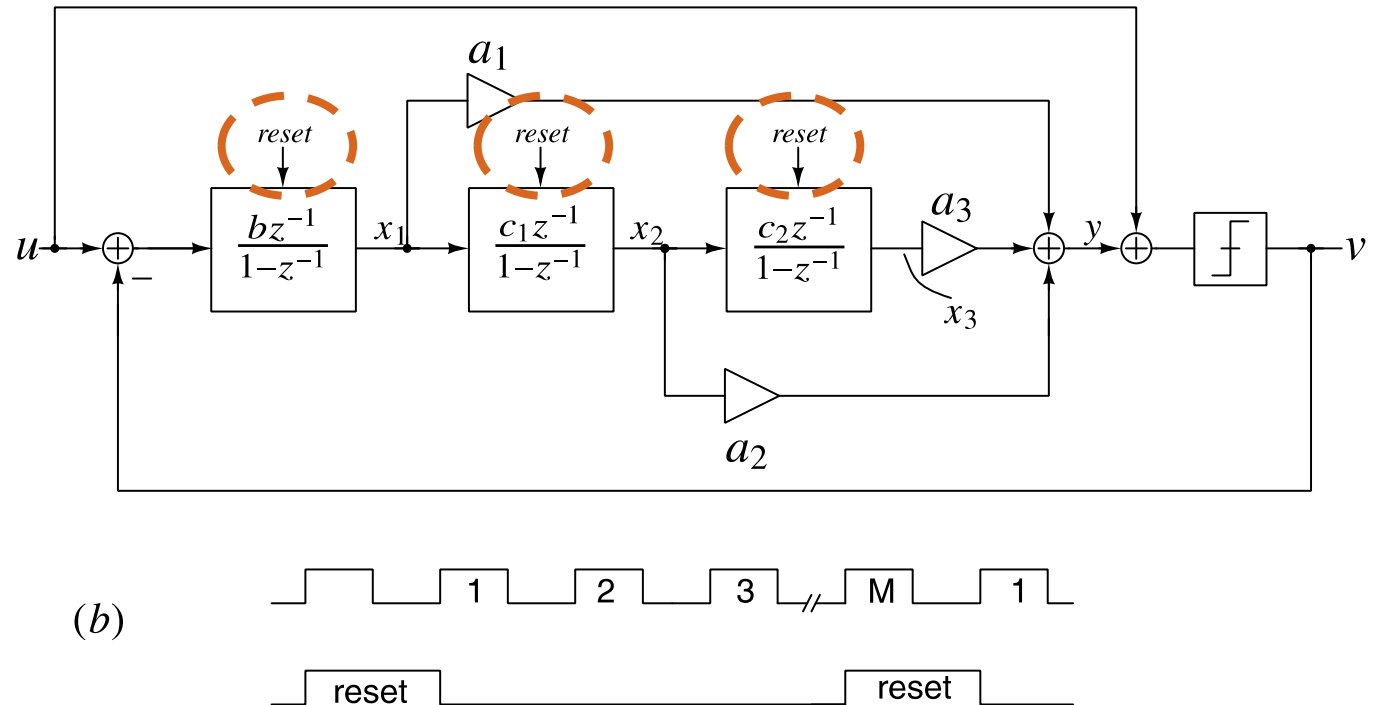

**Figure 12.3** Third-order IADC.




# **EE 240C**

## **Analog-Digital Interface Integrated Circuits**

### **Limits on ADC Power Dissipation**
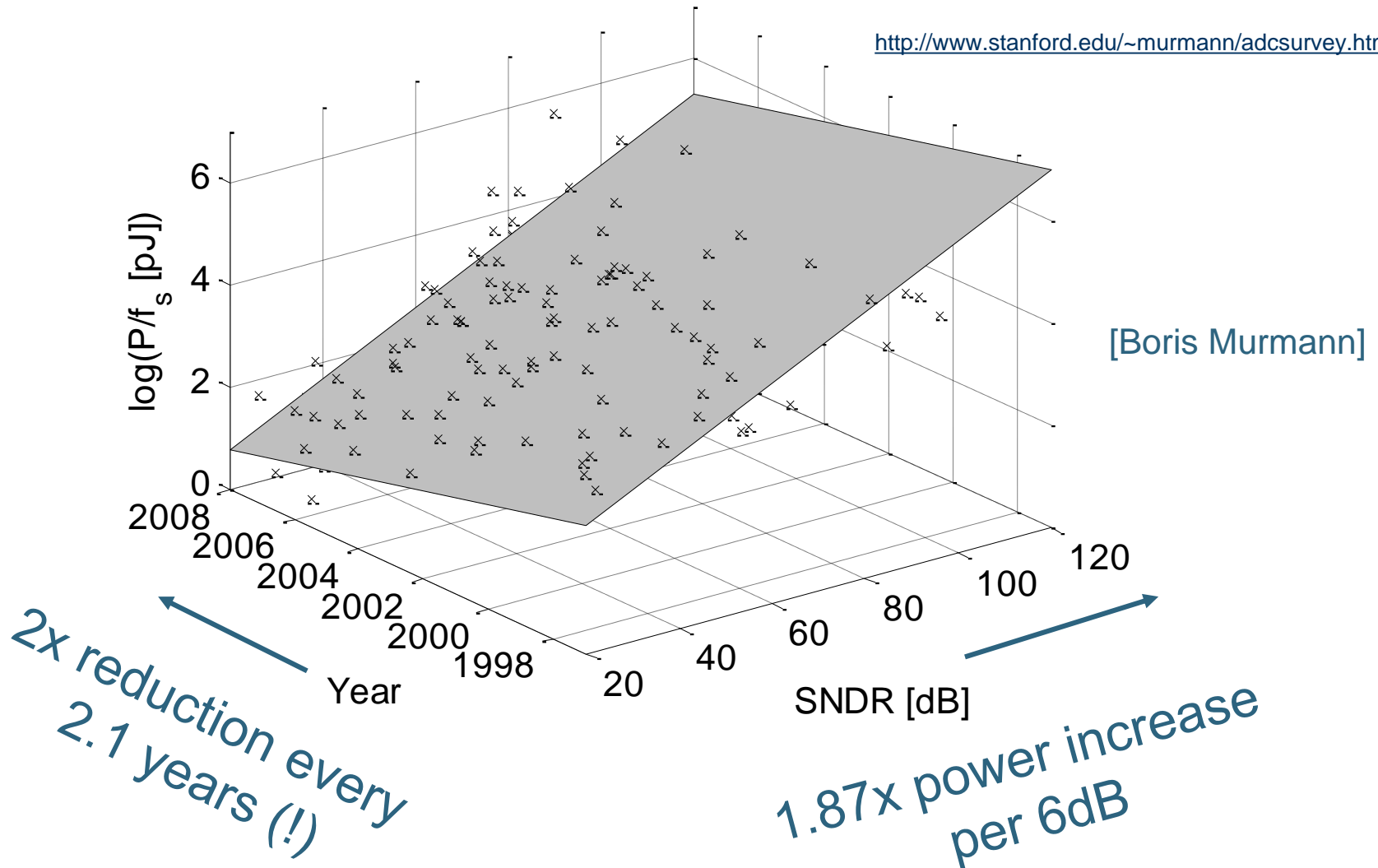
# Power Dissipation Trend

<http://www.stanford.edu/~murmnn/adcsurvey.html>



# Predicting the Trend

---

- Figures of Merit
- Fundamental Limits
- Practical Limits

# ADC Figures of Merit (1)

---

- Objective
  - Compare performance of different ADCs
- Can use FOM to combine several performance metrics into one single number
- What are reasonable FOMs for ADCs?
- What's the impact of technology scaling?
- Trends and limits?
  
- Reference: B. Murmann, "Limits on ADC Power Dissipation," in *Analog Circuit Design*, by M. Steyaert, A.H.M Roermund, J.H. van Huijsing (eds.), Springer, 2006.

# ADC Figures of Merit (2)


---

$$\text{FOM}_1 = f_s \cdot 2^{\text{ENOB}}$$

[R. H. Walden, "Analog-to-digital converter survey and analysis," *IEEE Journal on Selected Areas in Communications*, April 1999]

- This FOM suggests that adding a bit to an ADC is just as hard as doubling its bandwidth
- Is this a good assumption?

# Survey Data

 

[Walden, "Analog-to-digital converter survey and analysis," *IEEE J. Selected Areas Comm.*, April 1999]

# ADC Figures of Merit (3)

---

$$\text{FOM}_W = \frac{\text{Power}}{f_s \cdot 2^{\text{ENOB}}}$$

[R. H. Walden, "Analog-to-digital converter survey and analysis," *IEEE Journal on Selected Areas in Communications*, April 1999]

- Walden Figure of Merit
- Most widely used FOM
- In typical circuits power  $\sim$  speed
  - $\text{FOM}_W$  captures this tradeoff correctly
- Power vs. ENOB
  - One additional bit = 2x in power?

# ADC Figures of Merit (4)

---

- In a circuit that is limited by thermal noise, each additional bit in resolution means...
  - 6dB SNR, 4x less noise power, 4x bigger C
  - Power  $\sim G_m \sim C$  increases 4x
- Even worse: Flash ADC
  - Extra bit means 2x number of comparators
  - Each of them needs double precision
  - Transistor area 4x, Current 4x to maintain current density
  - Net result: Power increases 8x
- "Tends to work" because not all power in an ADC is noise limited
  - E.g. Digital power, biasing circuits, etc.



# ADC Figures of Merit (5)

---

$$\begin{aligned}\text{FOM}_3 &= \frac{\text{Power}}{2 \cdot \text{Conversion Bandwidth}} \\ &= \text{"Energy / Nyquist Sample"} \\ &= [\text{J}/\text{conv.}]\end{aligned}$$

- Compare only power of ADCs with approximately same SNR or SNDR (ENOB)
- Useful numbers (~state-of-the-art):
  - 10b (~9 ENOB) ADCs: 0.25 ... 1 mW/MHz
  - 12b (~11 ENOB) ADCs: 2 ... 6 mW/MHz

# ADC Figures of Merit (6)


---

$$\text{FOM}_S = \text{DR}(dB) + 10 \log_{10}\left(\frac{\text{BW}}{\text{Power}}\right)$$

- Schreier Figure of Merit
- Power vs. ENOB
  - One additional bit = 4x in power
  - Thermal noise limited ADCs
- HF Schreier FoM:
  - SNDR instead of DR: includes distortion

$$\text{FOM}_{S,\text{HF}} = \text{SNDR}(dB) + 10 \log_{10}\left(\frac{\text{BW}}{\text{Power}}\right)$$


# FOM (ISSCC & VLSI 1998 – 2018)

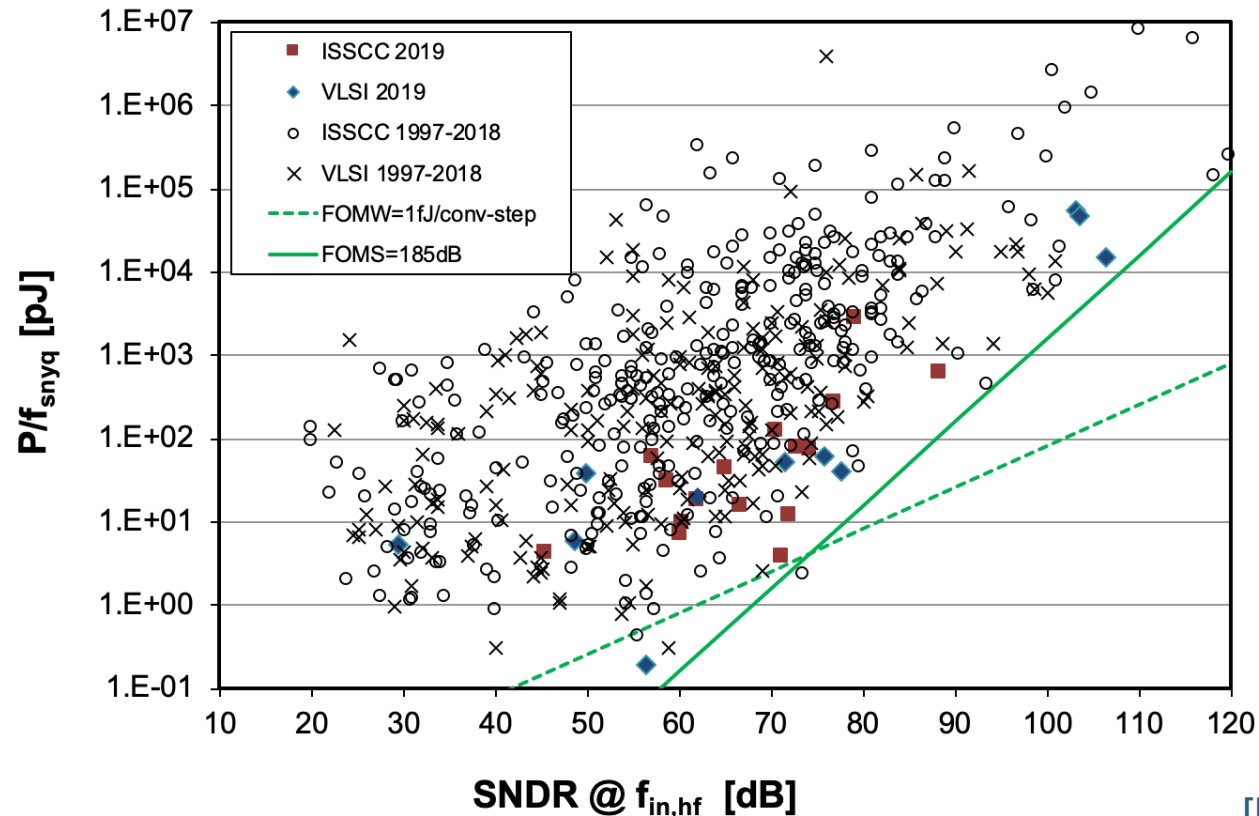

[Murmans]

- Technology-limited at lower SNDR:  $100 \text{ fJ} = 1\text{V } 100 \text{ fF} / \text{conv}$
- Noise-limited at higher SNDR

# FOM (ISSCC & VLSI 1998 – 2018)

 

- Some improvement over time at low  $f_{snyq}$  (1 dB / year)
- Progress at high  $f_{snyq}$  driven by technology scaling (2x / 1.6yr)

# **EE 240C**

## **Analog-Digital Interface Integrated Circuits**

### **Fundamental Limits**

# Fundamental Limits


- Fundamental power limit for a class-B amplifier driving a single capacitor [Vittoz, ISCAS 1990]

$$P = 8 \cdot f_{sig} \cdot C V_{sig}^2 \quad V_n^2 = \frac{k_B T}{C} \quad SNR = \frac{0.5 \times V_{sig}^2}{V_n^2}$$

$$\therefore P = 8k_B T \cdot SNR \cdot f_{sig}$$

- Class-A power limit is  $\pi$  times higher
- At  $f_{sig} = f_s/2 \rightarrow FOM_S = 195$  dB

# Switched Capacitor Circuits

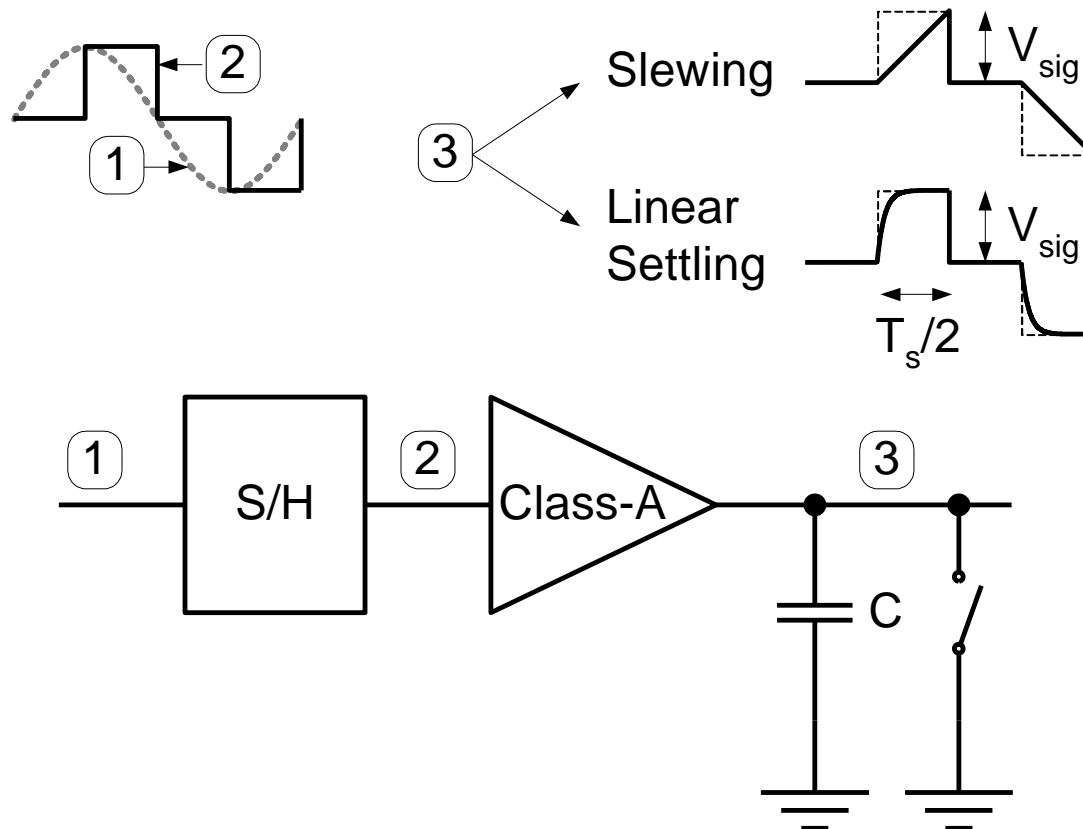

# Case 1: 100% Slewing

---

$$I_{bias} = C \cdot \frac{dV}{dt} = C \cdot \frac{V_{sig}}{T_s / 2} = 4 \cdot C \cdot V_{sig} \cdot f_{sig}$$

$$P = 2 \cdot V_{sig} \cdot I_{bias} \qquad SNR = \frac{0.5 \times V_{sig}^2}{k_B T / C}$$

$$\therefore P = 16 k_B T \cdot SNR \cdot f_{sig}$$



## Case 2: 100% Linear Settling


$$I_{bias} = C \cdot \left. \frac{dV}{dt} \right|_{max} = C \cdot \left. \frac{d}{dt} \right|_{max} \left[ V_{sig} \left( 1 - e^{-t/\tau} \right) \right] = C \cdot \frac{V_{sig}}{\tau}$$

Number of settling time constants:  $N = \frac{T_s / 2}{\tau}$

$$\therefore P = 16 \cdot N \cdot k_B T \cdot SNR \cdot f_{sig}$$

- Much worse
  - E.g. N=6.9 for settling to 0.1% precision

# Limit Lines

 

# **EE 240C**

## **Analog-Digital Interface Integrated Circuits**

### **Practical Limits**

# Discussion

---


- Orders of magnitude away from limits
- Slope of limit lines is much steeper than fit to experimental data
- What contributes to these large gaps?
  - Must keep in mind that ADCs are not just single capacitor circuits ...
- The following analysis factors in practical considerations
  - Not fundamental, but somewhat unavoidable in today's implementations

# Design Space Partitioning

---

- High SNR
  - Complexity  $\sim 1$  (e.g. first integrator in sigma-delta ADC)
  - Limited by thermal noise
- Moderate SNR
  - Complexity  $\sim \text{Bits}$  (e.g. pipelined ADC)
  - Partly limited by thermal noise
- Low SNR
  - Complexity  $\sim 2^{\text{Bits}}$  (e.g. flash ADC)
  - Limited by matching, quantization noise

## High SNR SC-Stage (1)

 

- Considerations
  - Noise is multiple of  $k_B T / C$  ( $n_f$ )
  - Swing is only a fraction of  $V_{DD}$  ( $\alpha$ )
  - Feedback factor ( $\beta$ )
  - $g_m / I_D$  is upper bounded (especially if slewing must be avoided)

# High SNR SC-Stage (2)


---

To avoid slewing:  $\frac{g_{m1}}{I_{bias}} \leq \frac{1}{\beta \cdot V_{sig}}$

$$\therefore P = 16 \cdot N \cdot n_f \cdot \frac{1}{\alpha} \cdot k_B T \cdot SNR \cdot f_{sig} \cdot \max \left( 1, \frac{1}{\frac{g_{m1}}{I_{bias}} \cdot \beta \cdot V_{sig}} \right)$$

- Graph on following slide shows result assuming
  - $n_f=5$ ,  $\alpha=2/3$ ,  $\beta=0.5$ , onset of slewing

# High SNR SC-Stage (3)

 

- Close to experimental data at high SNDR!




# Medium SNR

---

- Consider two cases
- Pipeline ADC using SC stages
  - Partially limited by thermal noise
- Continuous time  $G_m$ -C integrator
  - Limited by distortion

# Pipeline ADC

 


- Theoretical near optimum power scaling
  - Scale capacitance by gain of preceding stage
  - Stage 1 consumes half of total power
  - Adding one bit means power goes up 4x
- Caveat
  - Usually impractical to scale capacitors down to  $C/2^m$

# Stage Scaling Example


Number of Amplifiers	13	12	11	10
Stage Capacitances	1	1/4	1/16	1/64
	1/2	1/8	1/32	1/128
	1/4	1/16	1/64	1/128
	1/8	1/32	1/128	1/128
	1/16	1/64	1/128	1/128
	1/32	1/128	1/128	1/128
	1/64	1/128	1/128	1/128
	1/128	1/128	1/128	
	1/128	1/128		
	1/128			
$\Sigma C$	2.03	0.54	0.17	0.086
$C_{\text{single}}$	1/2	1/8	1/32	1/128
Relative Power Pipeline/Single SC Stage ( $\Sigma C/C_{\text{single}}$ )	4.06	4.32	5.44	11.01

- Example is simplistic, but in line with state-of-the art
  - 10bits ~0.5mW/Msample/s, 12bits ~2mW/Msample/s

# Pipeline ADC Limit Line

 

# $G_m$ -C Integrator

 


$$IM_3 \cong \frac{3}{32} \left( \frac{V_{id,max}}{V_{ov}} \right)^2$$

$$\eta_{cur} = \frac{i_{od,max}}{I_{bias}}$$

$$\eta_{cur} \cong \frac{V_{id,max}}{V_{ov}} = \sqrt{\frac{32}{3} IM_3}$$

- Only a small fraction of bias current can be steered into load
  - E.g.  $IM_3=60\text{dB}$ ,  $\eta_{cur}=10\%$

# Gm-C Limit Line

 

# Low SNR

- Power of matching limited class-B circuit [Kinget, CICC 1996]


$$P = 24 \cdot C_{ox} \cdot A_{VT}^2 \cdot f_{sig} \cdot \left( \frac{V_{sig,rms}}{3 \cdot \sigma_{Vos}} \right)^2$$

- Refined result for flash ADC, assuming
  - Class-A, 1/2 LSB matching with  $3\sigma$ -confidence,  $2^B$  components, additional  $E_{dyn}$  per clock cycle, partial supply usage ( $\alpha$ )

$$P = \left( 12\pi \cdot \frac{1}{\alpha} \cdot C_{ox} \cdot A_{VT}^2 \cdot 2^{3B} + 2 \cdot E_{dyn} \cdot 2^B \right) \cdot f_{sig}$$

- Example:  $\alpha=2/3$ ,  $C_{ox}=15\text{fF}/\mu\text{m}^2$ ,  $A_{vt}=3\text{mV}\cdot\mu\text{m}$ ,  $E_{dyn}=60\text{fJ}$  ( $\sim 10$  gates in  $0.13\mu\text{m}$  CMOS)

# End Result

 



# Discussion

---

- Shown results include only minor assumptions about technology
- Scaling brings some good, some bad news offsetting each other
  - Lower  $V_{DD}$ , lower  $V_{swing}/V_{DD}$ , ...
  - + Lower  $E_{dyn}$ , higher  $f_t$  enables moderate/weak inversion operation with high  $g_m/I_D$ , ...
- Limit lines won't move much, unless someone hands us a new disruptive technology

# **EE 240C**

## **Analog-Digital Interface Integrated Circuits**

### **Digitally Assisted Analog Circuits**


# Future Opportunities

---


- More intelligent ADCs
  - Improved average power dissipation by adapting to instantaneous speed/resolution requirements
- "Minimalistic" ADCs using significantly simpler circuits
  - Analog front-end:
    - Meet noise specification
    - Relax systematic error specs, e.g. distortion
  - Digital compensation of resulting non-idealities
  - Digital post-processing is (within limits) "free" in terms of area and energy
 
# Digital Logic Energy Trend

Mainstream ADC technologies, standard logic library data



# ADC/Digital Logic Energy Ratio

 


[Boris Murmann]

# Energy Ratio in 2007

- Interpretation for digitally enhanced ADCs (energy centric)

SNDR	$E_{\text{ADC}}/E_{\text{NAND2}}$
30	4,679
50	37,432
70	299,479
90	2,396,045

 

Additional digital processing is costly!




Several tens of thousand gates are "free"



Use as many gates as you can fit...

# Digital Logic Gate Density Trend

 

# **EE 240C**


## **Analog-Digital Interface Integrated Circuits**

### **ADC Testing**


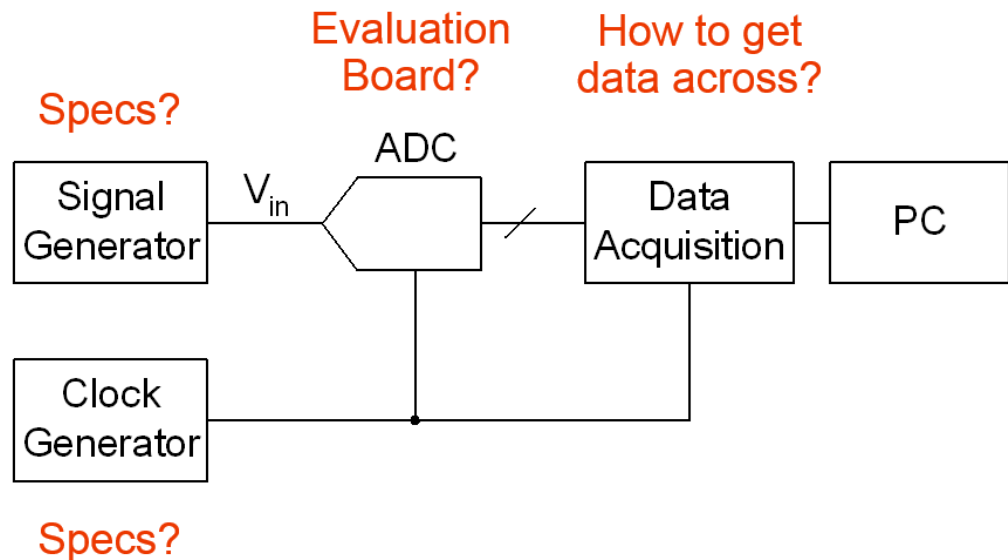
# Testing ADCs

- Test equipment
  - Signal source
  - Clock generator
  - Supplies
- Test fixture
- Data acquisition



[Boris Murmann]

# Signal Source

- Want: SFDR > 85dB @  $f_{in} = f_s/2 = 37.5\text{MHz}$




- Harmonic distortion ( $f > 1\text{MHz}$ ): -35dBc
- Need something better...



- ~ \$40k
- $f = 100\text{kHz} \dots 3\text{GHz}$
- Harmonic distortion ( $f > 1\text{MHz}$ ): -30dBc !

# Filtering Out Harmonics

 

- Given  $HD = -30\text{dBc}$ , we need a stopband rejection  $> 60\text{dB}$  to get  $SFDR > 90\text{dB}$

# Available Filters

## Elliptical Function Bandpass Filters 1kHz to 20MHz



[www.tte.com](http://www.tte.com), or  
[www.allenavionics.com](http://www.allenavionics.com)

### Stopband to Passband Bandwidth Ratios

Series Number	BWR	*Stopband Attenuation
Q34	4.0:1	-40dBc
Q40	4.0:1	-40dBc
Q36	10.0:1	-60dBc
Q54	2.5:1	-40dBc
Q70	3.5:1	-60dBc
Q56	3.5:1	-60dBc

- Want to test at many frequencies  
→ Need to have many different filters!

# Tunable Filter




[www.klmicrowave.com](http://www.klmicrowave.com)

K&L Model	Frequency Range (MHz)	Passband Insertion Loss	Length Inch/mm	Width Inch/mm	Height Inch/mm
5BT-30/76-5-N/N	30-76	1.3 dB Max	9.80/249	5.38/137	2.75/50
5BT-63/125-5-N/N	63-125	1.3 dB Max	9.80/249	5.38/137	2.75/50
5BT-125/250-5-N/N	125-250	1.3 dB Max	9.80/249	5.38/137	2.75/50
5BT-250/500-5-N/N	250-500	1.0 dB Max	9.80/249	5.38/137	2.75/50
5BT-375/750-5-N/N	375-750	1.0 dB Max	9.80/249	5.38/137	2.75/50
5BT-500/1000-5-N/N	500-1000	1.0 dB Max	9.80/249	5.38/137	2.75/50
5BT-750/1500-5-N/N	750-1500	1.0 dB Max	9.80/249	5.38/137	2.75/50
5BT-1000/2000-5-N/N	1000-2000	1.0 dB Max	7.38/187	2.88/73	2.75/50
5BT-1200/2600-5-N/N	1200-2600	1.0 dB Max	7.38/187	2.88/73	2.75/50

Beware: The filters themselves also introduce distortion
 
# Clock Generator

- The clock signal controls sampling instants – which we assumed to be precisely equidistant in time (period  $T$ )
  - See earlier lecture for a discussion of aperture uncertainty
- Typically use sine wave and "square up" with inverter chain



# Jitter Supression

---

- Once we have a good enough generator, other circuit and test setup related issues may determine jitter
- Usually, clock jitter in the single-digit picosecond range can be prevented by appropriate design techniques
  - Separate supplies
  - Separate analog and digital clocks
  - Short inverter chains between clock source and destination
- Few, if any, other analog-to-digital conversion non-idealities have the same symptoms as sampling jitter
  - RMS noise proportional to input frequency
  - RMS noise proportional to input amplitude
- So, if sampling clock jitter is limiting your dynamic range, it's easy to tell, but may be difficult to fix ...

# Evaluation Board

---

- Planning begins with converter pin-out
  - Uhps, my clock pin is right next to a digital output ...
- Not "black magic", but requires extreme care
- Key aspects
  - Supply/ground routing
  - Bypass capacitors
  - Coupling between signals
- Good idea to look at ADC vendor datasheets for example layouts/schematics/application notes
  - E.g. Analog Devices AD9235 Data Sheet



# One Thing to Remember...

---

- A converter does not just have one "input"
  - Clock
  - Power supply, ground
  - Reference voltage
- For good practices on how to avoid issues see e.g.
  - Analog Devices Application Note 345:  
"Grounding for Low-and-High-Frequency Circuits"
  - Maxim Application Note 729:  
"Dynamic Testing of High-Speed ADCs, Part 2"

# How to Get the Bits Off Chip?

- "Full swing" CMOS signaling works well for  $f_{CLK} < 100\text{MHz}$
- But we want to build faster ADCs ...
- Alternative to CMOS: LVDS – Low Voltage Differential Signaling
- LVDS vs. CMOS:
  - Higher speed, also more power efficient at high speed
  - Two pins/bit!


 


Figure 1. LVDS Output Levels

Analog Devices Application Note 586: "LVDS Data Outputs for High Speed ADCs"

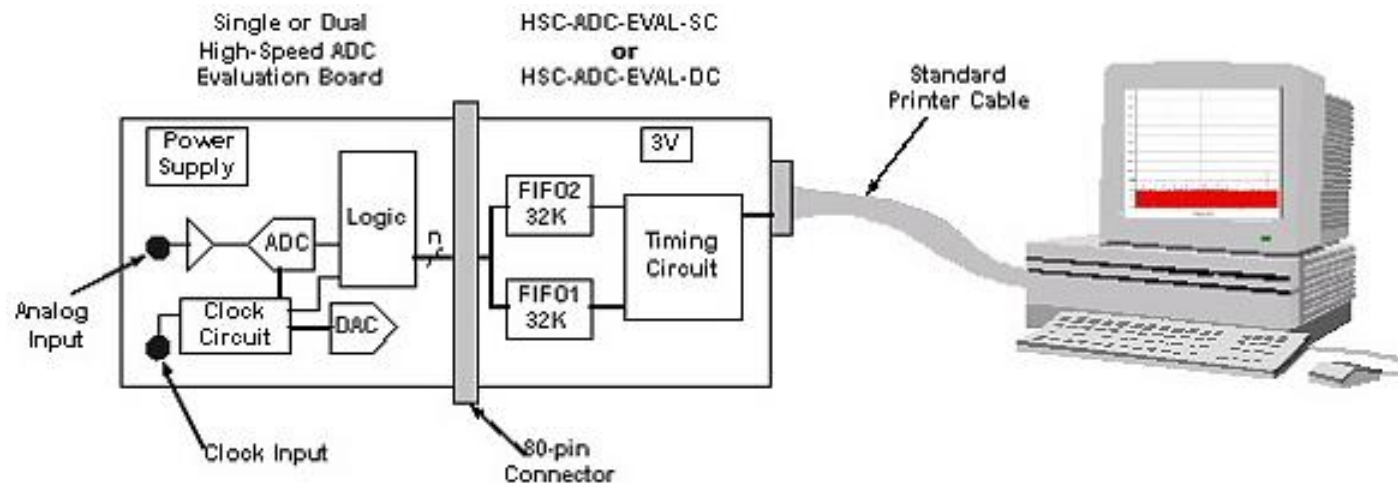
# Data Acquisition

- Several options:
  - Logic analyzer with PC interface
  - FIFO board, interface to PC DAQ card
  - Vendor kit, simple interface to printer port:



[Analog Devices, [High-Speed ADC FIFO Evaluation Kit](#)]

# Complete Setup

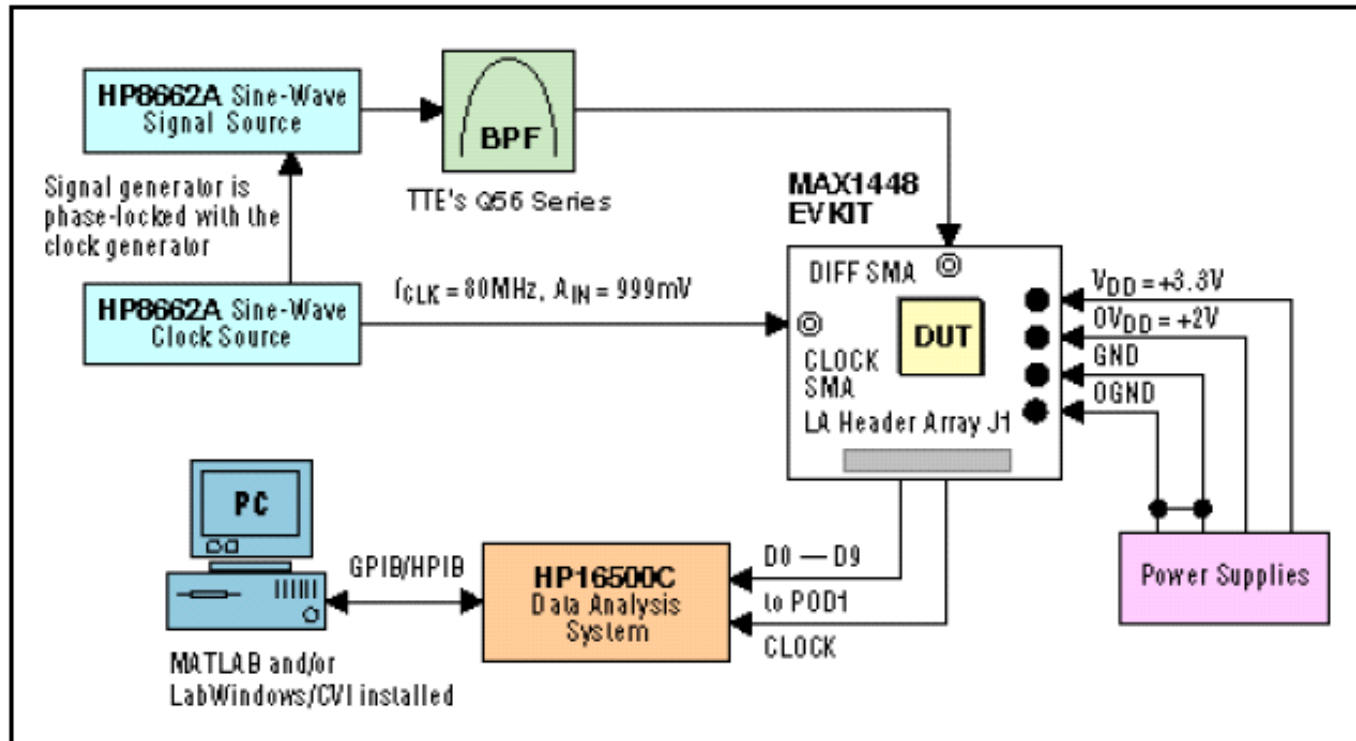

[Maxim Application Note 729: "Dynamic Testing of High-Speed ADCs, Part 2]